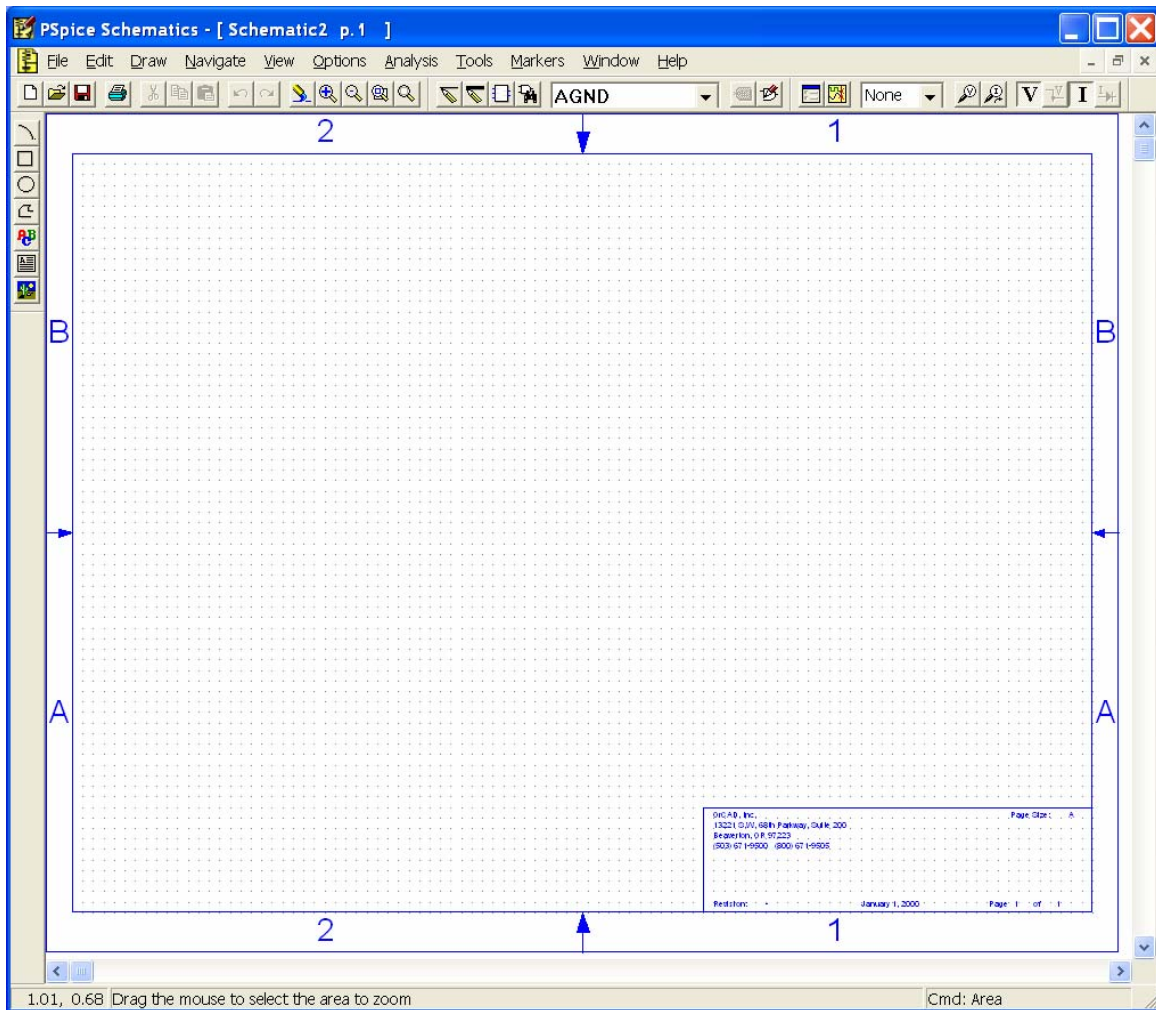


Short Tutorial on PSpice


Spice is a program developed by the EE Department at the University of California at Berkeley for computer simulation of analog circuits. In its original form you tell Spice what elements are in the circuit (resistors, capacitors, etc.), and then enter the circuit diagram as an ASCII file showing what nodes each element is connected to. Every node is assigned a number, and there is always a ground node, which is Number 0. You then tell Spice what information you want -- bias conditions, frequency response, and/or transient response. Spice does the circuit analysis and puts out an ASCII file with the information.

Using Spice is not very intuitive to use because the input is an ASCII file rather than a circuit diagram, and the output is another ASCII file rather than a graph. Several companies have developed graphical user interfaces for Spice, which make it much easier to use. One of the most popular is PSpice. PSpice provides a free student version of its program which can be downloaded from www.pspice.com.


To use PSpice, start with the PSpice *Schematics* program. When you start up you will get a screen which looks like this:




To put in a component, use the *Draw* drop-down menu, and select *Get new part* (or use the shortcut Ctrl-G). This will bring up a dialog box which will allow you to select parts from libraries. If the part you want is not on the list, try another library – parts such as transistors will probably be in *eval.slb*, while things such as voltage sources will be in *analog.slb*. Select the part you want and place it on the schematic:

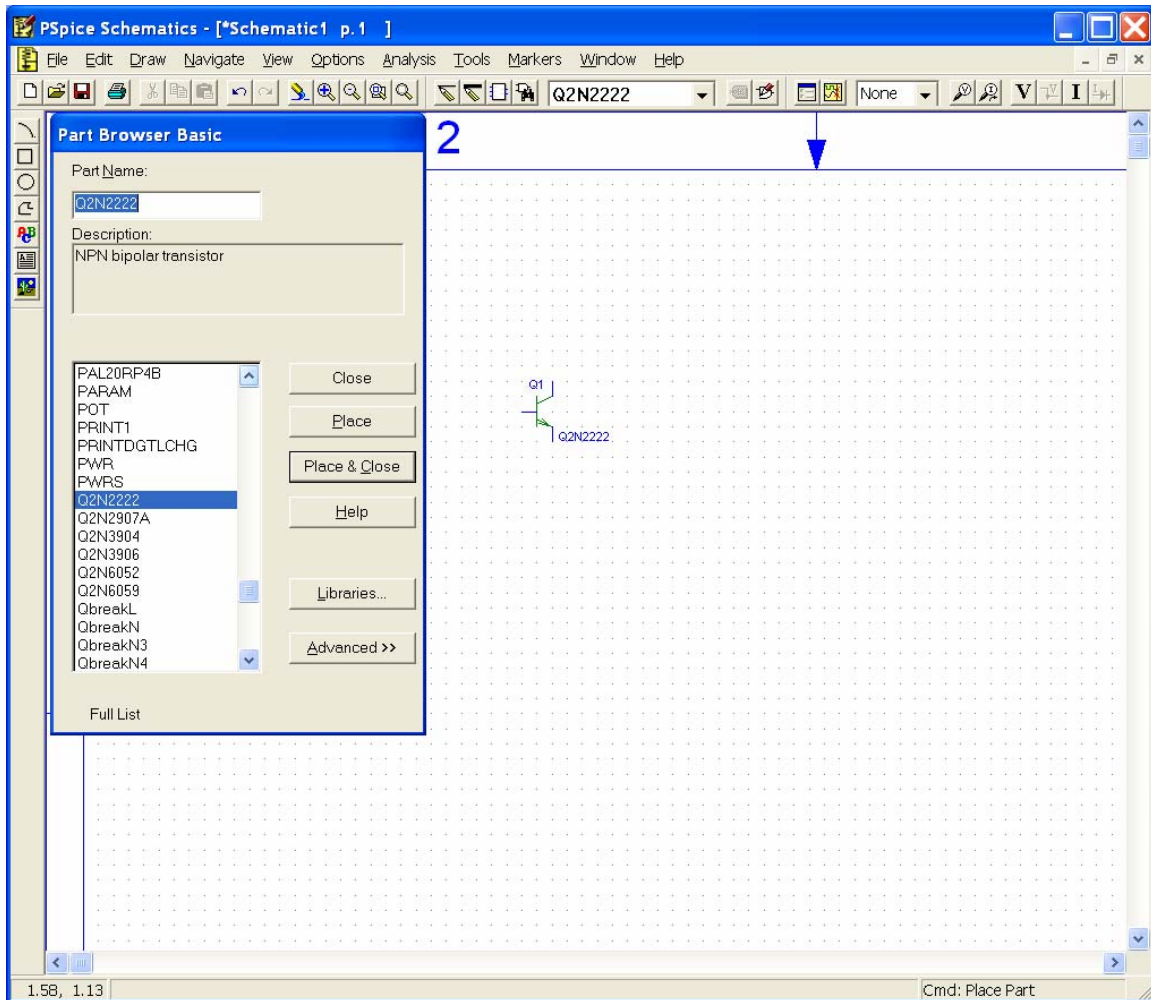


Continue placing the components you need. (If need a component of the same type as one you have already placed, you can use the *Draw – Place Part* (Ctrl-P) shortcut.) You can rotate an object by clicking on it to highlight it, then use *Edit – Rotate* (or Ctrl-R). You can change the value of a component by double-clicking on the component value, and entering a new value. You can connect components together by placing wires – *Draw – Wire* (or Ctrl-W). Be sure to place an analog ground (AGND). Use the component VDC for DC power supplies, and VAC for signal sources. When done you will have something which looks like this:

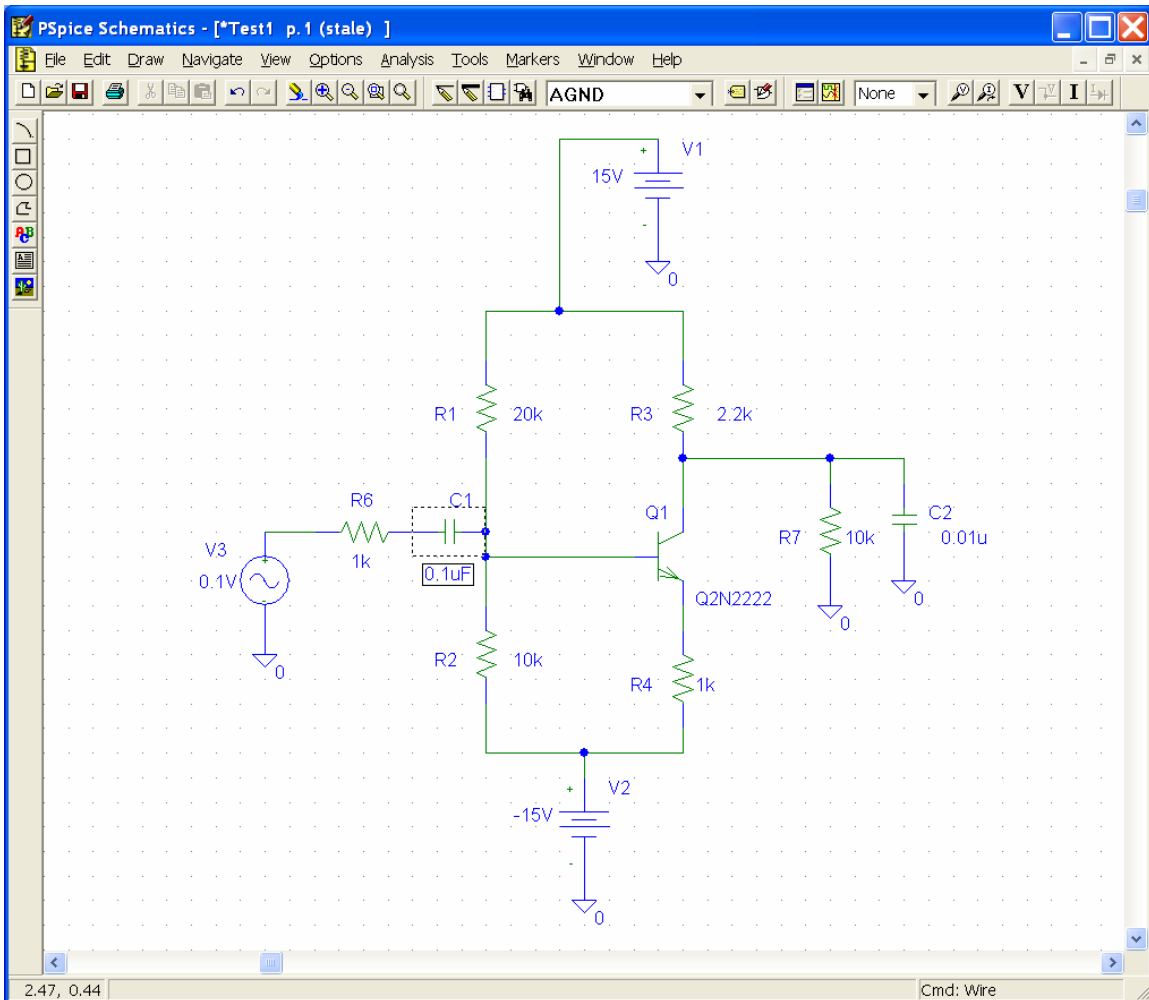

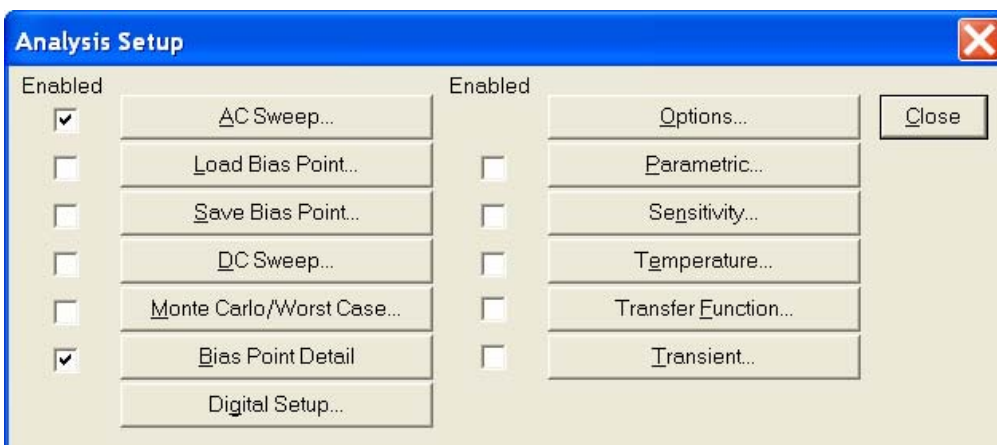
Be sure to save the file, then go to *Analysis – Setup*. Here you will tell PSpice what you want it to do. Always select *Bias Point Detail*. In this case we will also select *AC Sweep* which will give the frequency response of the circuit.



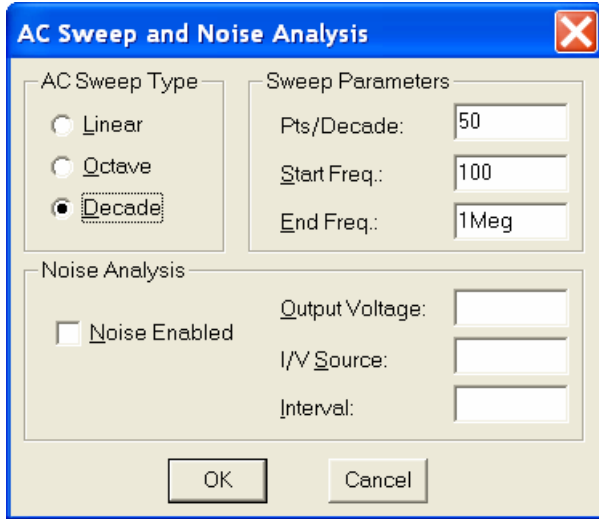
Click on *AC Sweep* to tell what frequency range you want to use:



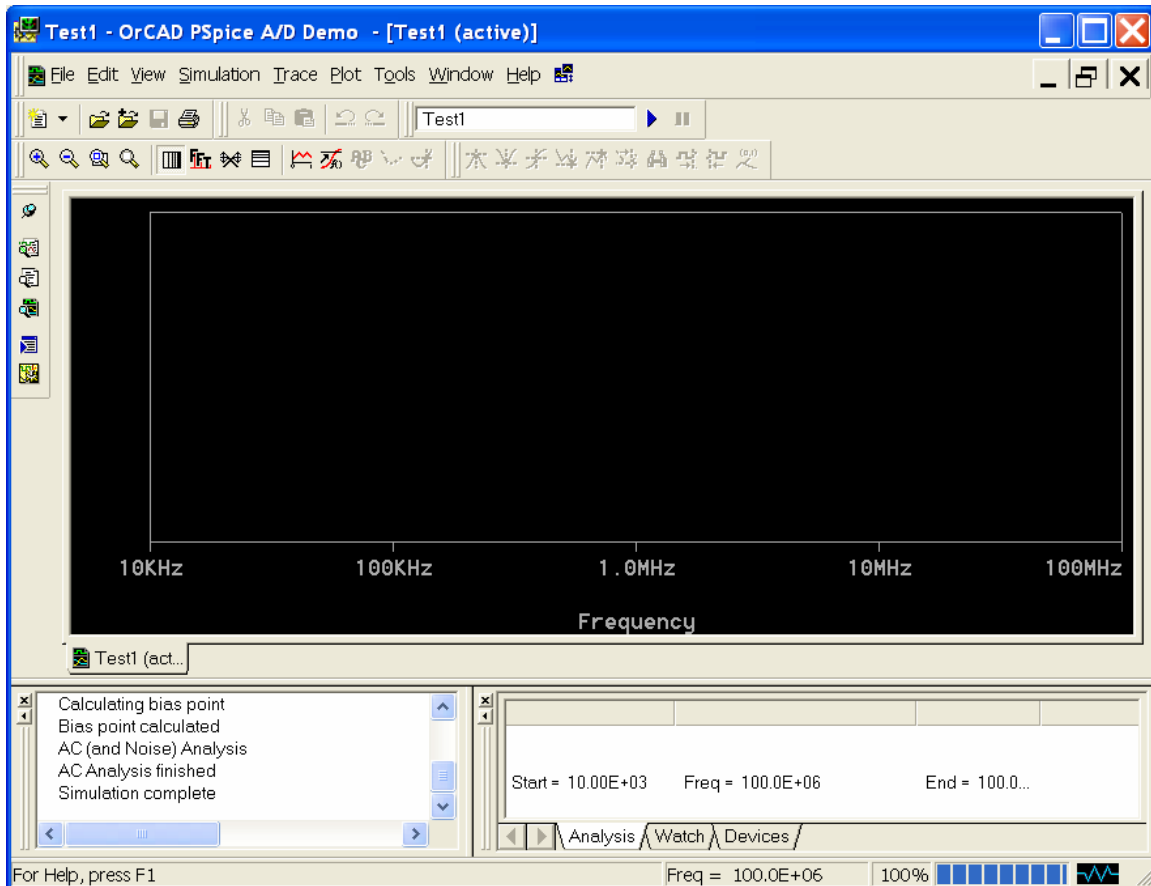
Here we will cover the frequencies from 100 Hz to 1 MHz. (Note: Use Meg for 10^6 . If you use M, PSpice will interpret this as milli (10^{-3} .) Now choose *Analysis* – *Simulate* and PSpice will run, and pop up an analysis window:



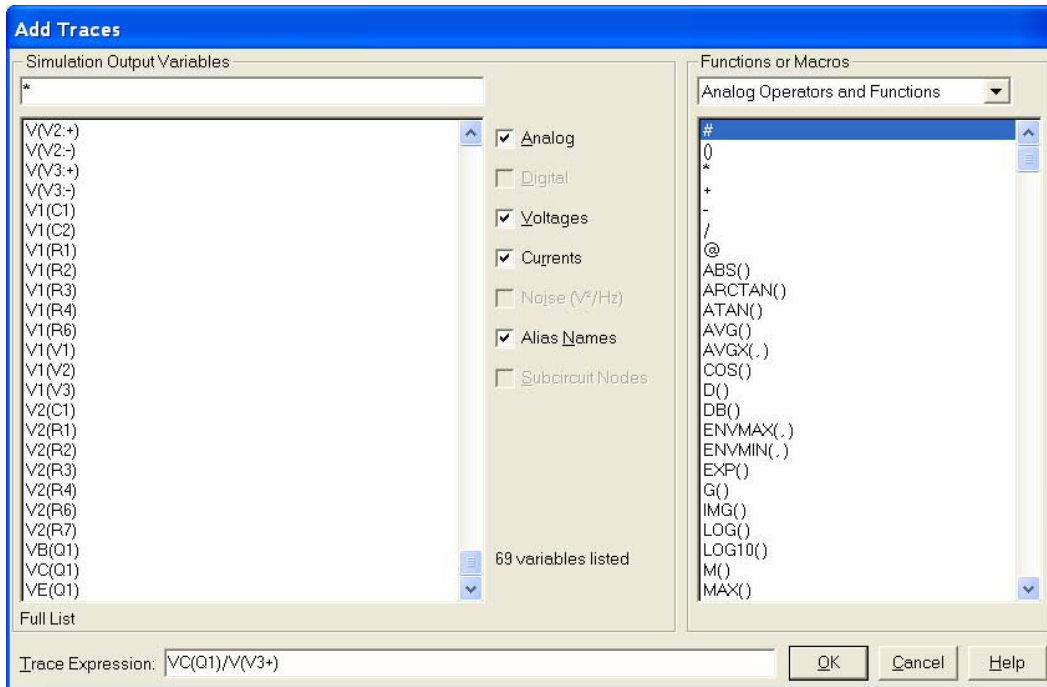In this window choose *Trace – Add Trace*. Since we're interested in the gain of the circuit, we want to plot the output voltage divided by the input voltage. The output voltage is the voltage at the collector of Q1, and the input voltage is the voltage at the + terminal of V3, so we plot $VC(Q1)/V(V3+)$.




We now see the frequency response plot:

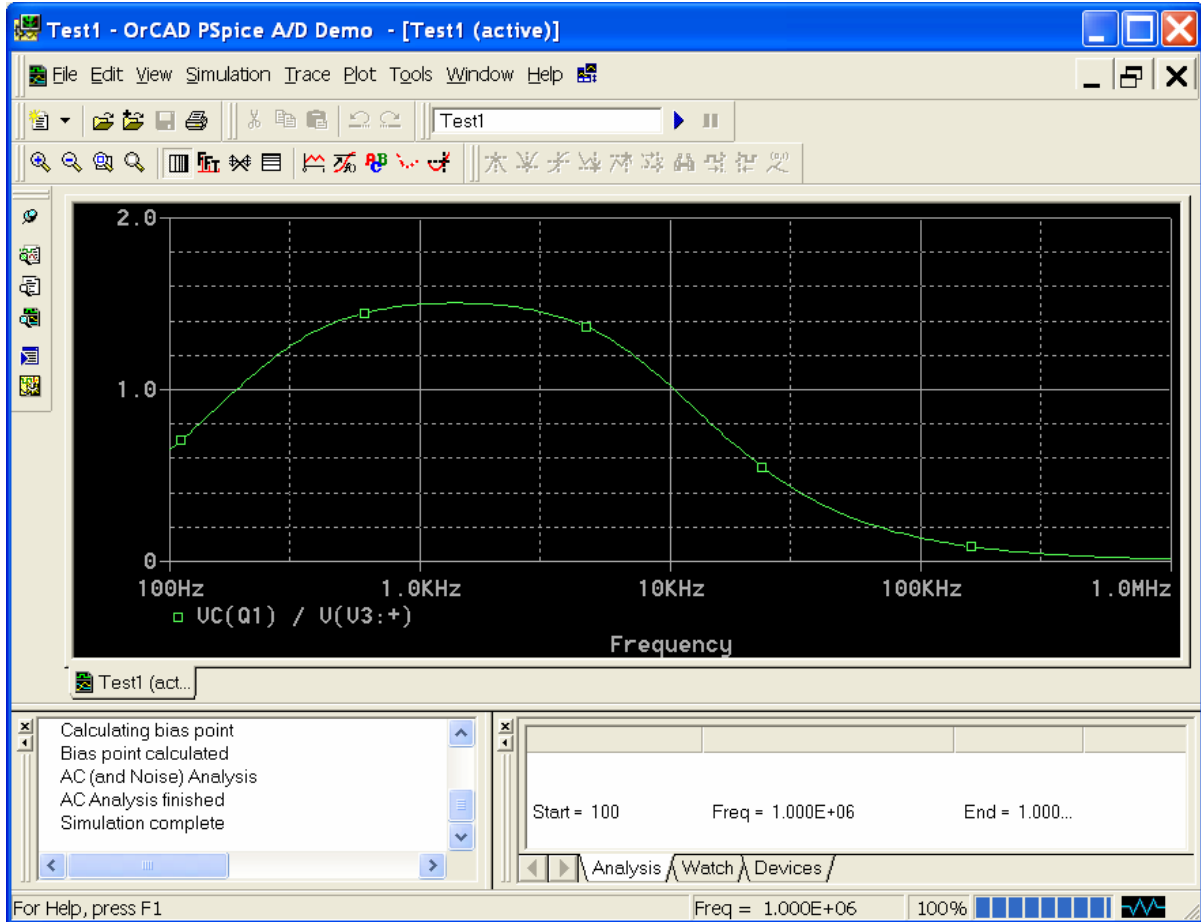

We see the circuit has a gain of about 1.5 at a frequency of 1 kHz. The theoretical value is about $(RL \parallel RC)/RE$, or 1.8.

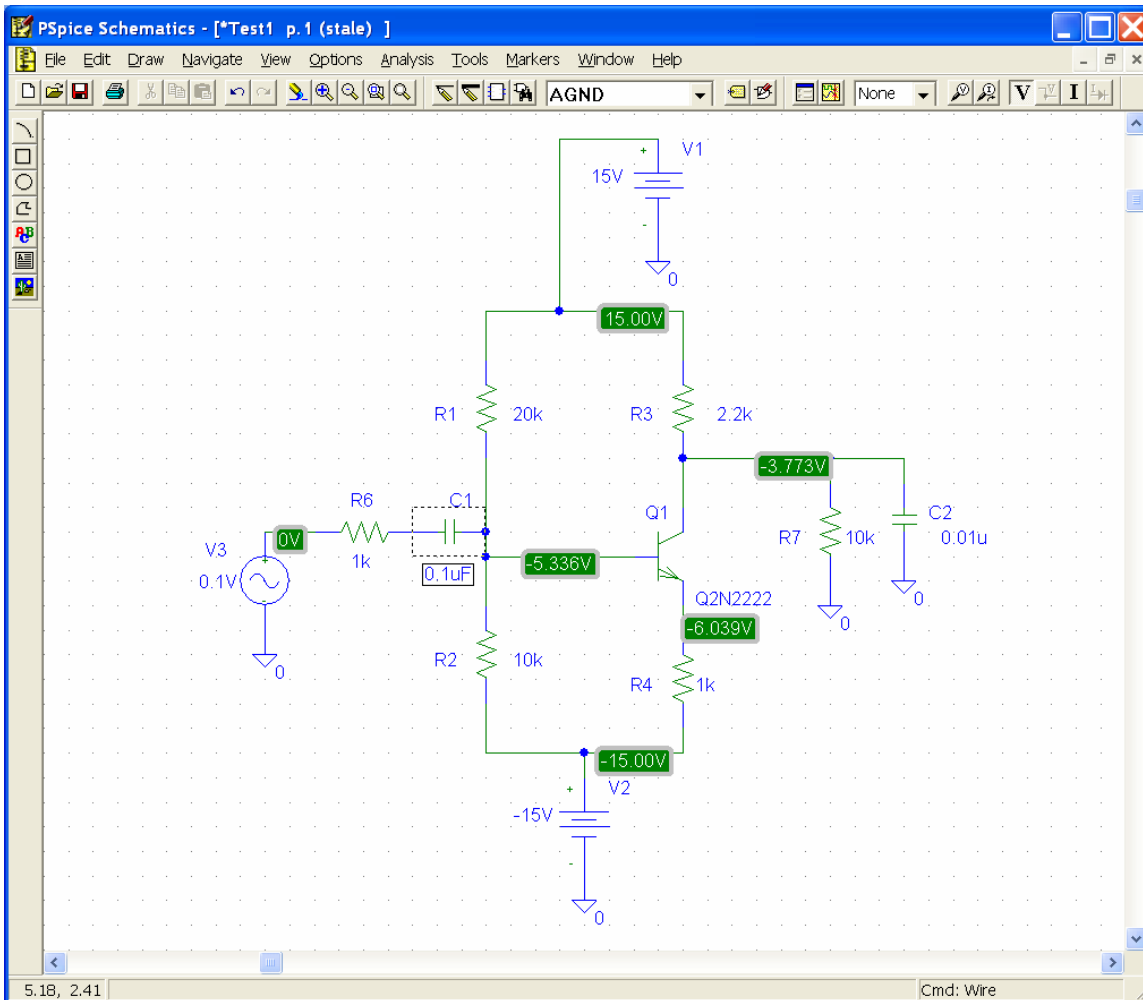To see the bias voltages and currents, you can look at the ASCII output file. However, it is easier to go back to the *Schematic* program and select *Analysis – Display Results on Schematic* and then *Enable Voltage Display* and/or *Enable Current Display*. Here is the schematic with the bias voltages displayed:



It is instructive to look at the ASCII output file. Here is part of it:

```

Q_Q1          $N_0002 $N_0001 $N_0003 Q2N2222
R_R4          $N_0004 $N_0003 1k
R_R2          $N_0004 $N_0001 10k
C_C2          $N_0002 0 0.01u
V_V2          $N_0004 0 -15V
R_R6          $N_0006 $N_0005 1k
V_V3          $N_0006 0 DC 0V AC 0.1V
V_V1          $N_0007 0 15V
R_R1          $N_0001 $N_0007 20k
R_R3          $N_0002 $N_0007 2.2k
R_R7          0 $N_0002 10k
C_C1          $N_0005 $N_0001 0.1uF

```

This is the type of file Spice needs – it shows that Q1 is a 2N2222 transistor, and its collector is connected to Node 2, its base to Node 1, and its emitter to Node 3.

Later on in the output file we find the specifications for the 2N2222 transistor:


```
      Q2N2222
      NPN
      IS  14.340000E-15
      BF  255.9
      NF  1
      VAF  74.03
      IKF  .2847
      ISE  14.340000E-15
      NE  1.307
      BR  6.092
      NR  1
      RB  10
      RC  1
      CJE  22.010000E-12
      MJE  .377
      CJC  7.306000E-12
      MJC  .3416
      TF  411.100000E-12
      XTF  3
      VTF  1.7
      ITF  .6
      TR  46.910000E-09
      XTB  1.5
      CN  2.42
      D   .87
```

The standard Spice model assumes the 2N2222 has a β of 255.9. You can edit the transistor model if you want to use a different value of β .


We can also see the bias voltages at the nodes:

NODE	VOLTAGE	NODE	VOLTAGE
(\$N_0001)	-5.3359	(\$N_0002)	-3.7732
(\$N_0003)	-6.0390	(\$N_0004)	-15.0000
(\$N_0005)	0.0000	(\$N_0006)	0.0000
(\$N_0007)	15.0000		

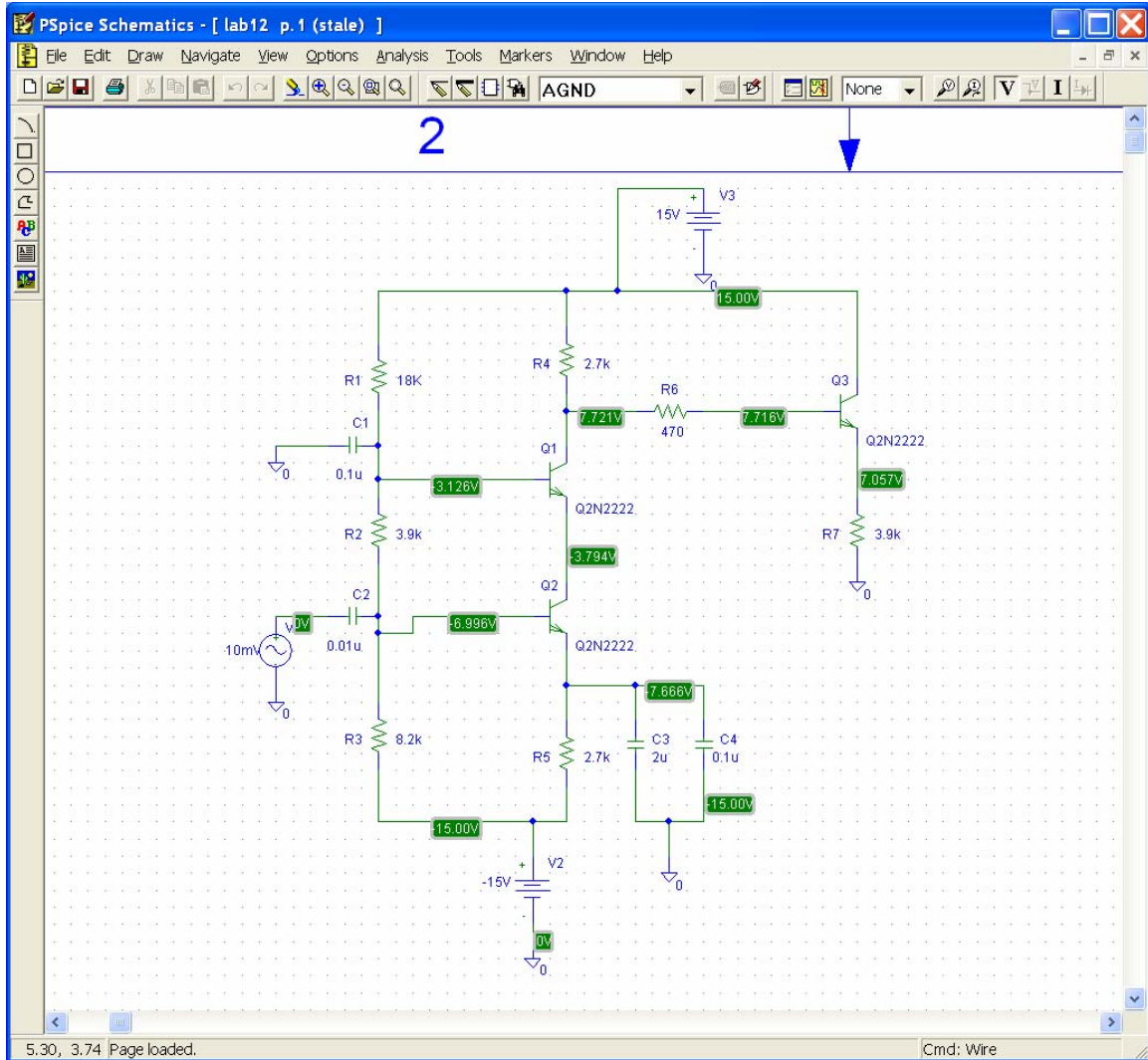
Here is the schematic for the RF amplifier circuit of Lab 12:



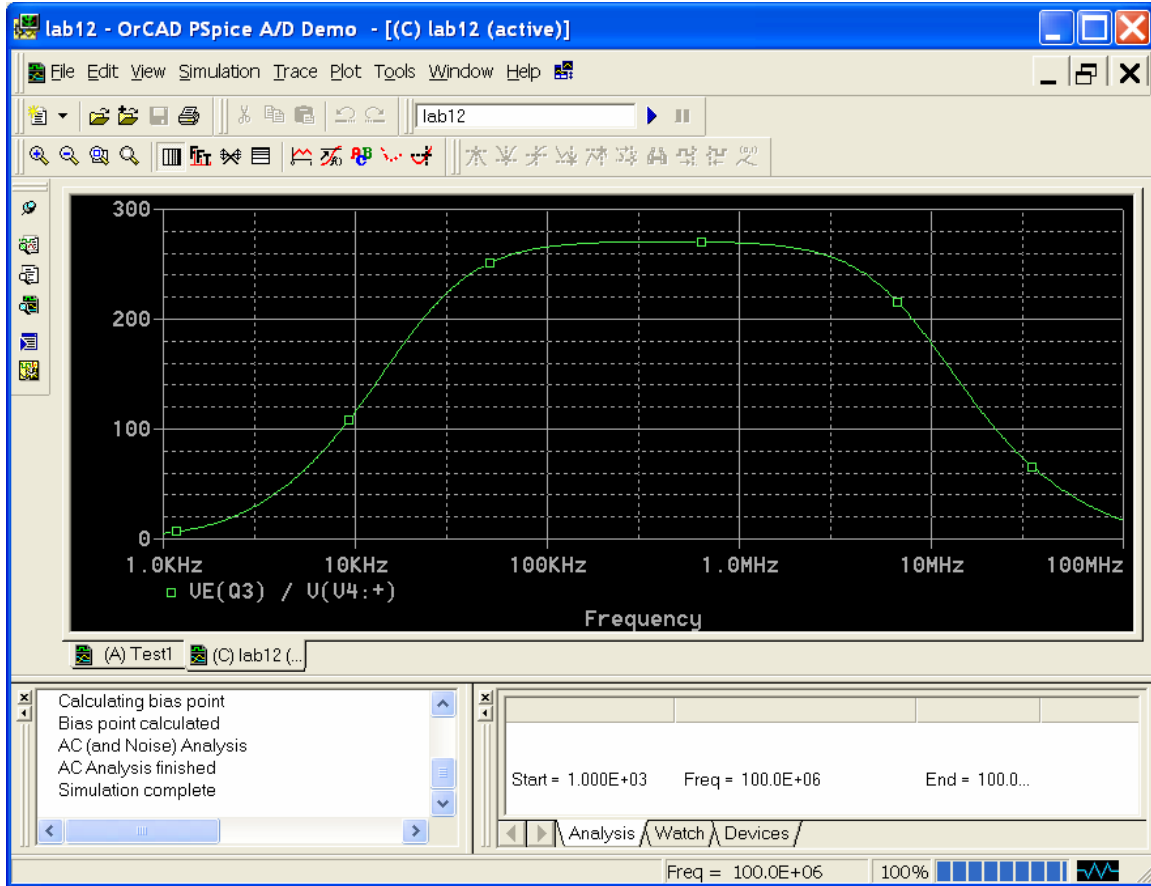
and the frequency response shows the passband gain is about 280:



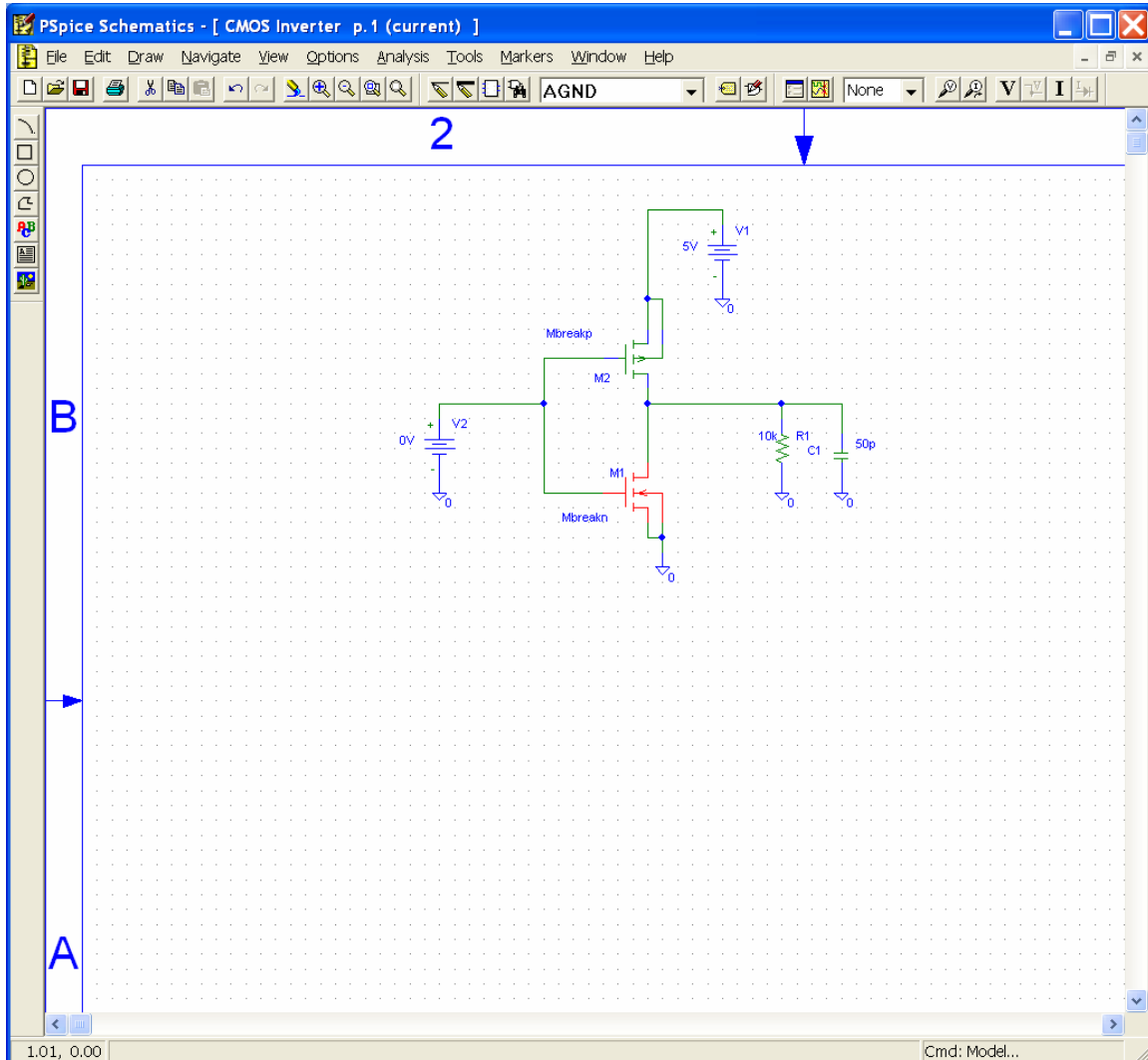
For some circuits the transient response is more important. For example, consider the CMOS inverter:



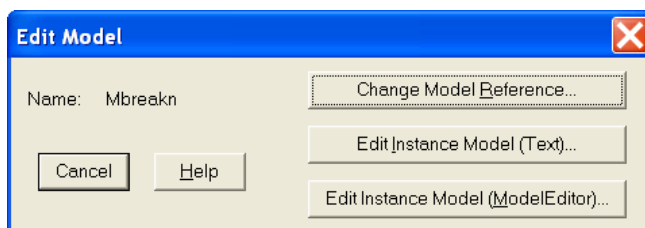The MOSFET models are located in the *breakout.slb* library, under the names *Mbreakn* (NMOS) and *Mbreakp* (PMOS). We now need to define the parameters of the MOSFETS: highlight the NMOS transistor and select *Edit – Model*:




Select *Edit Instance Model (Text)*:

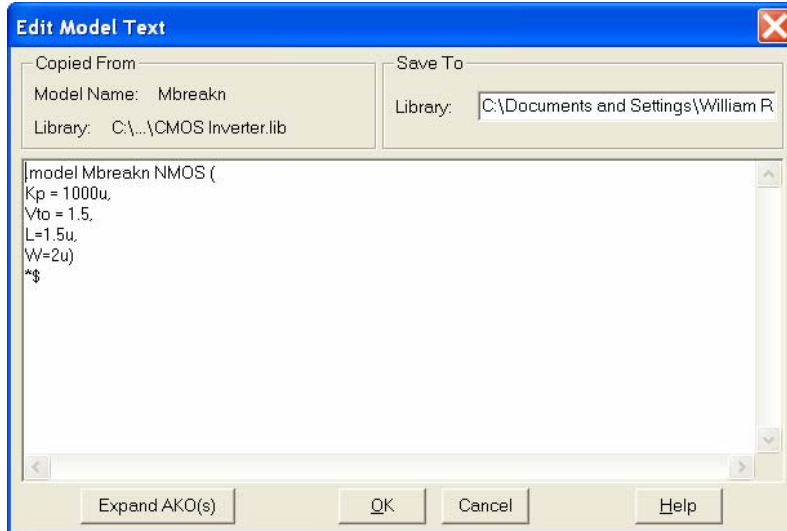


and enter appropriate values for the parameters. Here we have $k_n' = 100 \mu A/V^2$, $V_t = 1.5 V$, $L = 1.5 \mu m$, and $W = 2 \mu m$.

Do the same for the PMOS transistor.

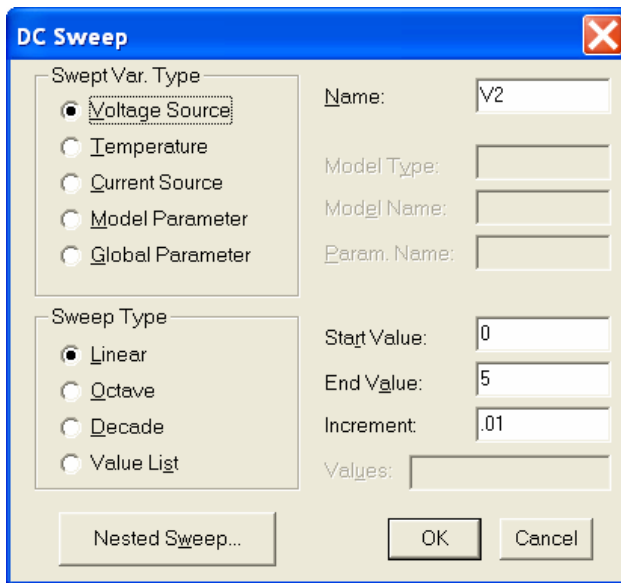Now we will do a DC sweep rather than an AC sweep. Choose *Analysis – Setup*, then select *DC Sweep*. Sweep source V2 from 0V to 5V at 0.01V increments:



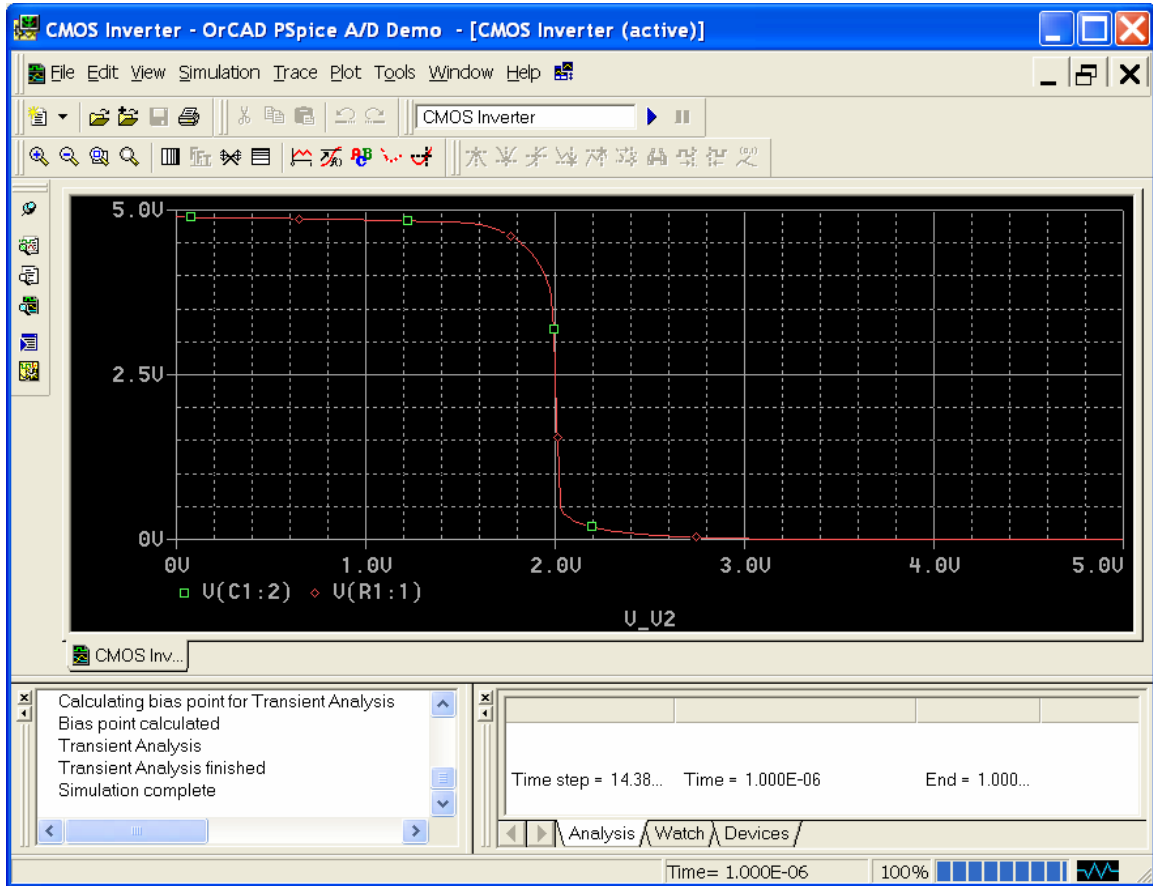In the Graph window, choose *Trace – Add Trace*, and add $V(R1:1)$, the voltage at the load resistor:




and we have the voltage transfer function for the inverter.

Let's look at the rise and fall times of the circuit. Change the input voltage source to a *VPWL* (piece-wise linear source). Double-click on the source, and enter the shape of the source voltage:

Name	Value
REFDES	= V6
T1	99.9n
V1	0
T2	100n
V2	5
T3	200n
V3	5
T4	200.1n

Include Non-changeable Attributes
 Include System-defined Attributes

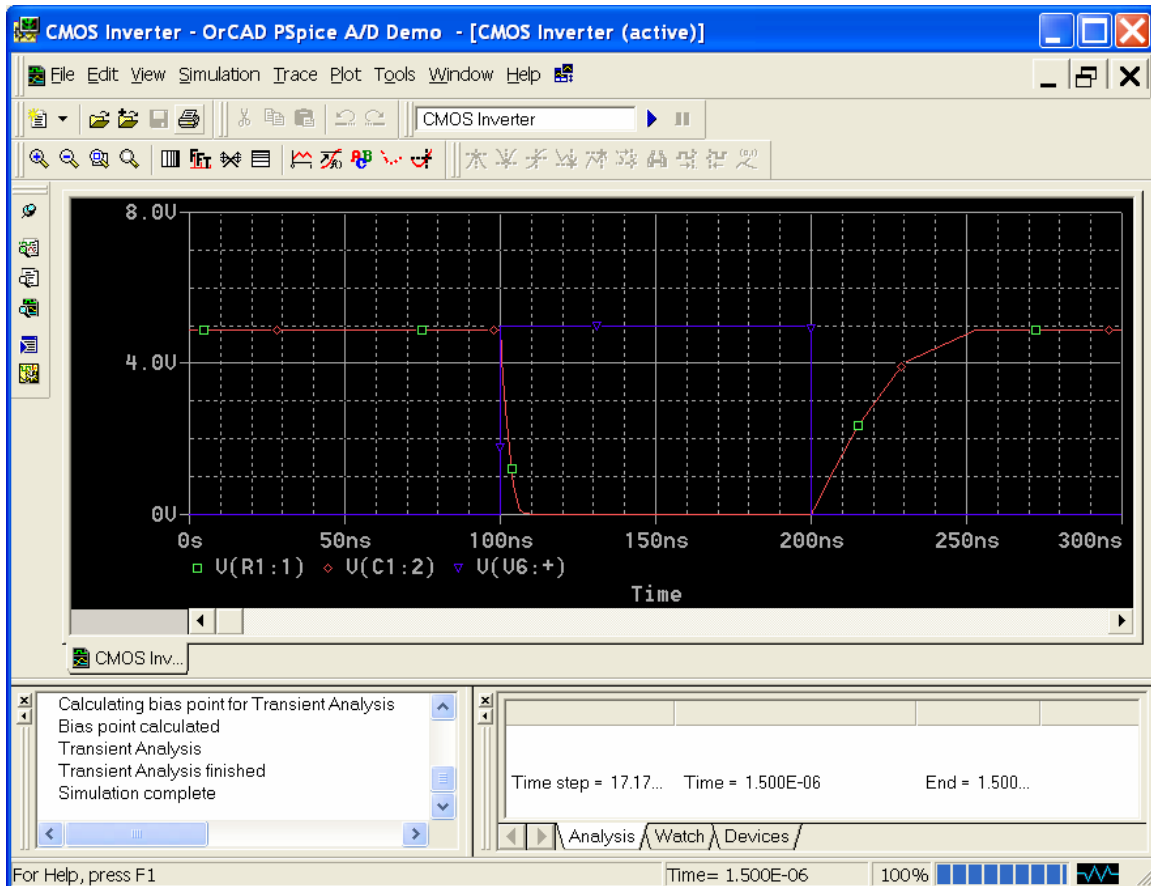Have the source change from 0 V at 99.9 ns to 5 V at 100 ns, then from 5 V at 200 ns to 0 V at 200.1 ns. This will give a pulse input with a 0.1 ns rise time. Under *Analysis – Setup*, choose *Transient*, and simulate the circuit. In the graph window plot $V(R1:1)$:



and we can see the rise and fall times of the CMOS inverter.