

EE321 – Fall 2002

Homework 2

Due September 9, 2002

1. Problem 1.13.

- Power dissipated is 24 mW.

2. Problem D1.15.

- Upper limit on V_i is 40 mV.

3. Problem 1.18.

- $A_v = 39$ dB
- $A_p = 78$ dB
- Largest sinewave input is 78 mV.
- Power available is 0.5 W. (Answer in book is wrong.)

4. Problem 1.27.

- Answer in book is correct.

5. Problem 1.29.

-

$$A_v = \frac{-\alpha v_s R_C}{(1 - \alpha)R_B + R_E + R_e}$$

- Answer in book is wrong.

6. Problem 1.34.

- Answer in book is correct.

7. Problem 1.42.

- Answer in book is correct.

8. Problem 1.43. Is $T_i(s)$ a high-pass or low-pass transfer function? Is $T_o(s)$ a high-pass or low-pass transfer function?

- Answer in book is correct.