


EE 321 - Exam 3

April 18, 1989

Name: _____

Closed book. One page of notes and a calculator are allowed. Show all work. Partial credit will be given. No credit will be given if an answer appears with no supporting work.

1. Consider the following circuit:

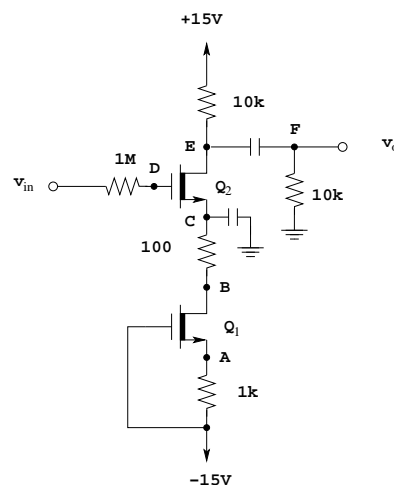

The MOSFET's are matched, and $k'_n(W/L) = 2 \text{ mA/V}^2$, and $V_t = -2 \text{ V}$. Ignore the output resistance r_o , and assume all capacitors are large (all AC signals are passed through, all DC signals are blocked).

- Find I_{D_1} , the drain current through Q_1 .
- What are the bias voltages V_A , V_B , V_C , V_D , V_E and V_F ?
- Draw the small-signal equivalent circuit for the amplifier.
- What is g_{m_2} , the transconductance of Q_2 ?
- What is the input resistance?
- What is the voltage gain v_o/v_i ?

$$(a) \quad I_{D1} = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS1} - V_{t1})^2 \quad (\text{assuming sat.})$$

$$\text{and } I_{D1} = (V_A - (-15V)) / 1k$$

$$V_{GS1} = V_{G1} - V_{S1} = -15V - V_A$$

$$\therefore \frac{1}{2} k_n' \left(\frac{W}{L}\right) (-15V - V_A - (-2V))^2 = (V_A - (-15V)) / 1k$$

$$\frac{1}{2} (2 \text{ mA/V}^2) (-13V - V_A)^2 = (V_A + 15V) / 1k$$

Multiply through by 1k

$$1 \text{ V}^{-1} (-13V - V_A)^2 = (V_A + 15V)$$

$$169 + 26V_A + V_A^2 = V_A + 15$$

$$V_A^2 + 25V_A + 154 = 0$$

$$V_A = \frac{-25 \pm \sqrt{(25)^2 - 4(154)}}{2} = \frac{-25 \pm 3}{2} = -11, -14$$

$$\text{If } V_A = -11V, \text{ then } V_{GS1} = V_{G1} - V_A = -15 - (-11) = -4V.$$

$V_{GS1} < V_{t1}$, so Q is off - cannot be

$$\text{If } V_A = -14V, \text{ then } V_{GS1} = V_{G1} - V_A = -15 - (-14) = -1V$$

$V_{GS1} > V_{t1}$, so Q on - correct

$$\therefore V_A = -14V$$

$$I_{D1} = \frac{V_A - (-15V)}{1k} = \frac{-14V + 15V}{1k} = 1 \text{ mA}$$

$$\underline{\underline{I_{D1} = 1 \text{ mA}}}$$

$$(b) \quad V_A = -14V \quad (\text{from (a)})$$

$$V_D = 0V \quad (\text{cap open for DC})$$

$$V_F = 0V \quad (\text{"})$$

$$I_{D2} = I_{D1} \Rightarrow V_{GS2} = V_{GS1} = -1V$$

$$V_{GS2} = V_D - V_C \Rightarrow V_C = V_D - V_{GS2} = 0 - (-1V) = 1V$$

$$\therefore V_C = +1V$$

$$\frac{V_C - V_B}{100} = I_D = 1mA$$

$$V_B = V_C - I_D(100) = 1V - (1mA)(100\Omega) = 0.9V$$

$$\frac{15V - V_E}{10k} = I_D$$

$$V_E = 15V - I_D(10k) = 15V - (1mA)(10k) = 5V$$

$$V_A = -14V$$

$$V_B = 0.9V$$


$$V_C = 1V$$

$$V_D = 0V$$

$$V_E = 5V$$

$$V_F = 0V$$

(c)

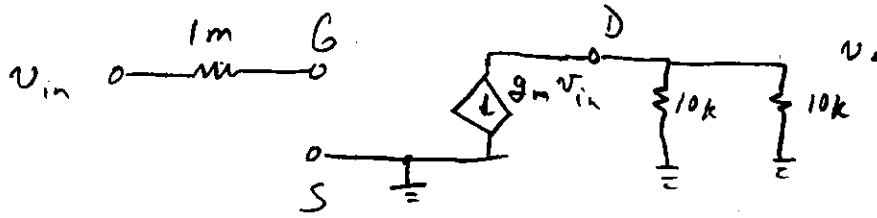

$$(d) \quad g_m = \frac{I_D}{(V_{GS_2} - V_{t_2}) / 2} = \frac{1\text{mA}}{(-1\text{V} - (-2\text{V})) / 2} = 2\text{mA/V}$$

(e) No current flows into gates, so $R_{in} = \infty$


(f) From small signal model

$$v_o = -g_m v_{in} (10\text{k} \parallel 10\text{k})$$

$$\frac{v_o}{v_i} = -g_m (5\text{k}) = -(2\text{mA/V})(5\text{k}) = -10$$


2. For the following problem it is known that $V_t = 2\text{ V}$ for the NMOS FET, but $k'_n(W/l)$ is not known.

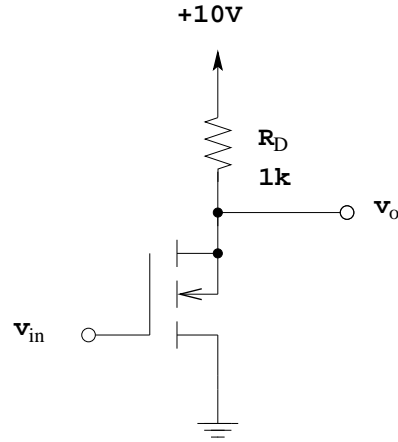- (a) Your lab partner builds the following circuit using the MOSFET, but the circuit fails to function. What mistake has been made, and how would you correct it?



- (b) After making the correction, you find that $V_o = 6\text{ V}$ when $V_{in} = 4\text{ V}$. Determine $k'_n(W/L)$ for the MOSFET.
- (c) The MOSFET is next used as a switch by changing R_D from $1\text{ k}\Omega$ to $100\text{ k}\Omega$. Find V_D when $v_{in} = 0\text{ V}$, and and when $v_{in} = 4\text{ V}$.

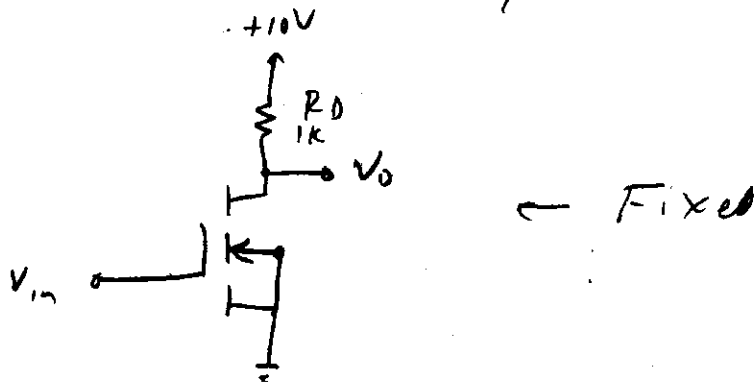(a) Need to connect body to source, not drain



(b) $V_{in} = 4V \Rightarrow V_{GS} = 4V$

$V_o = 6V \Rightarrow I_D = \frac{10V - 6V}{1k} = 4mA$

$V_{DS} = V_o = 6V$

$V_{DS} > V_{GS} - V_{th}$ so Q in saturation

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_{th})^2$$


$$4mA = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (4 - 2)^2$$

$$k_n' \left(\frac{W}{L}\right) = 2mA/V^2$$

(c) $V_{in} = 0 \Rightarrow V_{GS} = 0 \Rightarrow Q \text{ off} \Rightarrow I_D = 0 \Rightarrow V_o = 10V$

$V_{in} = 4V \Rightarrow V_{GS} > V_{th}$; Q will be in triode

Q will act like a resistor

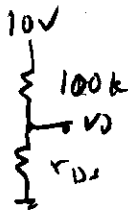


$$V_o = \frac{r_{DS}}{10k + r_{DS}} 10V$$

$$r_{DS} = \frac{1}{k_n' \left(\frac{W}{L}\right) (V_{GS} - V_{th})} = \frac{1}{(2mA/V^2)(4V - 2V)}$$

$$= 250\Omega$$

$$V_o = \frac{250\Omega}{10k + 250} 10V = 0.24V$$

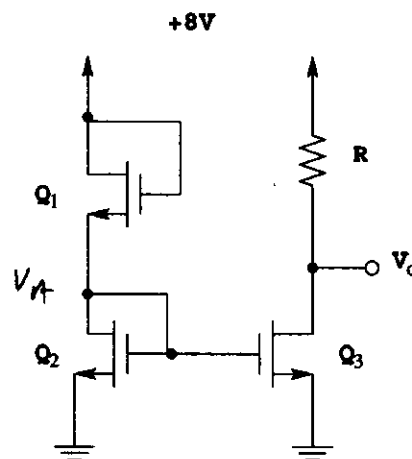3. For the MOSFETs in the circuit below $k'_n(W/L) = 5 \mu\text{A}/\text{V}^2$, and $V_t = 2 \text{ V}$. Select R to obtain $V_o = 6 \text{ V}$. Neglect the effect of r_o .



Q_1 and Q_2 identical

$$I_{D1} = I_{D2} \Rightarrow V_{GS1} = V_{GS2} \Rightarrow 8 - V_A = V_A \Rightarrow V_A = 4 \text{ V}$$

$$I_{D1} = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (V_{GS1} - V_t)^2 = \frac{1}{2} (5 \mu\text{A}/\text{V}^2) (4\text{V} - 2\text{V})^2 = 20 \mu\text{A}$$

Q_3 and Q_2 identical, and $V_{GS3} = V_{GS2}$, so

$$I_{D3} = I_{D2} = I_{D1} = 20 \mu\text{A}$$

$$I_{D3} = \frac{8\text{V} - V_o}{R} \Rightarrow R = \frac{8\text{V} - V_o}{I_{D3}} = \frac{8\text{V} - 6\text{V}}{20 \mu\text{A}} = 100 \text{ k}\Omega$$