

## EE 321 - Exam 3


November 15, 2002

Name: \_\_\_\_\_


Closed book. One page of notes and a calculator are allowed. Show all work. Partial credit will be given. No credit will be given if an answer appears with no supporting work.

For all the circuits below, assume the capacitors are large so they block DC and pass all signals of interest.

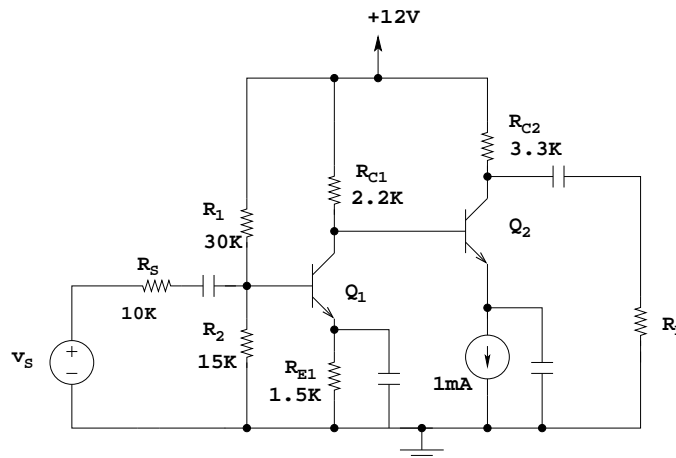1. In the circuit below, both transistors have  $\beta = 100$ .
  - (a) Find the bias voltages  $V_{B1}$ ,  $V_{C1}$ ,  $V_{E1}$ ,  $V_{C2}$  and  $V_{E2}$ .
  - (b) Find the bias collector currents  $I_{C1}$  and  $I_{C2}$ .
  - (c) Find the small-circuit parameters for  $Q_2$ :  $r_\pi$ ,  $r_e$  and  $g_m$ .



1. (a) DC - Capacitors are open circuits

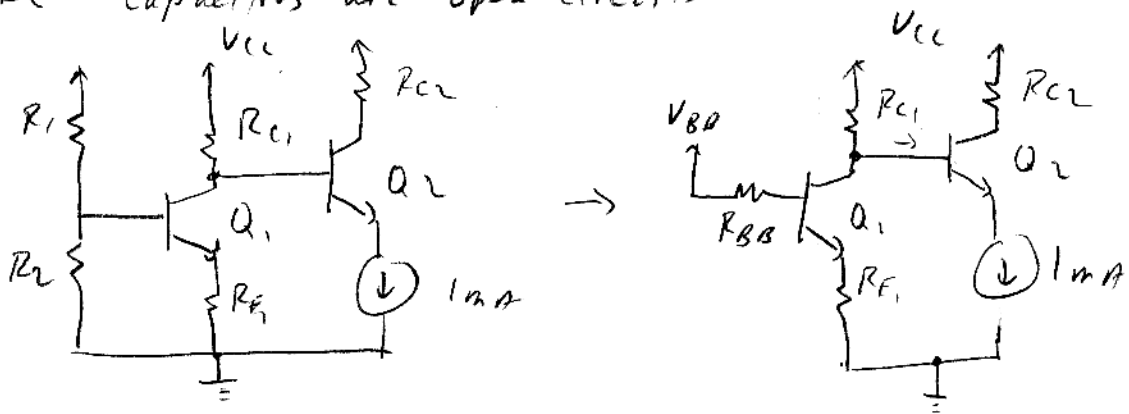

$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{15k}{15k + 30k} 12V = 4V$$

$$R_{BB} = R_1 \parallel R_2 = \frac{(15k)(30k)}{(15k + 30k)} = 10k$$

KVL through  $Q_1$ :  $V_{BB} = I_{B1} R_{BB} + V_{BE1} + (\beta + 1) I_{B1} R_{E1}$

$$I_{B1} = \frac{V_{BB} - V_{BE1}}{R_{BB} + (\beta + 1) R_{E1}} = \frac{4V - 0.7V}{10k + (101)(1.5k)} = 0.020 \text{ mA}$$

$$I_{E1} = (\beta + 1) I_{B1} = 2.1 \text{ mA}$$

$$I_{C1} = \beta I_{B1} = 2.0 \text{ mA}$$

$$V_{E1} = I_{E1} R_{E1} = 3.1 \text{ V}$$

$$V_{B1} = V_{E1} + V_{BE1} = 3.1V + 0.7V = 3.8 \text{ V}$$

$$V_{C1} = V_{CC} - R_{C1}(I_{C1} - I_{B2}) \quad \text{Don't know } I_{B2} \text{ yet}$$

$$I_{E2} = 1 \text{ mA}$$

$$I_{B2} = I_{E2} / (\beta + 1) = 0.0099 \text{ mA}$$

$$I_{C2} = \beta I_{B2} = 0.99 \text{ mA}$$

$$V_{C1} = V_{CC} - R_{C1}(I_{C1} - I_{B2}) = 7.5 \text{ V}$$

$$V_{B2} = V_{C1} = 7.5 \text{ V}$$

$$V_{E2} = V_{B2} - V_{BE2} = 7.5V - 0.7V = 6.7 \text{ V}$$

$$V_{C2} = V_{CC} - I_{C2} R_{C2} = 8.7 \text{ V}$$

$V_{B1} = 3.8 \text{ V}$
$V_{C1} = 7.5 \text{ V}$
$V_{E1} = 3.1 \text{ V}$
$V_{B2} = 7.5 \text{ V}$
$V_{C2} = 8.7 \text{ V}$
$V_{E2} = 6.7 \text{ V}$
$V_{CE1} = 4.4 \text{ V}$ Active
$V_{CE2} = 2.0 \text{ V}$ Active

(b) From (a)  $I_{C1} = 2.0 \text{ mA}$

$$I_{C2} = 0.99 \text{ mA}$$


$$r_{\pi 2} = \frac{V_T}{I_{B2}} = \frac{25 \text{ mV}}{0.0099 \text{ mA}} = 2.5 \text{ k}\Omega$$

$$r_{e2} = \frac{V_T}{I_{E2}} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$


$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{0.99 \text{ mA}}{25 \text{ mV}} = 40 \text{ mA/V}$$

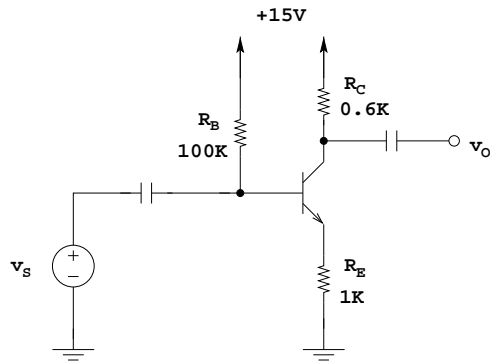2. The BJT in the circuit below has  $\beta = 100$ . You may ignore  $r_o$  for this problem.

- Find a value for  $r_e$ .
- Draw the small-circuit equivalent model.
- Calculate the voltage gain of the circuit.
- Find the input resistance of the circuit.



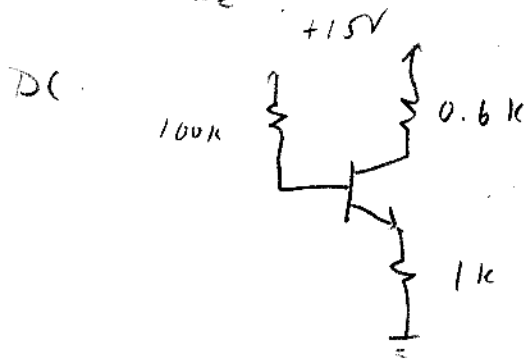2. (a)  $r_e = \frac{V_T}{I_E}$ , so need  $I_E$



$$V_{CC} = I_B R_B + V_{BE} + (\beta + 1) I_B R_E$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} = \frac{15V - 0.7V}{100k + (101)(1k)} = 0.071 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 7.2 \text{ mA}$$

$$V_E = I_E R_E = 7.2 \text{ V}$$


$$I_C = \beta I_B = 7.1 \text{ mA}$$

$$V_C = V_{CC} - I_C R_C = 10.7 \text{ V}$$

$$V_{CE} = V_C - V_E = 3.5 \text{ V}, \text{ so } Q \text{ is active}$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{7.2 \text{ mA}} = 3.5 \Omega$$

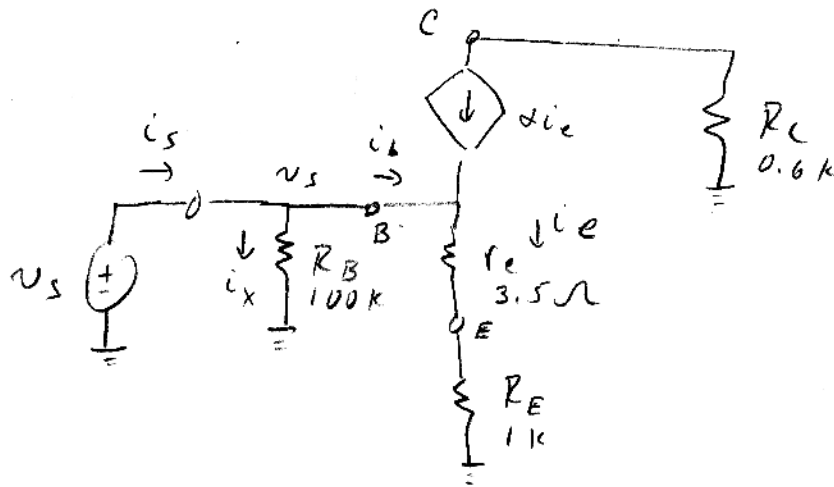(b) Small signal - use T model (because we have  $R_E$ )



$$(c) v_o = -\beta i_e R_C$$

$$i_e = \frac{v_s}{r_e + R_E}$$

$$v_o = \frac{-\beta R_C}{r_e + R_E} v_s$$

$$\frac{v_o}{v_s} = \frac{-\beta R_C}{r_e + R_E} = 0.59 \text{ V/V}$$

$$(d) R_i = \frac{v_s}{i_s}$$


$$i_s = i_x + i_b \quad i_x = \frac{v_s}{R_B} \quad i_b = \frac{i_e}{\beta + 1} = \frac{v_s}{(\beta + 1)(r_e + R_E)}$$

$$i_s = i_x + i_b = \frac{v_s}{R_B} + \frac{v_s}{(\beta + 1)(r_e + R_E)}$$


$$R_i = \frac{v_s}{i_s} = \frac{v_s}{\frac{v_s}{R_B} + \frac{v_s}{(\beta + 1)(r_e + R_E)}} = \frac{1}{\frac{1}{R_B} + \frac{1}{(\beta + 1)(r_e + R_E)}}$$

$$R_i = R_B \parallel (\beta + 1)(r_e + R_E) = 100k \parallel (101)(1.035k) = 51k$$

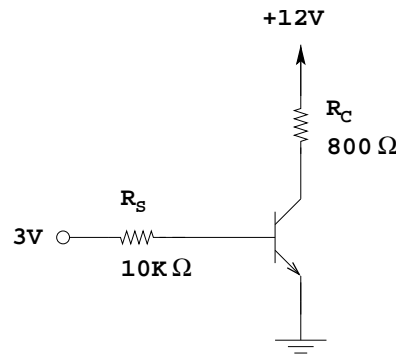- (e) Find the value of  $\beta$  needed for the BJT in the circuit below such that the BJT is just on the edge of saturation – i.e.,  $I_B = I_{B_{EOS}}$ .



3.

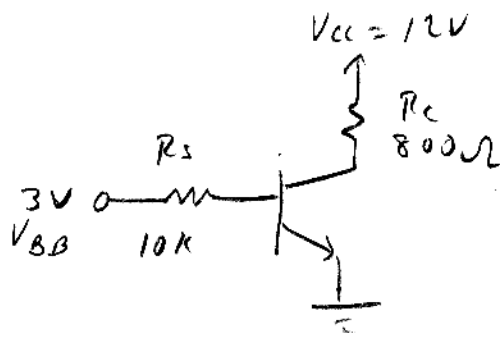

$$I_{C_{sat}} = \frac{V_{CC} - V_{CE_{sat}}}{R_C} = \frac{12V - 0.2V}{0.8k} = 15mA$$

$$V_{BB} = I_B R_S + V_{BE} \Rightarrow I_B = \frac{V_{BB} - V_{BE}}{R_S} = \frac{3V - 0.7V}{10k} = 0.23mA$$

$$I_{B_{EoS}} = \frac{I_{C_{sat}}}{\beta} \Rightarrow \beta = \frac{I_{C_{sat}}}{I_{B_{EoS}}} = \frac{15mA}{0.23mA} = 64$$

$\beta = 64 \Rightarrow Q$  just saturated