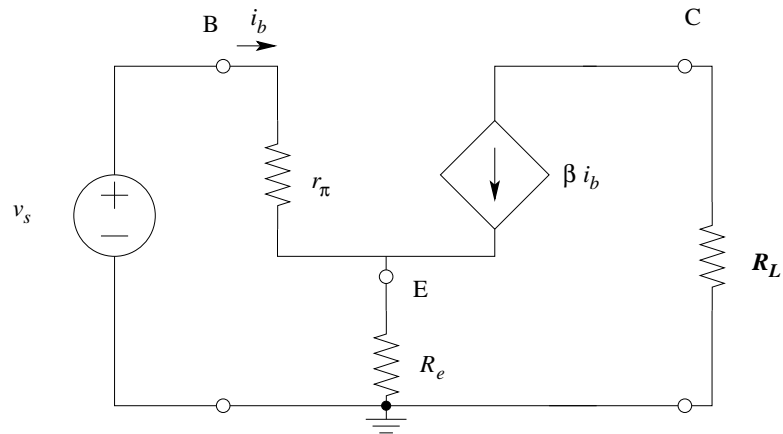


EE321 – Fall 2002

Homework 1

Due August 30, 2002

1. Consider the circuit below:



- (a) Find the voltage gain, v_C/v_B . v_B is the voltage at node B, v_C is the voltage at node C. The answers should be in terms of the circuit elements r_π , R_e , β and R_L .

- (b) Find the input resistance between terminals B and G.