

EE 321
Fall 2002

Homework #1


Solutions

EE321 - Fall 2002

Homework 1

Due August 30, 2002

1. Consider the circuit below:

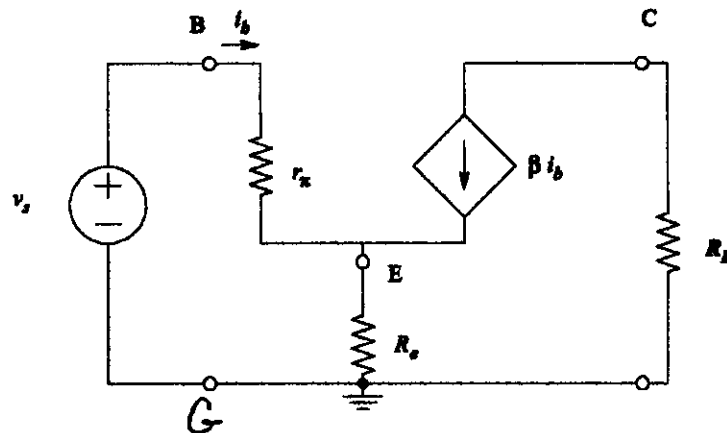

- (a) Find the voltage gain, v_C/v_B . v_B is the voltage at node B, v_C is the voltage at node C. The answers should be in terms of the circuit elements r_π , R_e , β and R_L .

$$v_C = -\beta i_b R_L \quad i_e = i_b + \beta i_b \quad v_B = i_b r_\pi + R_e i_e$$

$$v_B = i_b r_\pi + (\beta i_b + i_b) R_e \Rightarrow i_b = \frac{v_B}{r_\pi + (\beta + 1) R_e}$$

$$v_C = \frac{-\beta v_B R_L}{r_\pi + (\beta + 1) R_e} \quad \frac{v_C}{v_B} = \frac{-\beta R_L}{r_\pi + (\beta + 1) R_e}$$

- (b) Find the input resistance between terminals B and G.

$$R_{in} = \frac{v_B}{i_b} \quad \text{From (a)} \quad i_b = \frac{v_B}{r_\pi + (\beta + 1) R_e}$$

$$\therefore R_{in} = r_\pi + (\beta + 1) R_e$$