

EE 321
Fall 2002

Homework #3

Solutions

2.8 (a) Standard inverting op-amp circuit

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} = -\frac{100k}{10k} = -10$$

$$R_{in} = R_1 = 10k\Omega$$

(b) The extra $10k\Omega$ resistor on the output has no effect on V_o - op amp will adjust V_o until $V_- = V_+$

$$\frac{V_o}{V_i} = -10 \quad R_{in} = 10k\Omega$$

(c) Extra $10k\Omega$ from V_- to ground has no effect - V_- is a virtual ground so no current flows through extra resistor

$$\frac{V_o}{V_i} = -10 \quad R_{in} = -10k\Omega$$

(d) Extra $10k\Omega$ from V_+ to ground has no effect - No current flows into + input, so no voltage drop across resistor, so $V_+ = 0$ as before.

$$\frac{V_o}{V_i} = -10 \quad R_{in} = 10k\Omega$$

(e) $V_- = V_+ = 0$. No connected directly to V_- , so $V_o \approx 0$

$$\frac{V_o}{V_i} = 0 \quad R_{in} = 10k\Omega$$


(f) $V_- = V_i \quad V_o = A(V_+ - V_-) = -AV_- = -AV_i$

For ideal op amp, $A \approx \infty$, so $V_o = -\infty V_i$

$$\frac{V_o}{V_i} = -\infty \quad R_{in} = 0$$

2.16

(a)

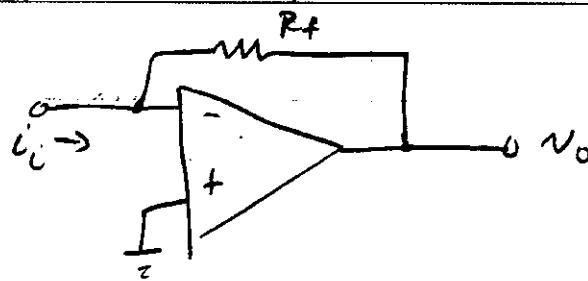

i_i goes through R_f and $V_- = V_+ = 0$, so


$$i_i = \frac{V_- - V_o}{R_f} = \frac{-V_o}{R_f} \Rightarrow V_o = -R_f i_i$$

For a transresistance amplifier (Table 1.11)

$$R_m = \frac{V_o}{i_i} = \frac{-R_f i_i}{i_i} = -R_f$$

$$R_{in} = \frac{V_i}{i_i} \quad V_i = V_- = 0, \text{ so } R_{in} = \frac{0}{i_i} = 0$$

(b)

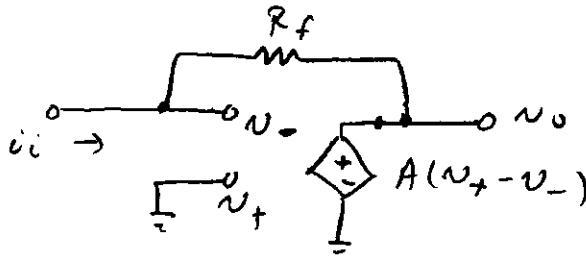

$$V_o = A(V_+ - V_-) = -A V_- \Rightarrow V_- = -V_o/A$$

$$i_i = \frac{V_- - V_o}{R_f} = \frac{-V_o/A - V_o}{R_f} = \frac{-(1+A)V_o}{A R_f}$$



$$V_o = \frac{-A R_f}{1+A} i_i$$

$$R_m = \frac{V_o}{i_i} = \frac{-R_f}{(1+A)}$$

$$V_- = -V_o/A = \frac{-R_f}{1+A} i_i$$

$$R_{in} = \frac{V_i}{i_i} = \frac{V_-}{i_i} = \frac{R_f}{1+A}$$

2.17

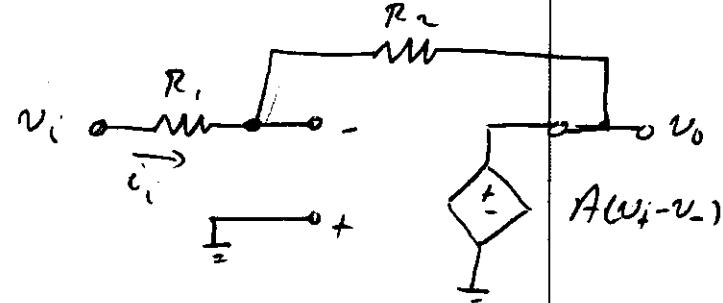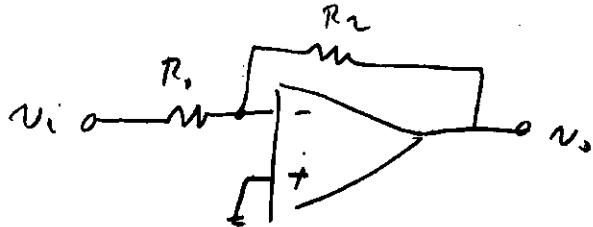

$$\textcircled{1} \quad v_o = A(v_+ - v_-) = -Av_- \quad (\text{because } v_+ = 0)$$

$$\textcircled{2} \quad i_i = \frac{v_i - v_-}{R_1} = \frac{v_- - v_o}{R_2} \Rightarrow v_- = \frac{v_o R_1 + v_i R_2}{R_1 + R_2}$$

$$v_o = -Av_- = -A \cdot \frac{v_o R_1 + v_i R_2}{R_1 + R_2}$$

Solve for v_o :


$$\textcircled{4} \quad v_o = \frac{-Av_i R_2}{R_1(1+A) + R_2}$$

Note that $i_i = \frac{v_i - v_o}{R_1 + R_2}$

$$\therefore i_i = \frac{v_i - \left(\frac{-Av_i R_2}{R_1(1+A) + R_2} \right)}{R_1 + R_2} = \frac{v_i(1+A)}{R_1(1+A) + R_2}$$

$$v_i = i_i \left[\frac{R_1(1+A) + R_2}{1+A} \right] \boxed{R_{in} = \frac{v_i}{i_i} = \frac{R_1(1+A) + R_2}{1+A}}$$

2.22

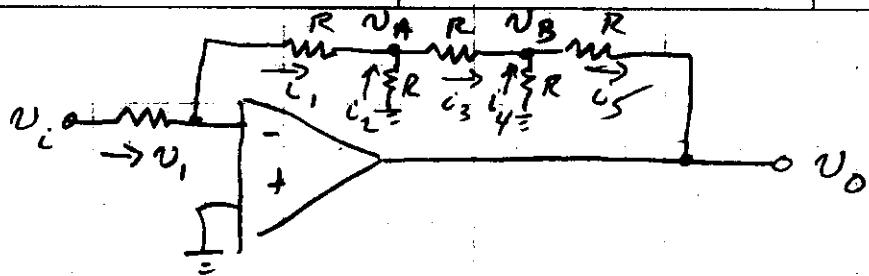

$$v_- = v_+ = 0 \Rightarrow i_1 = \frac{v_i}{R}$$

$$i_1 = \frac{v_- - v_A}{R} = \frac{-v_A}{R} \Rightarrow v_A = -v_i$$

$$i_2 = \frac{0 - v_A}{R} = \frac{v_i}{R} = i_1 = \frac{v_i}{R}$$

$$i_3 = i_1 + i_2 = 2i_1 = \frac{2v_i}{R}$$

$$i_3 = \frac{v_A - v_B}{R} \Rightarrow \frac{2v_i}{R} = v_A - v_B \Rightarrow 2v_i = v_B - v_A \Rightarrow 2v_i = 2v_i - 2i_1 R \Rightarrow 2i_1 R = -3v_i$$

$$i_4 = \frac{0 - v_B}{R} = \frac{3v_i}{R} = 3i_1 = \frac{3v_i}{R}$$


$$i_5 = i_3 + i_4 = 5i_1 = \frac{5v_i}{R}$$

$$i_5 = \frac{v_B - v_o}{R} = \frac{-3v_i - v_o}{R} = \frac{5v_i}{R}$$

$$-3v_i - v_o = 5v_i \Rightarrow v_o = -8v_i$$

$$\boxed{\frac{v_o}{v_i} = -8}$$

2.31

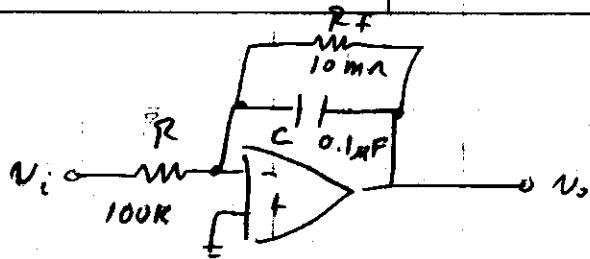

$$T(s) = -\frac{Z_2}{Z_1} \quad Z_2 = R_f // C = \frac{R_f \frac{1}{Cs}}{R_f + \frac{1}{Cs}} = \frac{R_f}{1 + R_f Cs}$$

$$Z_1 = R$$

$$\textcircled{1} \quad T(s) = -\frac{R_f/R}{1 + R_f Cs} = -\frac{10M/100k}{1 + (10M\Omega)(0.1\mu F)s} = \frac{-100}{1 + s}$$

For ideal integrator, $R_f = \infty$ so $T_{\text{ideal}}(s) = -\frac{1}{Rcs}$

$$\textcircled{2} \quad T_{\text{ideal}}(s) = -\frac{1}{Rcs} = \frac{-1}{(100k\Omega)(0.1\mu F)s} = \frac{-100}{s}$$

Bode plot for \textcircled{1}: DC gain = 100 = 40 dB

$$\omega_s = 1 \quad f_s = \frac{\omega_s}{2\pi} = 0.16 \text{ Hz}$$


$$\text{Bode plot for } \textcircled{2} \quad -T_{\text{ideal}}(\omega) = -\frac{100}{j\omega} \quad |T_{\text{ideal}}(\omega)| = \frac{100}{\omega}$$

$$|T_{\text{ideal}}(\omega)| = 20 \log_{10}(100) = 20 \log_{10}(\omega)$$

$$= 40 - 20 \log_{10}(\omega)$$

straight line; slope = -20 dB/decade

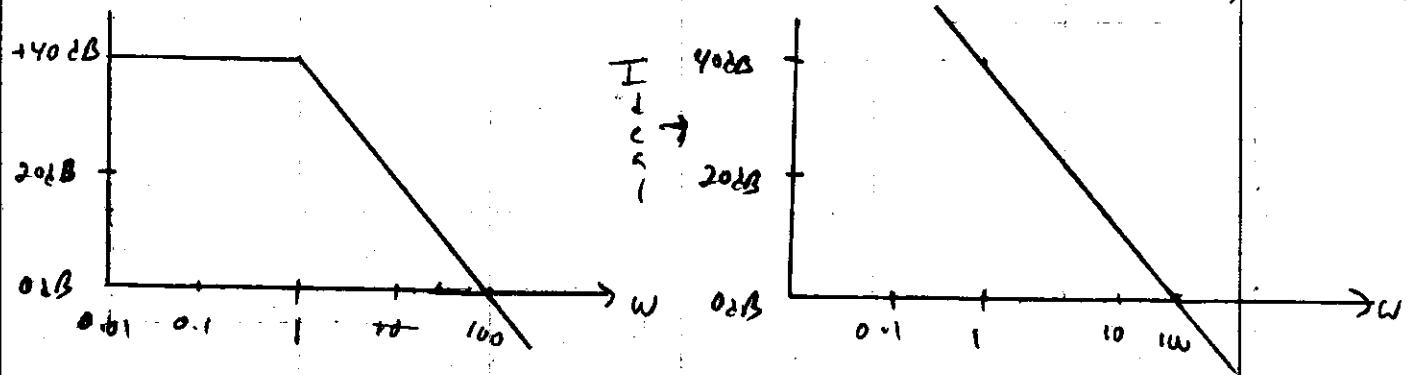Passes through 40 dB when $\omega = 1$, $f = 0.16 \text{ Hz}$



$$f > 0.16 \text{ Hz}$$

Circuit acts as amplifier for $\omega < \omega_0$ $WL < 1 \text{ rad/s}$


$$f < 0.16 \text{ Hz}$$

(b) High freq \Rightarrow short duration.

For short-duration pulses ($t < \frac{1}{\omega} = 1 \text{ sec}$) circuit acts as integrator

For single-time constant circuits
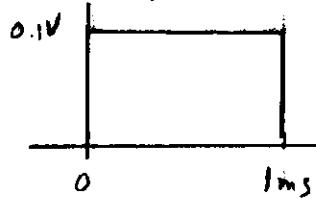
$$v_o(t) = v_o(\infty) - [v_o(\infty) - v_o(0^+)] e^{-t/\tau} \quad (\text{eqn A.9})$$



For $v_i = 0.1 \text{ V}$, $v_o = 100v_i = -10 \text{ V}$ if v_i left for a long time

$$\text{For } t < 0, v_o = 0$$

$$\text{For } 0 < t < 1 \text{ ms}, v_o(t) = -10 - [-10 - 0] e^{-t/\tau}$$



$$v_o(t) = -10 (1 - e^{-t/10})$$

Because $t \ll \tau = k\alpha$, $e^{-t/\tau} \approx 1 - t/\tau$ and $v_o(t) \approx -10 t/\tau = -10t$

$$\text{At } t_0 = 1 \text{ ms}, v_o(t_0) = -10(0.001) \text{ V} = -0.01 \text{ V}$$

$$\text{For } t > 1 \text{ ms}, v_o(t) \approx 0 - [0 - (-0.01)] e^{-t/10}$$

$$= -0.01 e^{-t} \text{ V}$$

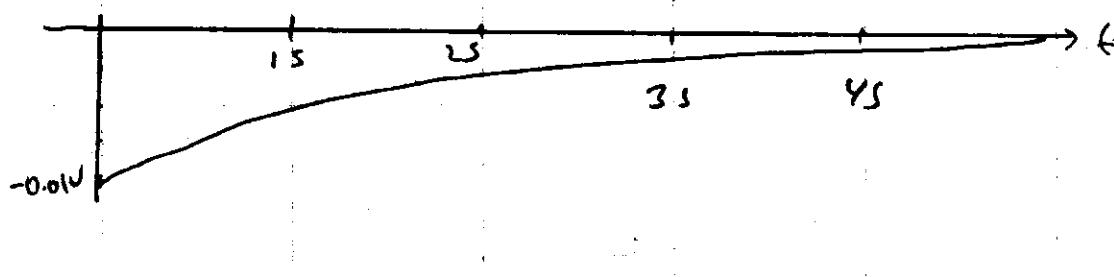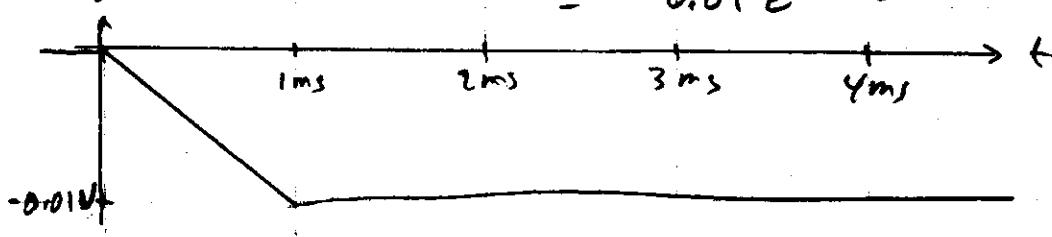

```
% Define component values
R = 100e3; C = 0.1e-6; Rf = 10e6;

% Find w0 and tau
tau = Rf*C; w0 = 1/tau;

% Create vector of frequencies
w = logspace(-2,3,1000);
s = j*w;


% Find T(w) = (-Rf/R)/(1+Rf C s)
T = (-Rf/R)./(1+Rf*C*s);
T_dB = 20*log10(abs(T));

% Find ideal integrator response, Tid = -1/RCs
Tid = -1./(R*C*s);
Tid_dB = 20*log10(abs(Tid));



figure(1)
semilogx(w,Tid_dB,'r')
hold on
semilogx(w,T_dB)
grid
xlabel('omega (rad/sec)');
ylabel('|T(omega)| (dB)');
title('Bode plot for Problem 2.31');
legend('Ideal Integrator','Actual Circuit')

% Plot time response
t = -1:(1/10000):5;
t0 = 0.001; % time pulse is turned off
v = zeros(size(t)); % Vector of all zeros same size as t
ii = find((t>0) & (t<t0)); % Time pulse is on
v(ii) = -10*(1-exp(-t(ii)/tau));
ii = find(t>t0); % Time pulse is off
v(ii) = -0.01*exp(-(t(ii)-t0)/tau);
figure(2)
subplot(211)
plot(t*1000,v) % Plot in milliseconds
axis([-t0*1000 5*t0*1000 -0.012 0.012])
grid
xlabel('t (ms)');
ylabel('v (volts)');
title('Pulse response of Problem 2.31')


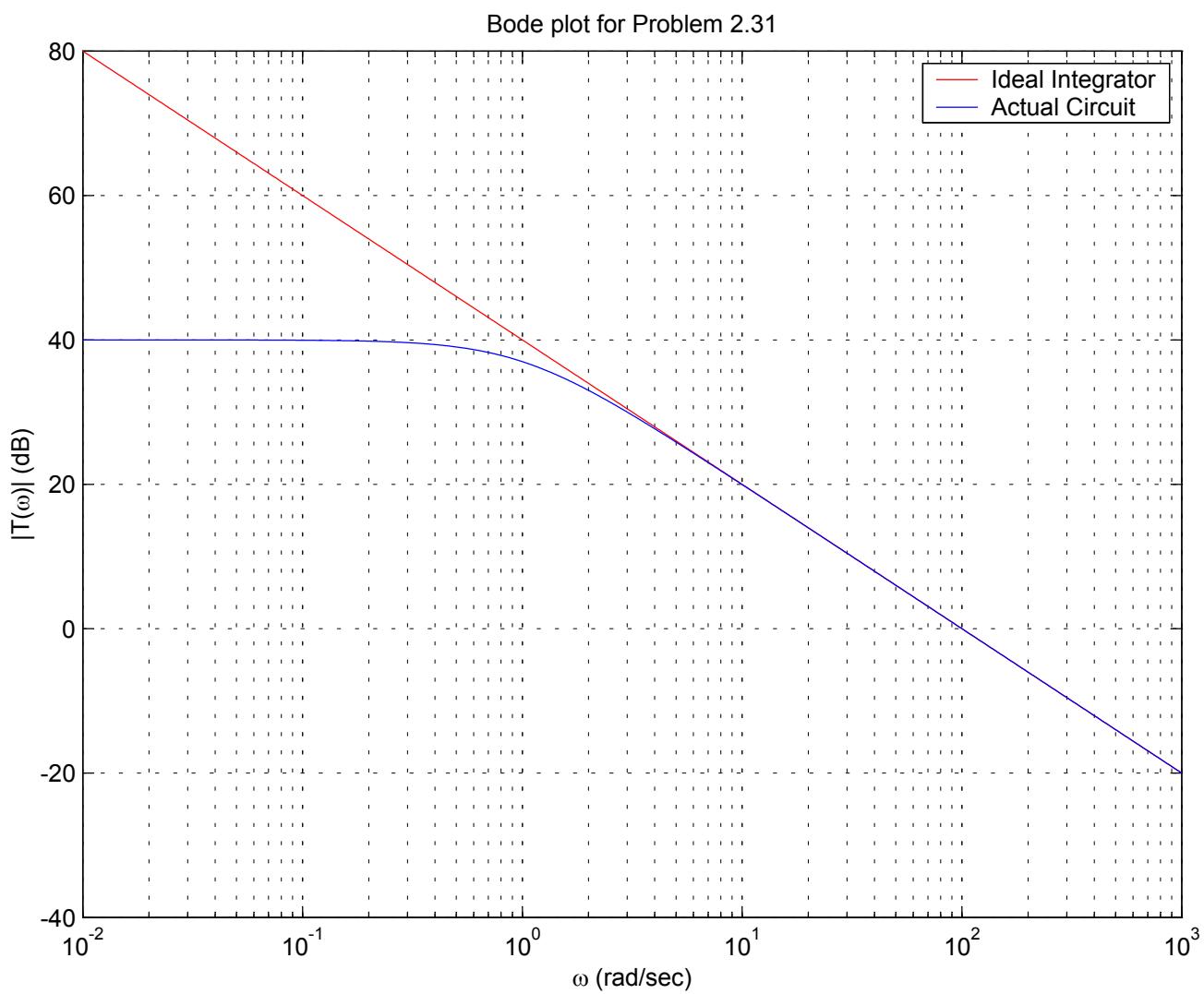
subplot(212)
plot(t,v)
axis([-1 5 -0.012 0.012])
grid
xlabel('t (sec)');
ylabel('v (volts)');
```



Pulse response of Problem 2.31

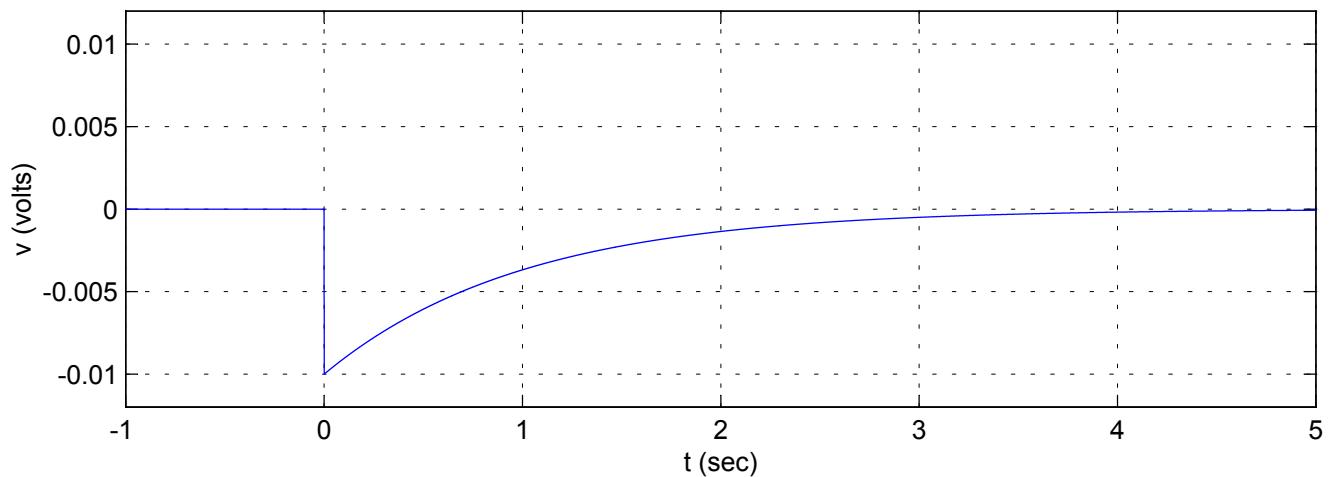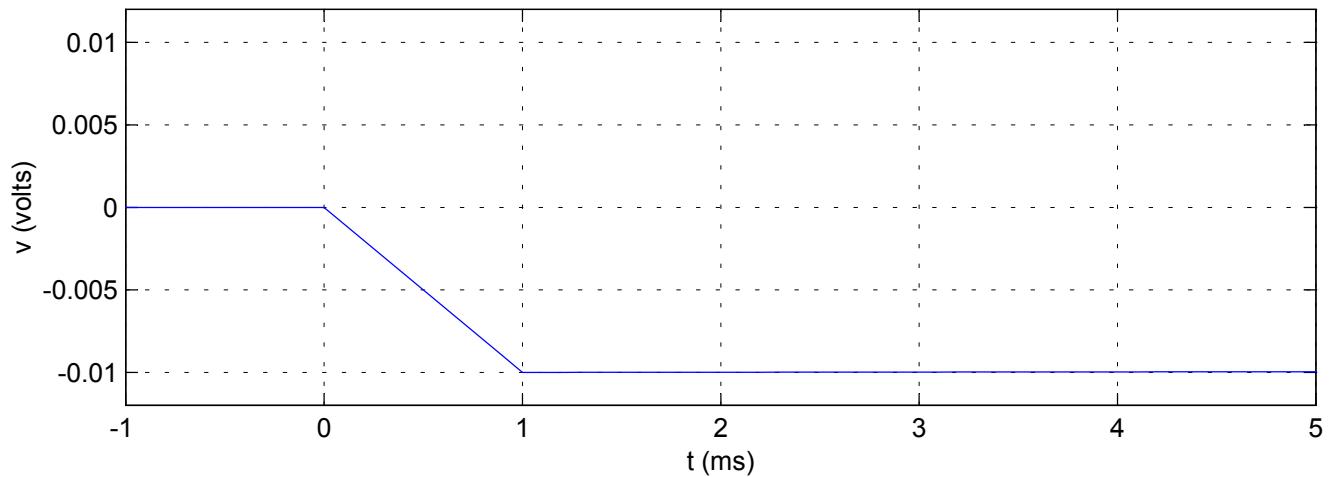

2.50

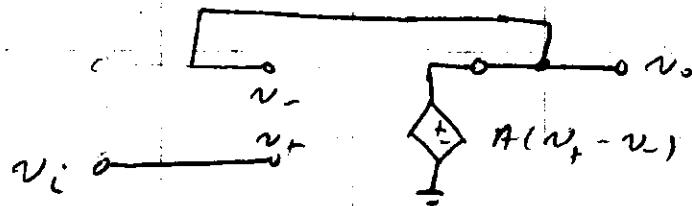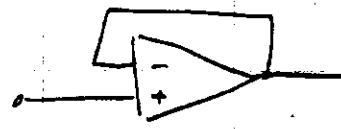


$$V_o = A(V_+ - V_-) \quad V_+ = V_i \quad V_- = V_o$$

$$\therefore V_o = A(V_i + V_o) \Rightarrow V_o = V_i \left(\frac{A}{1+A} \right)$$

$$\frac{V_o}{V_i} = \frac{A}{1+A}$$

A	V_o/V_i	$(1 - \frac{V_o}{V_i}) \times 100\%$
1000	0.999	0.1%
100	0.99	1%
10	0.91	9.1%

2.61

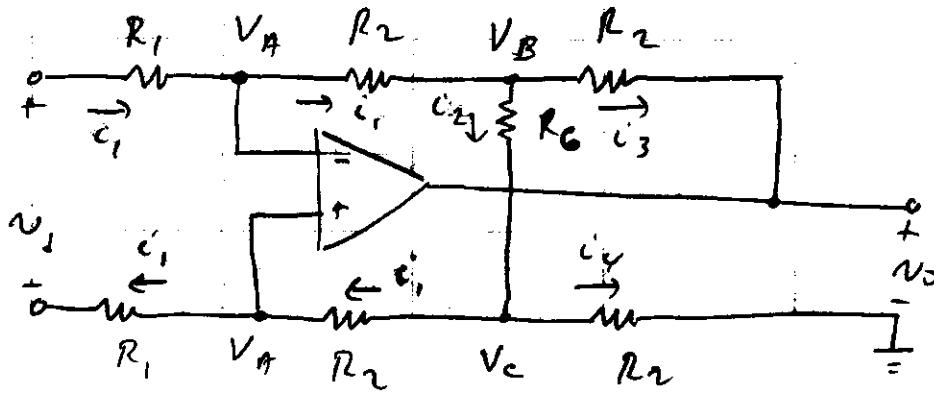

$$v_+ = v_- \Rightarrow i_1 = \frac{v_d}{2R_1}$$

$$i_1 = \frac{V_A - V_B}{R_2} = \frac{v_d}{2R_1} \Rightarrow V_B = \frac{2V_A R_1 - v_d R_2}{2R_1}$$

$$i_1 = \frac{V_C - V_A}{R_2} = \frac{v_d}{2R_1} \Rightarrow V_C = \frac{2V_A R_1 + v_d R_2}{2R_1}$$

$$i_2 = \frac{V_B - V_C}{R_G} = -v_d \frac{R_G}{R_1 R_C}$$

$$i_1 = i_2 + i_3 \Rightarrow -i_3 = i_1 - i_2 = \frac{v_d}{2R_1} + \frac{v_d R_2}{R_1 R_G}$$

$$i_3 = \frac{R_G + 2R_2}{2R_1 R_G} v_d$$

$$i_2 = i_1 + i_4 \Rightarrow i_4 = i_2 - i_1 = -i_3 = -\frac{R_G + 2R_2}{2R_1 R_G} v_d$$

$$v_o = -i_3 R_2 + i_2 R_G + i_4 R_2$$

$$= -\left(\frac{R_G + 2R_2}{2R_1 R_G}\right) v_d R_2 + \left(-\frac{R_2 v_d}{R_1 R_G}\right) R_G - \left(\frac{R_G + 2R_2}{2R_1 R_G}\right) v_d R_2$$

$$= -\frac{2R_2 R_2 - 2R_G R_2}{R_1 R_G} v_d = -2 \frac{R_2}{R_1} \left[1 + \frac{R_2}{R_G}\right] v_d$$

$$\frac{v_o}{v_d} = -2 \frac{R_2}{R_1} \left[1 + \frac{R_2}{R_G}\right]$$