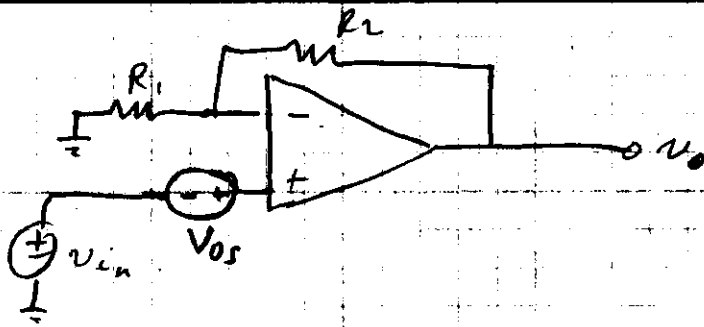


EE 321
Fall 2002

Homework #4

Solutions


2.87



$$v_o = \left(1 + \frac{R_2}{R_1}\right) (V_{os} + v_{in}) = 1000(4\text{mV} + V_i \sin \omega t)$$

$$v_{o\text{max}} = 1000(4\text{mV} + V_i) = 12\text{V}$$

$$V_i = 8\text{mV}$$

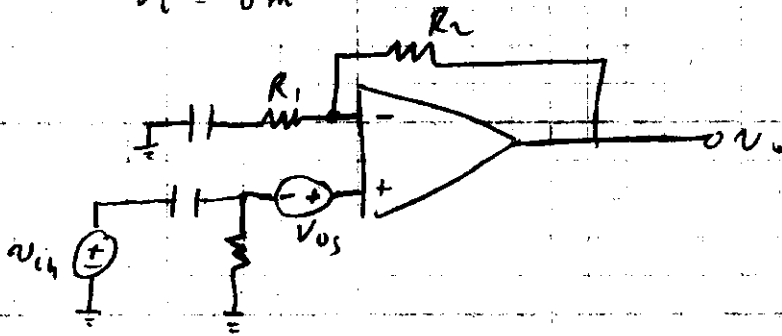

Use superposition

With $v_{in} = 0$, $v_+ = V_{os}$ so $v_- = v_+ = V_{os}$

No current flows through R_1 , so no current flows through R_2 , and $v_o = v_- = V_{os} = 4\text{mV}$


With V_{os} off and v_{in} on, capacitors act like shorts at AC, so $v_o = 1000 v_{in} = 1000 V_i \sin \omega t$

Add the two: $v_o = 4\text{mV} + 1000 V_i \sin \omega t$

$$v_{o\text{max}} = 4\text{mV} + 1000 V_i = 12\text{V}$$

$$V_i = \frac{12\text{V} - 4\text{mV}}{1000} \approx \frac{12\text{V}}{1000} = 12\text{mV}$$

2.91

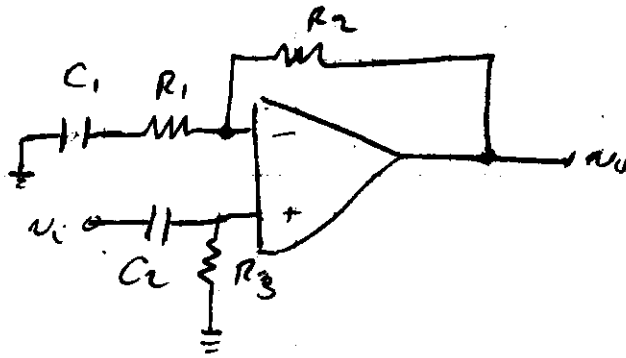

$$\frac{v_o}{v_i} = \left(1 + \frac{R_2}{R_1}\right)$$

Let $R_2 = 99 \text{ k}\Omega$, $R_1 = 1 \text{ k}\Omega$

Want $R_3 = R_2 = 99 \text{ k}\Omega$ (Want $R_3 = R_2 \parallel (R_1 + \frac{1}{C_2})$ at DC. At DC, $\frac{1}{C_2} = \infty$, so $R_3 = R_2$)

v_o sees R_1 , R_2 and C_1 in series, so $\omega_1 = \frac{1}{(R_1 + R_2)C_1}$

$$f_1 = \frac{1}{2\pi(R_1 + R_2)C_1} \quad C_1 = \frac{1}{2\pi(R_1 + R_2)f_1}$$


For $f_1 = 100 \text{ Hz}$, $C_1 = 16 \text{ nF}$

v_i sees C_2 and R_3 in series, so $f_2 = \frac{1}{2\pi R_3 C_2}$

$$C_2 = \frac{1}{2\pi R_3 f_2}$$

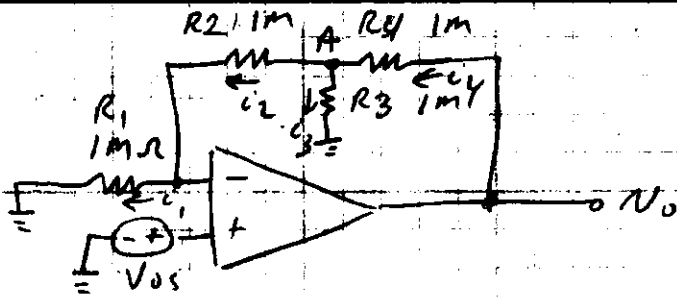For $f_2 = 10 \text{ Hz}$, $C_2 = 0.16 \mu\text{F}$





$$v_- = v_+ = V_{os} \quad i_1 = \frac{V_{os}}{R_1} \quad i_2 = i_1 = \frac{V_{os}}{R_1}$$

$$i_2 = \frac{V_A - v_-}{R_2} \Rightarrow V_A = i_2 R_2 + v_- = \frac{V_{os} R_2}{R_1} + V_{os}$$

$$i_3 = \frac{V_A}{R_3} = \frac{V_{os} R_2}{R_1 R_3} + \frac{V_{os}}{R_3}$$

$$i_4 = i_2 + i_3 = \frac{V_{os}}{R_1} + \frac{V_{os} R_2}{R_1 R_3} + \frac{V_{os}}{R_3}$$


$$i_4 = \frac{v_o - V_A}{R_4} \Rightarrow v_o = i_4 R_4 + V_A$$

$$v_o = \frac{V_{os} R_4}{R_1} + \frac{V_{os} R_2 R_4}{R_1 R_3} + \frac{V_{os} R_4}{R_3} + \frac{V_{os} R_2}{R_1} + V_{os}$$

$$\approx 2003 V_{os}$$

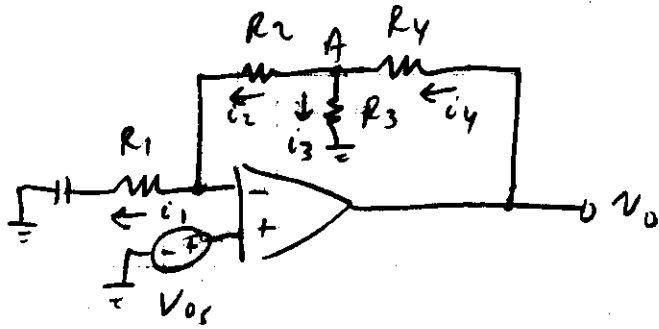For $V_{os} = \pm 5 \text{ mV}$, $v_o = \pm 10 \text{ V}$





$$v_+ = v_- = V_{05} \quad i_1 = 0 \quad i_2 = i_1 = 0$$

$$i_2 = \frac{V_A - v_-}{R_2} \Rightarrow V_A = i_2 R_2 + v_- = V_{05}$$

$$i_3 = \frac{V_A}{R_3} = \frac{V_{05}}{R_3}$$


$$i_4 = i_2 + i_3 = \frac{V_{05}}{R_3}$$

$$i_4 = \frac{v_0 - V_A}{R_4} \Rightarrow v_0 = i_4 R_4 + V_A$$

$$v_0 = \frac{V_{05} R_4}{R_3} + V_{05} = 1001 V_{05}$$

For $V_{05} = \pm 5 \text{ mV}$,

$$v_0 = \pm 5 \text{ V}$$

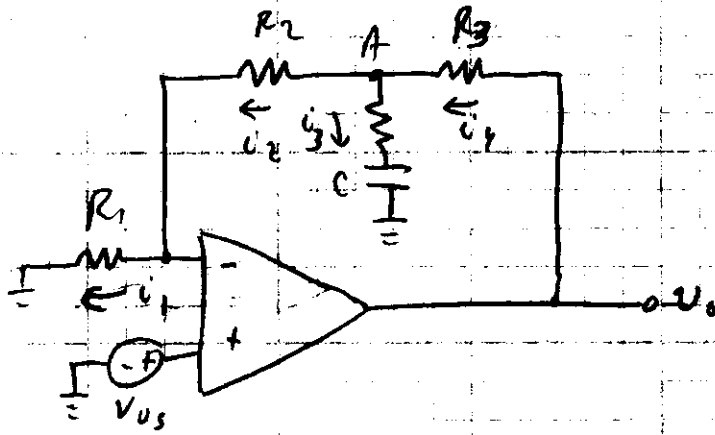

$$v_+ = v_- = v_{05} \quad i_1 = \frac{v_{05}}{R_1} \quad i_2 = i_1 = \frac{v_{05}}{R_1}$$

$$i_2 = \frac{v_A - v_-}{R_2} \Rightarrow v_A = i_2 R_2 + v_- = \frac{v_{05} R_2}{R_1} + v_{05}$$

$$i_3 = 0 \quad i_4 = i_2 + i_3 = \frac{v_{05}}{R_1}$$

$$i_4 = \frac{v_0 - v_A}{R_4} \Rightarrow v_0 = i_4 R_4 + v_A$$


$$v_0 = \frac{v_{05} R_4}{R_1} + \frac{v_{05} R_2}{R_1} + v_{05}$$

$$v_0 = 3 v_{05}$$

Für $v_{05} = \pm 5 \text{ mV}$,

$$v_0 = \pm 15 \text{ mV}$$

2.95

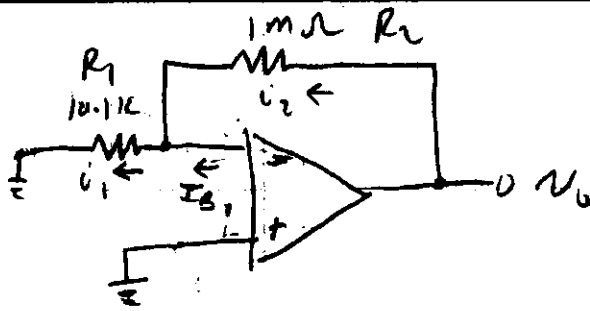

(a) $V_- = V_+ = 0 \Rightarrow i_1 = 0$

$i_1 = i_2 + i_{B1} \Rightarrow i_2 = -i_{B1}$ $V_0 = i_2 R_2 = -i_{B1} R_2$

$V_0 = \pm 0.10V$

Due to input bias current, $i_{B1} = \pm 100nA$

(b) $V_- = V_+ = V_{os}$ $i_1 = \frac{V_-}{R_1} = \frac{V_{os}}{R_1}$

$V_0 = i_1 (R_1 + R_2) = V_{os} \left(1 + \frac{R_1}{R_2}\right) = 100 V_{os} = \pm 0.10V$

Largest V_0 will be sum of absolute values of above.

$V_0 = 0.2V$

(c) $R_3 = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = 10k\Omega$

Assume $I_{B1} = 100nA$ $I_{B2} = 90nA$, for $10nA$ offset current

$V_+ = I_{B2} R_3 = 0.9mV$


$V_- = V_+ = 0.9mV$

$i_1 = \frac{V_-}{R_1} = 90nA$

$i_1 = i_2 + i_{B1} \Rightarrow i_2 = i_1 - i_{B1} = -10nA$


$V_0 = i_2 R_2 + V_- = -9.1mV$

$V_0 = \pm 9mV \approx \pm 10mV$

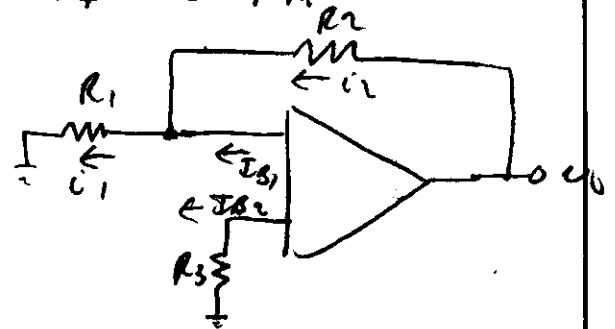

(d) Offset voltage is still 0.1V, so total is 110mV

3.9

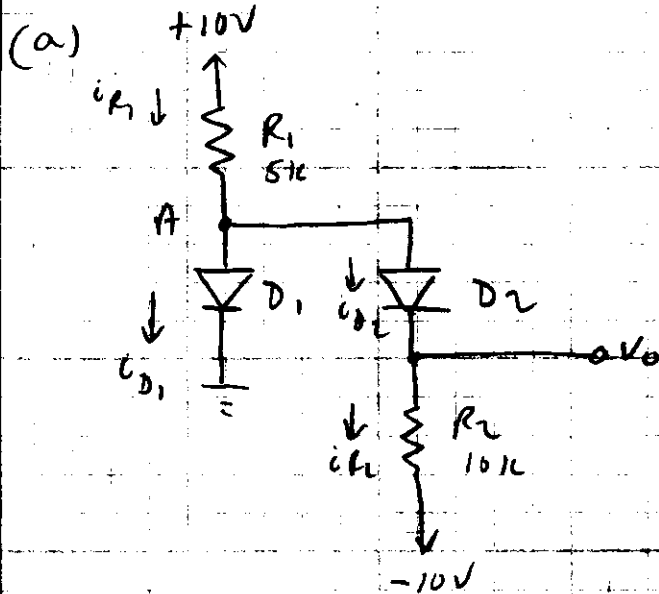

Assume D_1, D_2 both on:

$$V_A = 0, V_o = 0 \Rightarrow V_{D_1} = 0, V_{D_2} = 0$$

$$i_{R_1} = \frac{10V}{5k\Omega} = 2mA, \quad i_{R_2} = \frac{10V}{10k\Omega} = 1mA$$

$$i_{D_2} = i_{R_2} = 1mA$$

$$i_{R_1} = i_{D_1} + i_{D_2} \Rightarrow i_{D_1} = i_{R_1} - i_{D_2} = 1mA$$


$$\text{We have } V_{D_1} = 0, \quad i_{D_1} = 1mA \quad \text{OK}$$

$$V_{D_2} = 0, \quad i_{D_2} = 2mA \quad \text{OK}$$

\therefore Both diodes on,

$$V_o = 0V$$

$$I = i_{D_1} = 1mA$$

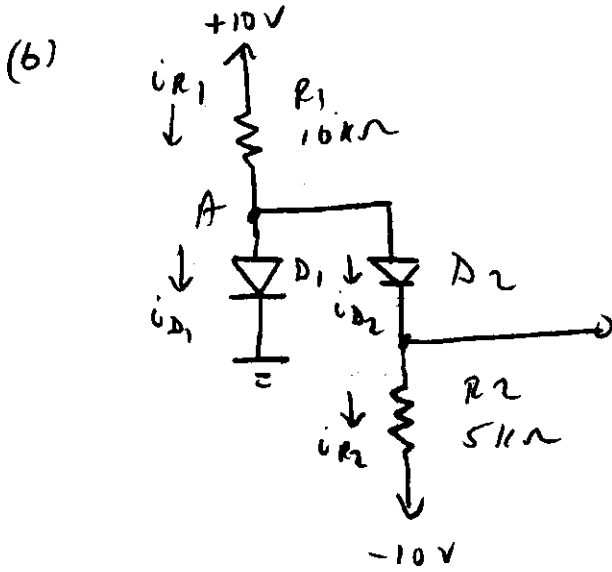

Assume both diodes on: $V_A = 0, V_0 = 0$

$$i_{R1} = \frac{10V}{10k\Omega} = 1mA \quad i_{D2} = i_{R2} = \frac{10V}{5k\Omega} = 2mA$$

$$i_{D1} = i_{R1} - i_{D2} = -1mA \leftarrow \text{Impossible}$$

Assume D_1 off, D_2 on

$$i_{D1} = 0 \Rightarrow i_{R1} = i_{D2} = i_{R2} = \frac{20V}{15k\Omega} = \frac{4}{3}mA$$

$$i_{R2} = \frac{V_0 - (-10V)}{R_2} \Rightarrow V_0 = i_{R2} R_2 - 10V = -\frac{10}{3}V$$


$$V_A = V_0 = -\frac{10}{3}V$$

$$V_{D1} = V_A = -\frac{10}{3}V \quad i_{D1} = 0 \quad \text{ok}$$

$$V_{D2} = V_A - V_0 = 0 \quad i_{D2} = \frac{4}{3}mA \quad \text{ok}$$

$$\therefore \boxed{V_0 = -\frac{10}{3}V \quad I = i_{D1} = 0}$$

3.11

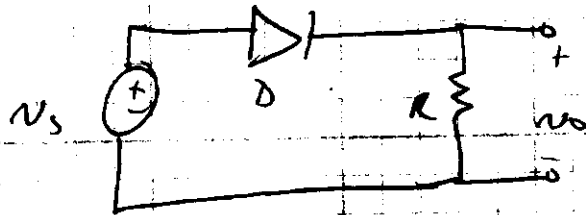

$$v_s = \sqrt{2} V_{Rms} \cos(\omega t) = 170 \cos(\omega t) \text{ V}$$

Max. i_R will be when $v_s = 170 \text{ V}$

$$R = \frac{v}{i} = \frac{170 \text{ V}}{0.1 \text{ A}} = 1.7 \text{ k}\Omega$$

When $v_s = -170 \text{ V}$, diode is off, no voltage across R ,

$$\text{so } v_o = -170 \text{ V}$$