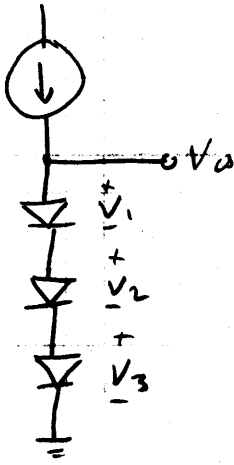


EE 321
Fall 2002

Homework #5

Solutions

3.22



$$n = 1 \quad I_s = 10^{-4} \text{ A}$$

Want $V_o = 2 \text{ V}$. Because the diodes

are identical, $V_1 = V_2 = V_3 = V_o/3$

$$I_1 = I_s e^{\left(\frac{V_1}{nV_T}\right)} = 10^{-4} e^{\left(\frac{2/3 \text{ V}}{1 \times 25 \text{ mV}}\right)}$$

$$I = 3.8 \text{ mA}$$

If 1 mA drawn away by a load,

$$I = 3.8 \text{ mA} - 1 \text{ mA} = 2.8 \text{ mA}$$

$$V = 3 \text{ mV} = 3 nV_T \ln(I/I_s) = 1.977 \text{ V}$$

$$\Delta V \approx 2.000 \text{ V} - 1.977 \text{ V} = 23.1 \text{ mV}$$

Note: I used $V_T = 25 \text{ mV}$. You will get slightly different answers if you use a different value for V_T .

3.24

$$V_1 = 0.650 \text{ V}, \quad I_1 = 0.2 \text{ mA}$$


$$V_2 = 0.750 \text{ V}, \quad I_2 = 10 \text{ mA}$$

$$\frac{I_1}{I_2} = \frac{I_s e^{V_1/nV_T}}{I_s e^{V_2/nV_T}} = e^{(V_1 - V_2)/nV_T}$$

$$\frac{V_1 - V_2}{nV_T} = \ln \frac{I_1}{I_2} \Rightarrow n = \frac{V_1 - V_2}{V_T \ln(I_1/I_2)} = 1.0225$$

$$I_s = I_1 e^{-V_1/nV_T} = 1.81 \times 10^{-15} \text{ A}$$

3.48

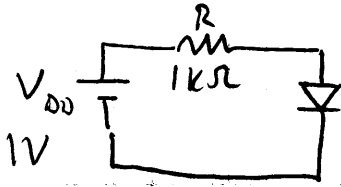

$$I_S = 10^{-15} \text{ A}$$

$$n = 1$$

$$V_T = 25 \text{ mV}$$

Assume $V_{D1} = 0.7 \text{ V}$

$$I_{D2} = \frac{V_R}{R} = \frac{V_{DD} - V_{D1}}{R} = 0.300 \text{ mA}$$

$$V_{D2} = n V_T \ln(I_{D2}/I_S) = 0.6607 \text{ V}$$

$$I_{D3} = \frac{V_{DD} - V_{D2}}{R} = 0.339 \text{ mA}$$

$$V_{D3} = n V_T \ln(I_{D3}/I_S) = 0.6638 \text{ V}$$

$$I_{D4} = \frac{V_{DD} - V_{D3}}{R} = 0.336 \text{ mA}$$

$$V_{D4} = n V_T \ln(I_{D4}/I_S) = 0.6635 \text{ V}$$

$$I_{D5} = \frac{V_{DD} - V_{D4}}{R} = 0.336 \text{ mA}$$

$$V_{D5} = n V_T \ln(I_{D5}/I_S) = 0.6635 \text{ V}$$

$$V_D = 0.6635 \text{ V}$$


$$I_D = 0.336 \text{ mA}$$

OR


$$V_D = V_{DD} - n V_T \ln\left(\frac{I_S R e^{(V_{DD}/n V_T)}}{n V_T}\right)$$

$$= 0.6635 \text{ V (from MATLAB)}$$

3.70

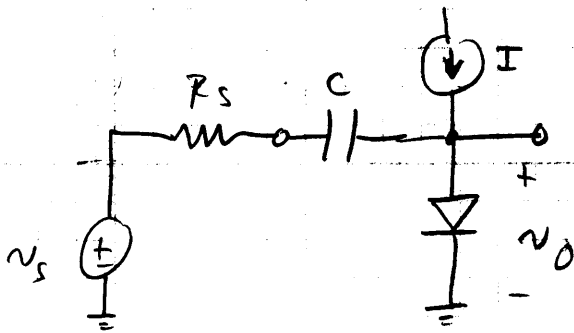

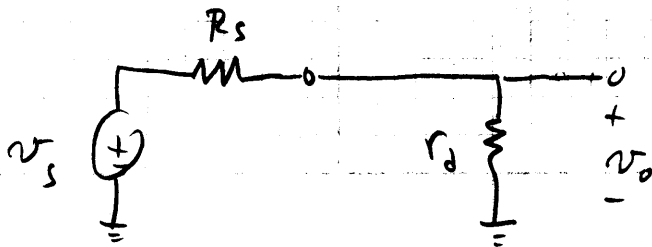Small-signal model: C is a short, I is an open, Diode is a resistor ($r_d = \frac{nV_T}{I}$)



$$v_o = \frac{r_d}{r_d + R_s} v_s = \frac{\frac{nV_T}{I}}{\frac{nV_T}{I} + R_s} v_s = \frac{nV_T}{nV_T + IR_s} v_s$$

Let $v_s = 10 \text{ mV}$, $R_s = 1 \text{ k}\Omega$, $n = 2$, $V_T = 25 \text{ mV}$

I	v_o
1 mA	0.476 mV
0.1 mA	3.333 mV
$1 \mu\text{A}$	9.804 mV

$$\frac{v_o}{v_s} = \frac{nV_T}{nV_T + IR_s} \Rightarrow I = \frac{\frac{nV_T}{(v_o/v_s)} - nV_T}{R_s}$$

For $\frac{v_o}{v_s} = \frac{1}{2}$, $I = \frac{nV_T}{R_s} = 50 \mu\text{V}$

3.77

$$V_z = V_{z0} + r_z I_z \quad (\text{eqn } 3.56)$$

$$V_{z0} = V_z - r_z I_z = 9.1 \text{ V} - (5 \Omega)(28 \text{ mA}) =$$

$$V_z = V_{z0} + r_z I_z = 8.96 \text{ V}$$

I_z	V_z
10 mA	9.01 V
100 mA	9.46 V