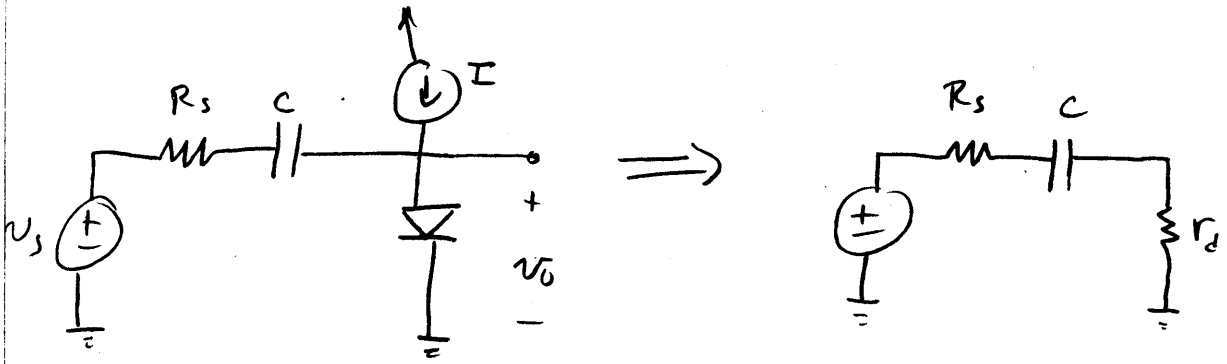


**EE 321**  
**Fall 2002**

**Homework #6**

**Solutions**

3.71



$$V_o(s)/V_s(s) = \frac{r_d}{r_d + \frac{1}{Cs} + R_s} = \frac{r_d Cs}{1 + (r_d + R_s)Cs}$$

$$r_d = \frac{nV_T}{I}$$

$$V_o(s)/V_s(s) = \frac{\frac{nV_T}{I} Cs}{1 + \left(\frac{nV_T}{I} + R_s\right)Cs}$$

3 dB freq:  $\omega_{3dB} = \frac{1}{\left(\frac{nV_T}{I} + R_s\right)C}$        $f_{3dB} = \frac{\omega_{3dB}}{2\pi} = \frac{1}{2\pi\left(\frac{nV_T}{I} + R_s\right)C}$

Let  $n=2$ ,  $V_T = 25 \text{ mV}$ ,  $R_s = 1 \text{ k}\Omega$ ,  $f_{3dB} = 100 \text{ Hz}$

$$C = \frac{1}{2\pi\left(\frac{nV_T}{I} + R_s\right)f_{3dB}}$$


$I$	$C$
$10 \mu\text{A}$	$0.26 \mu\text{F}$
$1 \text{ mA}$	$1.5 \mu\text{F}$

Need  $C > 1.5 \mu\text{F}$

For  $C = 1.5 \mu\text{F}$ ,  $f_{3dB} = 17 \text{ Hz}$  @  $I = 10 \mu\text{A}$

$f_{3dB} = 100 \text{ Hz}$  @  $I = 1 \text{ mA}$

3.80

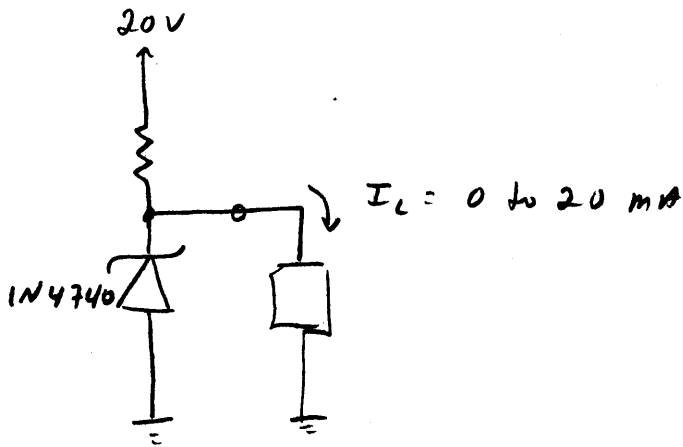

(a)  $V_{z0} = V_z - r_z I_{zT} = 10\text{V} - (7\Omega)(25\text{mA}) = 9.825\text{V}$

(b)  $V_s = 20\text{V} \pm 25\% \Rightarrow V_s \text{ between } 25\text{V} \text{ and } 15\text{V} \Rightarrow V_{s\text{min}} = 15\text{V}$

$I_{z\text{min}} = 5\text{mA}, r_z = 7\Omega, I_{L\text{max}} = 20\text{mA}$

$R \leq \frac{V_{s\text{min}} - V_{z0} - r_z I_{z\text{min}}}{I_{z\text{min}} + I_{L\text{max}}} = 205\Omega$


(c) Line Reg =  $\frac{\Delta V_o}{\Delta V_s} = \frac{r_z}{R+r_z} = \frac{7}{205+7} = 33\text{mV/V} = \underline{\underline{3.3\%}}$

For  $\pm 25\%$  change in  $V_s (\pm 5\text{V})$   $\Delta V_o = (33\text{mV/V})(10\text{V}) = 330\text{mV}$   
 $\% \text{ change} = 330\text{mV}/10\text{V} = 3.3\%$

(d) Load Reg =  $-(r_z || R) = -\frac{(7)(205)}{7+205} = \underline{\underline{6.8\text{mV/mA}}}$

For 20mA change,  $\Delta V_o = (6.8\text{mV/mA})(20\text{mA}) = 135\text{mV}$   
 $\% \text{ change} = \frac{135\text{mV}}{10\text{V}} \times 100 = \underline{\underline{1.35\%}}$

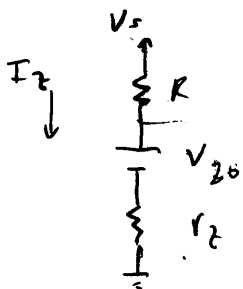(e) Maximum current is when  $I_L = 0$  and  $V_s = 25\text{V}$




$I_{z\text{max}} = \frac{V_s - V_{z0}}{R+r_z} = \frac{25 - 9.825}{205 + 7} = 72\text{mA}$

$V_{z\text{max}} = V_{z0} + r_z I_{z\text{max}} = 10.3\text{V}$

$P_{\text{max}} = I_{z\text{max}} V_{z\text{max}} = 744\text{mW}$

3.87

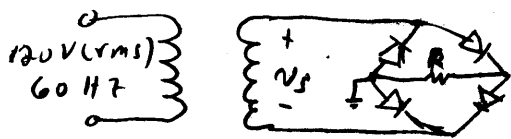

$$120 \text{ V RMS} \Rightarrow 120\sqrt{2} = 170 \text{ V peak}$$

$$10:1 \text{ step down} \Rightarrow \text{peak } v_s \text{ is } 17 \text{ V}$$

$$v_s = 17 \sin(120\pi t)$$

$$\text{By KVL, } v_s = v_R + 2 \times v_{\text{diode drop}}$$

$$v_{R \text{ peak}} = 17 - 2(0.7) = 15.6 \text{ V}$$

$v_s$  must reach 1.4V before the diodes turn on

Diodes will conduct when  $17 \sin(120\pi t) > 1.4$

$$120\pi t = \sin^{-1}\left(\frac{1.4}{17}\right) = 0.082$$


$$t = \frac{0.082}{120\pi} = 0.22 \text{ ms}$$

Diodes are off for 4 times this long each cycle

off for 0.88 ms out of  $\frac{1}{60 \text{ Hz}} = 16.7 \text{ ms}$

on for  $16.7 - 0.88 = 15.8 \text{ ms}$

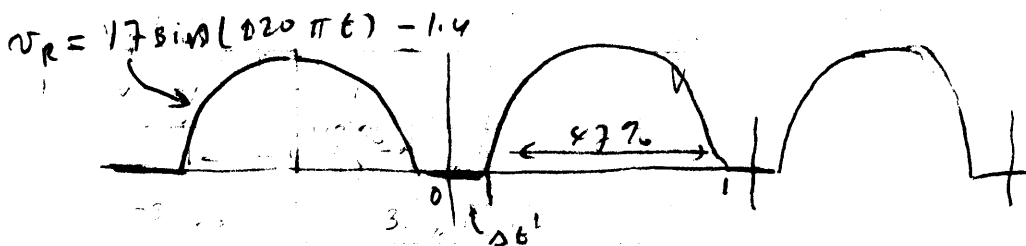% time on:  $\frac{15.8 \text{ ms}}{16.7 \text{ ms}} = 95\%$  of the time




$$v_{R \text{ avg}} = \frac{1}{T/2} \int_{t_1}^{t_2} (17 \sin(120\pi t) - 1.4) dt$$

$$= 120 \left[ \frac{-17}{120\pi} \cos(120\pi t) - 1.4t \right]_{0.22 \text{ ms}}^{\frac{1}{120} - 0.22 \text{ ms}} = 9.5 \text{ V}$$

$$i_{R \text{ avg}} = v_{R \text{ avg}} / R = 19.5 \text{ mA}$$

3.94

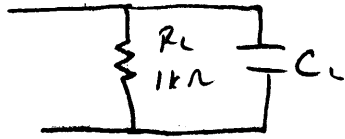

$$f = 160 \text{ Hz}$$

$$V_p = V_s - 2V_{D0} = 17 - 1.4 = 15.6 \text{ V}$$

$$V_{r1} = 0.1 V_p = 1.56 \text{ V}$$

$$V_{r2} = 0.01 V_p = 0.156 \text{ V}$$

$$(i) C_1 = \frac{V_p}{2f V_{r1} R} = \frac{15.6}{2(160)(1.56)(1k)} = 83 \mu\text{F}$$

$$(ii) C_2 = \frac{V_p}{2f V_{r2} R} = 830 \mu\text{F}$$

$$(a) V_0 = V_p - \frac{1}{2} V_r$$

$$(i) V_{01} = 15.6 - 1.56 = 14.04 \text{ V}$$

$$(ii) V_{02} = 15.6 - 0.156 = 15.444 \text{ V}$$

$$(b) \Delta t = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_p}} = \frac{1}{2\pi f} \sqrt{\frac{2V_r}{V_p}} = \frac{T}{2\pi} \sqrt{\frac{2V_r}{V_p}} \quad (\text{eq 3.72})$$

Diode conducts for  $\Delta t$  of each half cycle  $T/2$   
so fraction of time diode is on is  $\frac{\Delta t}{T/2} = \frac{2\Delta t}{T}$

$$(i) DC_1 = \frac{2\Delta t_1}{T} = \frac{1}{\pi} \sqrt{\frac{2V_{r1}}{V_p}} = 14\%$$

$$(ii) DC_2 = \frac{2\Delta t_2}{T} = \frac{1}{\pi} \sqrt{\frac{2V_{r2}}{V_p}} = 4.5\%$$

$$(c) i_{D_{av}} = I_L (1 + \pi \sqrt{V_p / 2V_{r1}}) \quad I_L = \frac{V_0}{R} \quad (\text{eq 3.76})$$

$$(i) i_{D_{av1}} = \frac{V_{01}}{R} (1 + \pi \sqrt{V_p / 2V_{r1}}) = 120 \text{ mA}$$

$$(ii) i_{D_{av2}} = 368 \text{ mA}$$

$$(d) i_{D_{peak}} = I_L (1 + 2\pi \sqrt{V_p / 2V_{r1}}) \quad (\text{eq 3.77})$$

$$(i) i_{D_{peak1}} = 230 \text{ mA}$$

$$i_{D_{peak2}} = 705 \text{ mA}$$


3.97

$$V_0 = 15V, \quad V_p = 16V, \quad V_r = 2V, \quad R = 150\Omega$$

(a) Need  $V_p = 16V$ , so  $V_s = V_p + 2 \times \text{diode drop} = 17.4V$

$$V_s (RMS) = \frac{V_s}{\sqrt{2}} = 12.3V$$

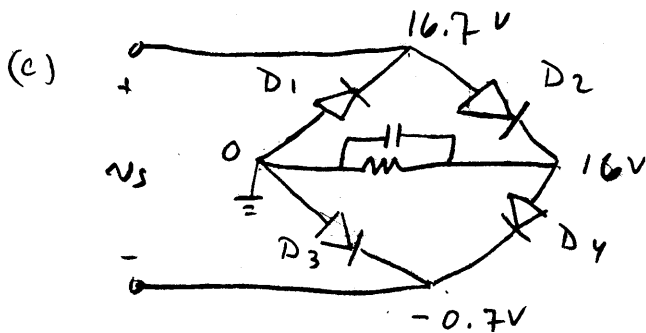(b)  $C = \frac{V_p}{2fV_r R} = \frac{16}{2(60)(2)(150)} = 444\mu F \rightarrow 500\mu F$



Voltages when  $V_s = 17.4V$

$D_2$  and  $D_3$  conduct

Reverse bias on  $D_1$  &  $D_4$  is  $16.7V$

$$PIV > 16.7V$$

(d)  $i_{D_{ave}} = I_L \left( 1 + \pi \sqrt{V_p / 2V_r} \right)$  (eq 3.76)

$$= \frac{V_0}{R} \left( 1 + \pi \sqrt{V_p / 2V_r} \right)$$

$$= \frac{15V}{150\Omega} \left( 1 + \pi \sqrt{16 / (2 \cdot 2)} \right) = 730mA$$

(e)  $i_{D_{max}} = I_L \left( 1 + 2\pi \sqrt{V_p / 2V_r} \right)$  (eq 3.77)

$$= 1.36A$$