

EE 321
Fall 2002

Homework #7

Solutions

4.5

Device	i_C (mA)	i_B (mA)	i_E (mA)	α	β
a	10.0	10.10	10.1	0.99	100
b	1.10	0.02	1.12	0.982	55
c	0.63	0.01	0.64	0.984	63
d	98.0	1.0	99.0	0.990	98
e	0.010	0.001	0.011	0.909	10
f	10.0	0.2	10.1	X	100
g	10.1	0.1	10.0	0.99	X
h	0.990	0.010	1.00	0.99	99
i	12.90	0.015	12.91	0.995	193

(a) $i_C = \alpha i_E \Rightarrow \alpha = i_C / i_E = 0.99 \quad \alpha = \frac{\theta}{\theta+1} = 0.99$ ✓

$$i_C = \beta i_B \Rightarrow i_B = i_C / \beta = 0.10 \text{ mA}$$

(b) $i_B = (1 - \alpha) i_E \Rightarrow \alpha = 1 - \frac{i_B}{i_E} = 0.982$

$$i_C = \alpha i_E = 1.10 \quad i_C = \beta i_B \Rightarrow \beta = i_C / i_B = 55$$

(c) $\alpha = \frac{\theta}{\theta+1} = 0.984$ ✓ $i_C = \beta i_B \Rightarrow i_B = i_C / \beta = 0.01$

$$i_C = \alpha i_E \Rightarrow i_E = i_C / \alpha = 0.64$$

(d) $\alpha = \frac{\theta}{\theta+1} = 0.990$ ✓ $\alpha = \frac{i_C}{i_E} = 0.990$ ✓

$$i_B = i_C / \beta = 1.0$$

(e) $\beta = \frac{i_E}{i_B} = 1; \beta = 10$ ✓

$$\alpha = \frac{\theta}{\theta+1} = 0.909$$

$$i_C = \alpha i_E =$$

$$(f) i_C = \beta i_B = 20.0 \quad \text{Inconsistent}$$

$$(g) i_C = \alpha i_E = 9.9 \quad \text{Inconsistent}$$


$$(h) \beta = i_C/i_B = 99 \quad \checkmark \quad \alpha = \frac{\beta}{\beta+1} = 0.99$$

$$i_E = (\beta+1) i_B = 1.00$$

$$(i) \alpha = \frac{\beta}{\beta+1} = 0.995 \quad \checkmark \quad i_C = \beta i_B = 2.90$$

$$i_E = (\beta+1) i_B = 2.91$$

4.10

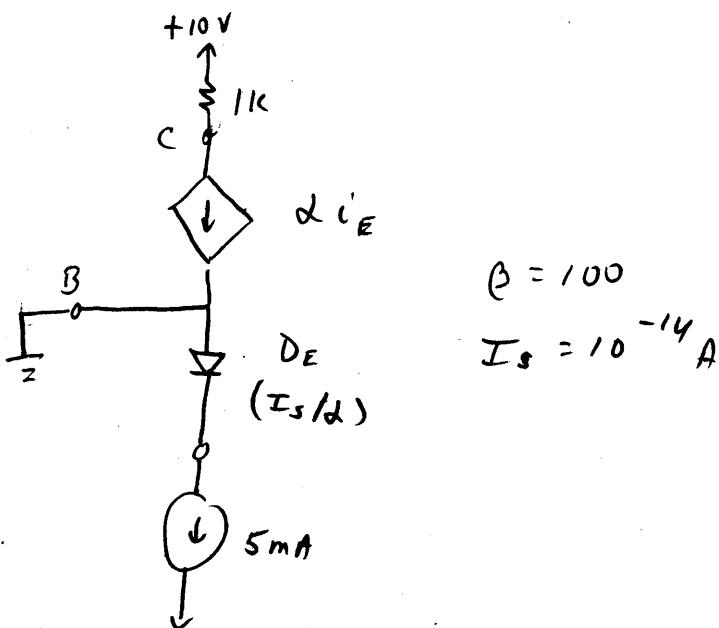

$$i_E = 5 \text{ mA} \quad i_C = \alpha i_E = \frac{\beta}{\beta+1} i_E = 4.95 \text{ mA}$$


$$i_E = (I_s/\alpha) e^{\frac{V_{BE}}{V_T}} \Rightarrow V_{BE} = V_T \ln \frac{\alpha i_E}{I_s} = 0.673 \text{ V}$$

$$V_E = V_B - V_{BE} = 0 \text{ V} - 0.673 \text{ V} = -0.673 \text{ V}$$

$$V_C = V_{CC} - i_C R_C = 10 \text{ V} - (4.95 \text{ mA})(1 \text{ k}) = 5.05 \text{ V}$$

$$i_B = i_C / \beta = 5.01 \mu \text{A}$$

4.15

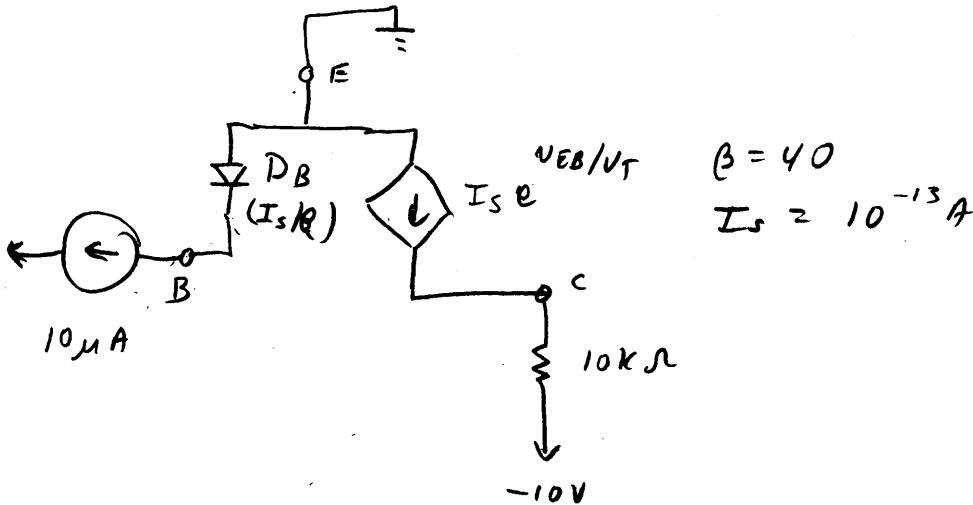

$$i_c = \beta i_B = (40)(10\mu A) = 0.40 \text{ mA}$$

$$i_c = I_s e^{v_{EB}/V_T} \Rightarrow v_{EB} = V_T \ln \frac{i_c}{I_s} = 0.553 \text{ V}$$

$$v_B = V_E - v_{EB} = 0 - 0.553 \text{ V} = -0.553 \text{ V}$$

$$v_C = -10 \text{ V} + i_c R_C = -10 \text{ V} + (0.40 \text{ mA})(10 k\Omega) = -6 \text{ V}$$

$$i_E = (\beta + 1)i_B = (41)(10\mu A) = 0.41 \text{ mA}$$

4.16


$$i_c = I_s e^{v_{EB}/V_T} \Rightarrow I_s = i_c e^{-v_{EB}/V_T} = 1.27 \times 10^{-14}$$

$$v_{EB} = V_T \ln i_c / I_s$$


$$\text{For } i_c = 10 \text{ mA: } v_{EB} = 0.684 \text{ V}$$

$$\text{For } i_c = 5 \text{ A: } v_{EB} = 0.840 \text{ V}$$

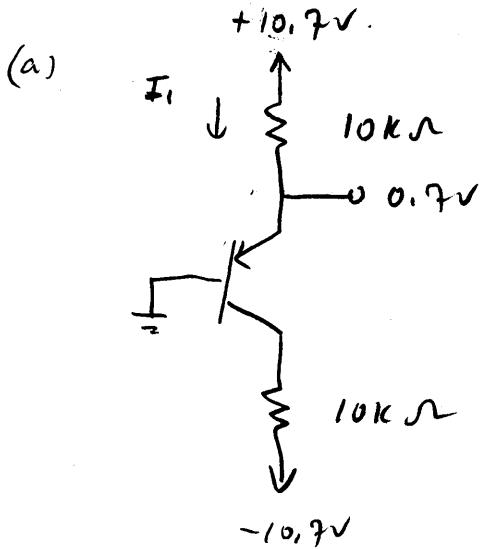4.19 Large $\beta \Rightarrow i_E \approx i_c, i_B \approx 0$


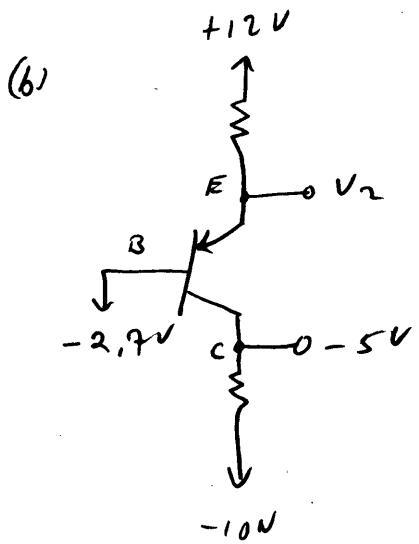
$$I_C = \frac{10.7V - 0.7V}{10k\Omega} = 1mA$$




$$V_{EB} = V_E - V_B \Rightarrow V_E = V_{EB} + V_B$$

$$V_B = -2.7V, \text{ so}$$

$$V_E = 0.7V - 2.7V = -2.0V$$

$$V_2 = V_E = -2.0V$$

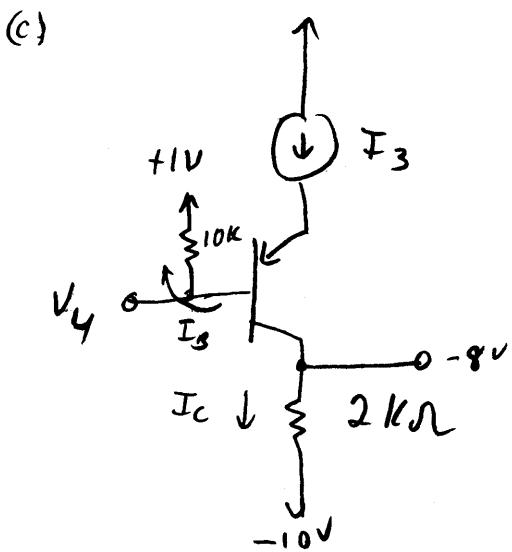


$$I_C = \frac{-8V - (-10V)}{2k\Omega} = 1mA$$

$$I_E \approx I_C = 1mA$$

$$I_3 = I_E = 1mA$$

$$V_4 = 1V + I_B(10k\Omega) = 1V$$

(d)

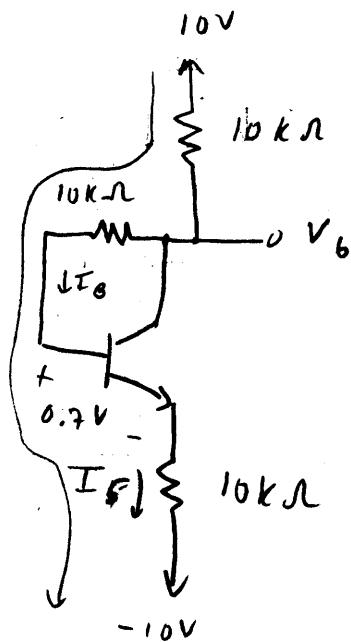

$$20V = I_C R_C + I_B R_B + V_{BE} + I_E R_E$$

$$= I_E R_E + V_{BE} + I_E R_E$$

$$(I_E \approx I_E; I_B \approx 0)$$


$$I_E = \frac{20 - V_{BE}}{R_C + R_E} =$$

$$= \frac{20 - 0.7}{10k + 10k} = 0.965 \text{ mA}$$

$$I_S = I_E = 0.965 \text{ mA}$$

$$V_B = 10V - I_C R_C = 10V - (0.965 \text{ mA})(10k\Omega) = 0.35V$$

4.36

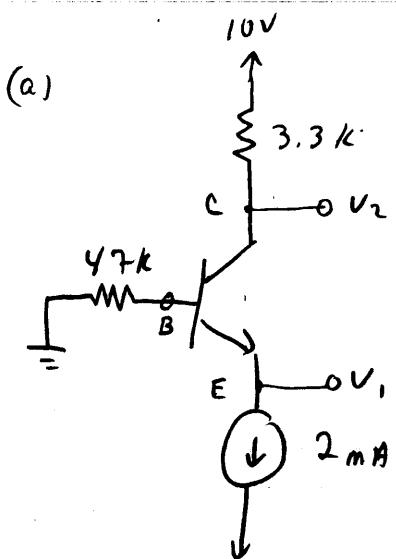

$$\alpha = \frac{\beta}{\beta+1} = 0.990$$

$$I_C = \alpha I_E = 1.98 \text{ mA}$$

$$V_2 = 10V - I_C R_C$$

$$= 10V - (1.98 \text{ mA})(3.3 \text{ k}\Omega) = 3.47V$$


$$I_B = I_C / \beta = 19.8 \mu\text{A}$$

$$V_B = 0 - I_B R_B = (-19.8 \mu\text{A})(4.7 \text{ k}\Omega)$$

$$= -0.931V$$

$$V_i = V_E = V_B - V_{BE} = -0.931 - 0.700$$

$$= -1.63V$$

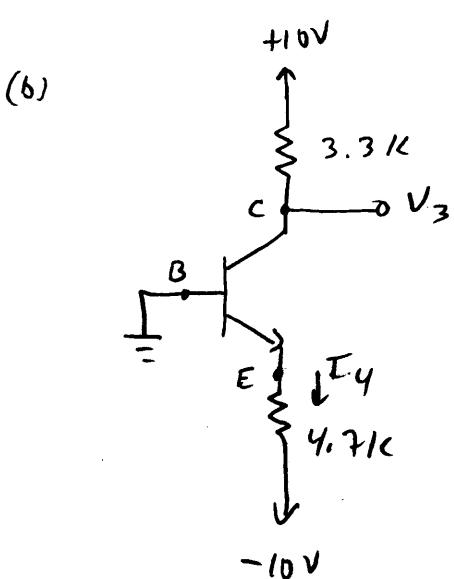

$$V_E = V_B - V_{BE} = 0 - 0.7 = -0.7V$$


$$I_4 = \frac{V_E - (-10V)}{R_E}$$

$$I_4 = \frac{-0.7V + 10V}{4.7k} = 1.98 \text{ mA}$$

$$I_C = \alpha I'_E = \alpha I_4 = 1.96 \text{ mA}$$

$$V_3 = 10V - I_C R_C$$
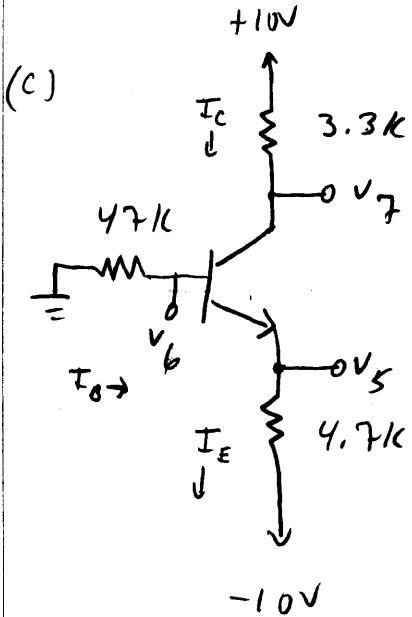
$$= 10V - (1.96 \text{ mA})(3.3 \text{ k}\Omega) = 3.53V$$



KVL from ground through
 R_B , V_{BE} , R_E to $-10V$:

$$10V = I_B R_B + V_{BE} + I_E R_E$$

$$= I_B R_B + V_{BE} + (\rho + 1) R_E$$

$$I_B = \frac{10 - V_{BE}}{R_B + (\rho + 1) R_E}$$


$$= \frac{10 - 0.7}{47k + (10)(4.7k)} = 0.019mA$$

$$\begin{aligned} V_U &= 0 - I_B R_B \\ &= 0 - (0.019mA)(47k\Omega) \\ &\approx -0.889V \end{aligned}$$

$$\begin{aligned} V_T &= 10V - I_C R_C = 10V - \beta I_B R_C \\ &= 10V - (100)(0.019mA)(3.3k\Omega) \approx 3.73V \end{aligned}$$

$$\begin{aligned} V_B &= V_B - V_{BE} = V_B - V_{BZ} = \\ &= -0.889V - 0.7V \approx -1.59V \end{aligned}$$

(d)

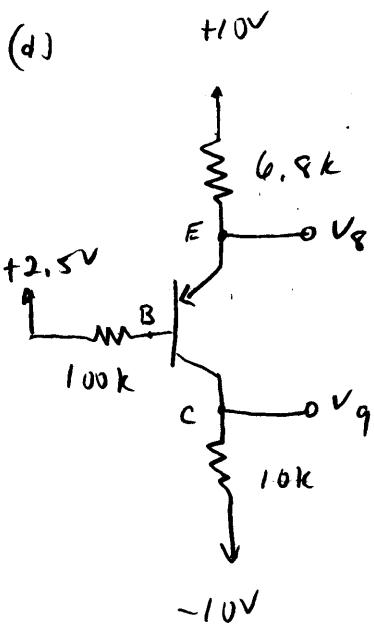

Do KVL from +10V through
 R_E , V_{EB} , R_B to +2.5V:

$$7.5V = I_E R_E + V_{EB} + I_B R_B \\ = (\beta + 1) I_B R_E + V_{EB} + I_B R_B$$



$$I_B = \frac{7.5V - V_{EB}}{(\beta + 1) R_E + R_B}$$

$$= \frac{7.5V - 0.7V}{(101)(6.8k) + 100k} = 8.64 \mu A$$

$$V_B = 10V - I_E R_E = 10V - (\beta + 1) I_B R_E \\ = 10V - (101)(8.64 \mu A)(6.8k) \\ = 4.06V$$

$$V_Q = I_C R_C - 10V = \beta I_B R_C - 10V \\ = (101)(8.64 \mu A)(10k) - 10V \\ = -1.36V$$


(e)

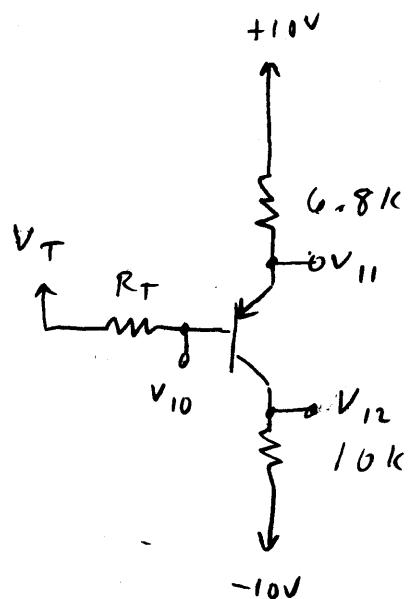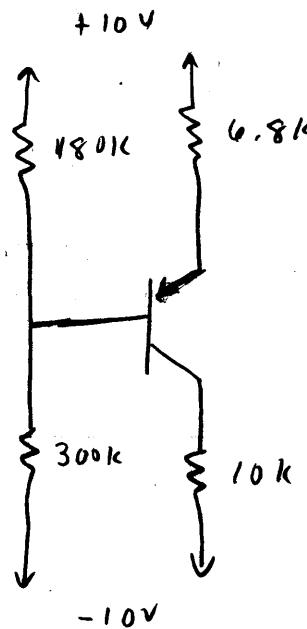

Simplify bias on base to its Thevenin equivalent:

$$R_T = 180k \parallel 300k = 112.5k$$
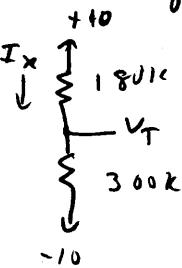
$$I_x = \frac{20V}{180k + 300k} = 41.7 \mu A$$



$$V_T = 10V - I_x(180k) = 2.5V$$

Do KVL from +10V through R_E , V_{EB} , R_T to V_T

$$10V - V_T = I_E R_E + V_{EB} + I_B R_T = (\beta + 1) I_B R_E + V_{EB} + I_B R_T$$

$$I_B = \frac{10V - V_T - V_{EB}}{(\beta + 1) R_E + R_T} = 8.51 \mu A$$

$$V_{10} = I_B R_T + V_T = 3.46V$$

$$V_{11} = 10V - I_E R_E = 10V - (\beta + 1) I_B R_E = 4.16V$$

$$V_{12} = I_C R_C - 10V = \beta I_B R_C - 10V = -1.49V$$