

EE321 – Fall 2002

Homework 8

Due October 21, 2002

1. Problem 4.23.
2. Problem 4.26.
3. Problem 4.29.
4. Problem 4.38.
 - When the problem asks “What happens if the transistor is replaced with another having $\beta = 100$?”, it wants you to find the value of V_C using the value of R_C you found for $\beta = 50$.
5. Problem 4.40.
 - The answers to Part (b) of 4.40 are
 - $V_1 = 0.837$ V
 - $V_2 = 1.54$ V
 - $V_3 = -2.22$ V
 - $V_4 = 2.86$ V
 - $V_5 = -1.52$ V