

**EE 321**  
**Fall 2002**

**Homework #8**

**Solutions**

4.23

$$i_c = I_s e^{\frac{v_{BE}}{V_T}} \left( 1 + \frac{v_{CE}}{V_A} \right) = 10^{-15} e^{\frac{v_{BE}/0.025}{100}} \left( 1 + \frac{v_{CE}}{100} \right)$$

$$i_c = \underbrace{I_s e^{\frac{v_{BE}}{V_T}}}_{y\text{-intercept}} + \underbrace{\frac{I_s e^{\frac{v_{BE}/V_T}{100}}}{V_A} v_{CE}}_{\text{slope}}$$

| $v_{BE}$ (V)   | 0.65  | 0.7   | 0.72  | 0.73  | 0.74  |
|----------------|-------|-------|-------|-------|-------|
| Intercept (mA) | 0.20  | 1.45  | 3.22  | 4.80  | 7.16  |
| Slope (mA/V)   | 0.002 | 0.014 | 0.032 | 0.048 | 0.072 |

| $v_{BE}$ (V)   | 0.65  | 0.7   | 0.72  | 0.73  | 0.74  |
|----------------|-------|-------|-------|-------|-------|
| Intercept (mA) | 0.20  | 1.45  | 3.22  | 4.80  | 7.16  |
| Slope (mA/V)   | 0.002 | 0.014 | 0.032 | 0.048 | 0.072 |

See next page for plot

4.26

$$r_o = \frac{1}{\text{slope}} = \frac{1}{3 \times 10^{-5} \text{ V}} = 33.3 \text{ k}\Omega$$


$$r_o = \frac{V_A}{I_C} \Rightarrow V_A = r_o I_C = (33.3 \text{ k}\Omega)(3 \text{ mA}) = 100 \text{ V}$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{30 \text{ mA}} = 3.33 \text{ k}\Omega$$

```

IS=1e-15;
VT=25e-3;
vCE=0:1:15;
VA = 100;
vbe = [0.65;0.7;0.72;0.73;0.74];
for ii=1:length(vbe)
    iC(ii,:) = IS*exp(vbe(ii)/VT)*(1+vCE/VA);
end
plot(vCE,iC*1000)
legend('v_{BE}=0.65V' , 'v_{BE}=0.70V' , 'v_{BE}=0.72V' , 'v_{BE}=0.73V' , 'v_{BE}=0.74V')
xlabel('v_{CE} (V)', 'FontSize',16)
ylabel('i_C (mA)', 'FontSize',16)
grid
title('i_C vs v_{CE} for different values of v_{BE}' , 'FontSize',18);

```

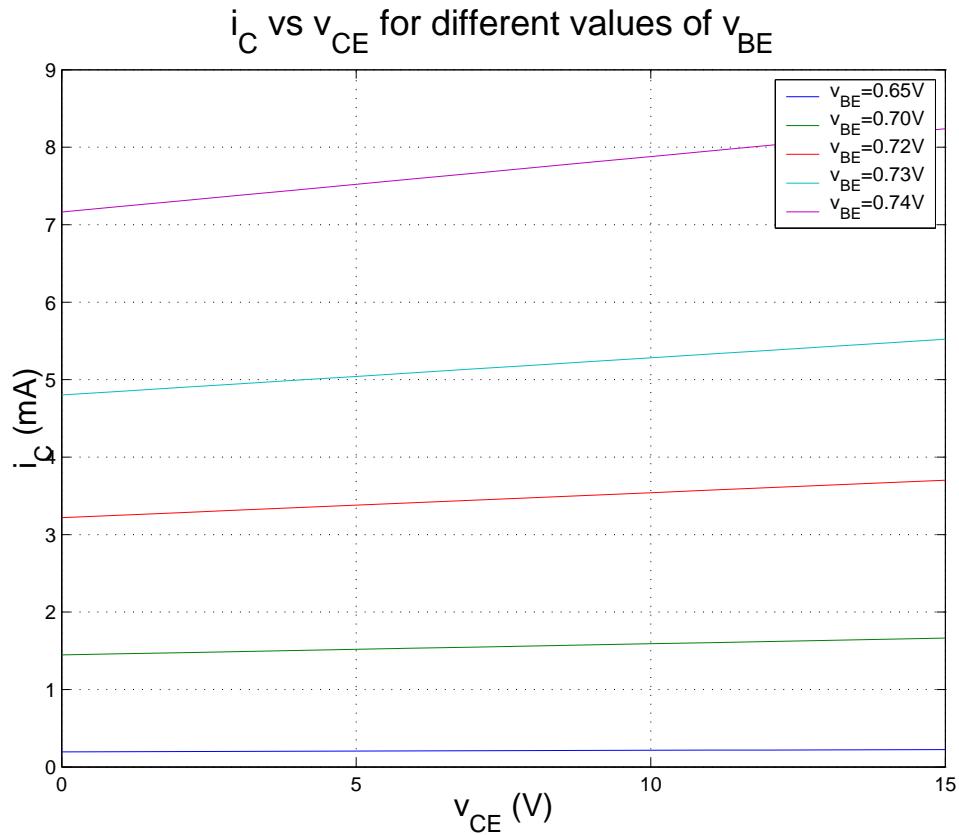

4.29

In the active region the plot of  $i_c$  vs.  $V_{CE}$  is a straight line

$$\therefore i_c = m V_{CE} + b$$

$$m = \frac{\text{rise}}{\text{run}} = \frac{i_{c2} - i_{c1}}{V_{CE2} - V_{CE1}} = \frac{1.1 \text{mA} - 1.0 \text{mA}}{10 \text{V} - 2 \text{V}} = 0.0125 \text{mA/V}$$

$$b = i_{c1} - m V_{CE1} = 1 \text{mA} - (0.0125 \text{mA/V})(2 \text{V}) = 0.975 \text{mA}$$


$$V_{CE} = \frac{i_c - b}{m} \quad \text{For } i_c = 0, \quad V_{CE} = \frac{-b}{m} = \frac{-0.975 \text{mA}}{0.0125 \text{mA/V}} = 78 \text{V}$$

OR

$$r_o = \frac{1}{\text{slope}} = \frac{\Delta V_{CE}}{\Delta i_c} = \frac{10 \text{V} - 2 \text{V}}{1.1 \text{mA} - 1.0 \text{mA}} = 80 \text{k}\Omega$$

$$r_o = \frac{V_A}{I_c} \Rightarrow V_A = r_o I_c = (80 \text{k}\Omega)(1 \text{mA}) = 80 \text{V}$$

4.38

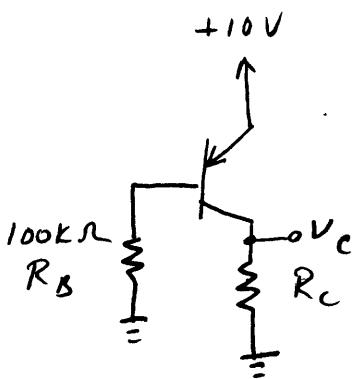

$$V_B = V_E - 0.7V = 10V - 0.7V = 9.3V$$

$$I_B = V_B / R_B = 9.3V / 100k\Omega = 93\mu A$$

$$I_C = \beta I_B = (50)(93\mu A) = 4.65mA$$

$$V_C = I_C R_C \Rightarrow R_C = V_C / I_C = 5V / 4.65mA = 1.075k\Omega$$

For  $\beta=100$ ,  $I_B$  will be the same, so

$$I_C = \beta I_B = (100)(93\mu A) = 9.3mA$$


$$V_C = I_C R_C = (9.3mA)(1.075k\Omega) = +10V$$

This is impossible - the transistor will not be in active mode - it will be saturated

$$V_C \approx 9.8V$$

4.40

+10V

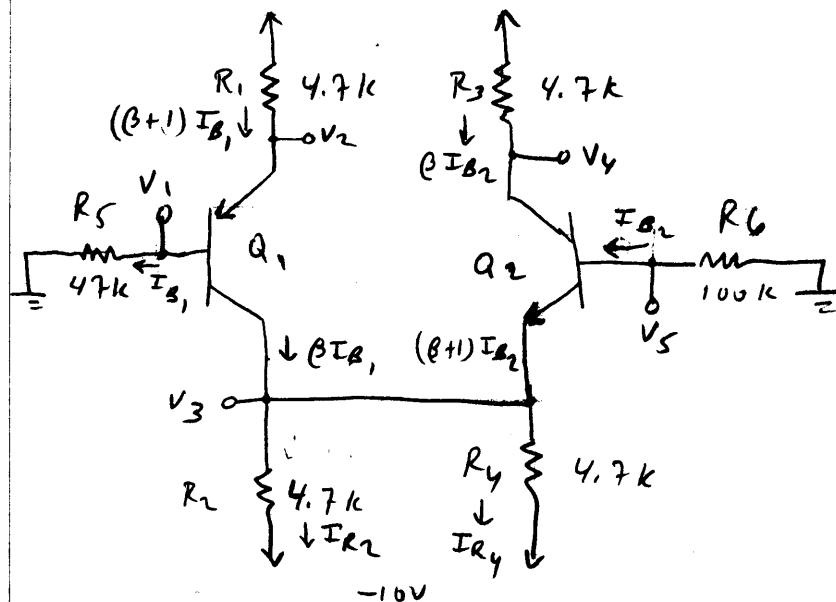

(a) With  $\beta = \infty$   $I_{B1} = I_{B2} = 0$ ,  $I_{C1} = I_{E1}$ , and  $I_{C2} = I_{E2}$

$$V_1 = 0 \quad (\text{because } I_{B1} = 0)$$

$$V_2 = V_1 + V_{E_{B1}} = 0 + 0.7V = 0.7V$$

$$V_5 = 0 \quad (\text{because } I_{B2} = 0)$$

$$V_3 = V_5 - V_{BE2} = 0 - 0.7V = -0.7V$$

Cannot find  $V_4$  because we do not know  $I_{C2}$ .

(We know  $I_{R2} = I_{Ry} = 9.3V / 4.7k$ , and  $I_{C1} + I_{E2} = I_{R2} + I_{Ry}$ ,

THERE IS NO WAY TO DETERMINE  $I_{C1}$ ,  $I_{E1}$  or  $I_{C2}$ )

(b)  $\beta = 100$

KVL from +10V through  $R_1$ ,  $V_{EB1}$ ,  $R_5$  to ground:

$$10V = (\beta + 1) I_{B1} R_1 + V_{EB1} + I_{B1} R_5 \Rightarrow I_{B1} = \frac{10V - 0.7V}{(\beta + 1) R_1 + R_5} = 0.0178mA.$$

KVL from GND through  $R_6$ ,  $V_{BE2}$ ,  $R_y$  to -10V:

$$\textcircled{1} \quad I_{B2} R_6 + V_{BE2} + I_{Ry} R_y = 10V$$

KCL at node  $V_3$ :

$$\textcircled{2} \quad \beta I_{B1} + (\beta + 1) I_{B2} = I_{R2} + I_{Ry}$$

$R_2$  and  $R_y$  are same size and same resistance, so

$$\textcircled{3} \quad I_{R2} = I_{Ry}$$

Eqs 1, 2, 3 are 3 eqns with 3 unknowns ( $I_{B_2}$ ,  $I_{R_2}$ ,  $I_{R_4}$ )

Solve these to find

$$I_{B_2} = 0.0152 \text{ mA}$$

$$I_{R_4} = 1.655 \text{ mA}$$

$$I_{R_2} = 1.655 \text{ mA}$$

$$V_1 = I_{B_2} R_5 = 0.837 \text{ V}$$

$$V_2 = V_1 + V_{EB_2} = 1.54 \text{ V}$$

$$V_3 = I_{R_2} R_2 - 10 \text{ V} = -2.22 \text{ V}$$

$$V_4 = 10 \text{ V} - (\beta + 1) I_{B_2} R_3 = 2.856 \text{ V}$$

$$V_5 = 0 \text{ V} - I_{B_2} R_6 = -1.52 \text{ V}$$

Consistency Check - calculate  $V_2$  and  $V_3$  other ways:

$$V_3 = V_5 - V_{BE_2} = -2.22 \text{ V} \quad \checkmark$$

$$V_2 = 10 \text{ V} - (\beta + 1) I_{B_2} R_2 = 1.55 \text{ V} \quad \checkmark$$