

EE321 – Fall 2002**Homework 9**

Due October 28, 2002

1. Problem 4.44.
2. Problem 4.48.
3. Problem 4.44.
4. Problem 4.55.
5. Problem 4.58.
6. Problem 4.61.
7. Problem 4.64.
8. Find the gain of the amplifier of Figure 1 of [Lab 8](#).