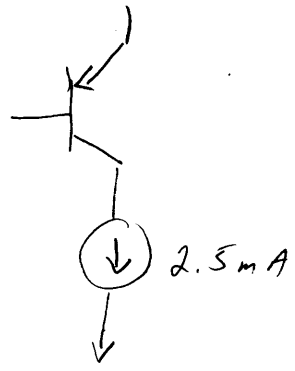


EE 321
Fall 2002

Homework #9

Solutions


4.44



$$\alpha = \frac{\beta}{\beta + 1} = \frac{50}{51} = 0.98$$

$$g_m = \frac{I_C}{V_T} = \frac{2.5 \text{ mA}}{25 \text{ mV}} = 100 \text{ mA/V}$$
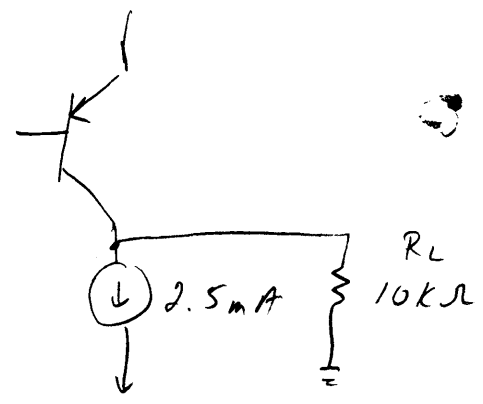
$$r_e = \frac{\alpha}{g_m} = \frac{0.98}{0.1 \text{ A/V}} = 9.8 \Omega$$




$$i_c = g_m v_{be}$$

$$v_c = i_c R_L = g_m v_{be} R_L$$

$$= (100 \text{ mA/V})(10 \text{ mV})(10 \text{ k}\Omega)$$

$$= 10 \text{ V}$$

4.48

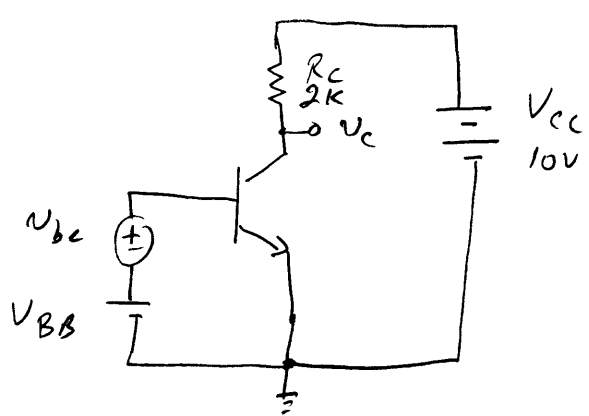

$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{10 \text{ V} - 2 \text{ V}}{2 \text{ k}\Omega} = 4 \text{ mA}$$

$$i_c = I_C + \frac{I_C}{V_T} v_{be}$$

$$= 4 \text{ mA} + \frac{4 \text{ mA}}{25 \text{ mV}} (0.004 \sin \omega t)$$

$$= 4 \text{ mA} + 0.64 \sin(\omega t) \text{ mA}$$

$$v_c = V_{CC} - i_c R_C = 10 \text{ V} - (4 \text{ mA} + 0.64 \sin(\omega t) \text{ mA}) 2 \text{ k}\Omega$$

$$= 10 \text{ V} - 8 \text{ V} - 1.28 \sin(\omega t) \text{ V}$$

$$= 2 \text{ V} - 1.28 \sin(\omega t) \text{ V}$$

$$i_B = i_c / \beta = 40 \mu\text{A} + 6.4 \sin(\omega t) \mu\text{A}$$

$$A_v = \frac{v_c}{v_i} = \frac{-1.28 \sin \omega t \text{ V}}{0.004 \sin \omega t \text{ V}} = -320 \text{ V/V}$$

4.55

$$I_E = 0.80 \text{ mA}$$

$$\alpha = 0.99$$

$$g_m = \frac{I_C}{V_T} = \frac{\alpha I_E}{V_T} = \frac{(0.99)(0.80 \text{ mA})}{25 \text{ mV}} = 32 \text{ mA/V}$$


$$r_e = \frac{\alpha}{g_m} = \frac{0.99}{32 \text{ mA/V}} = 31 \Omega$$

$$r_{\pi} = (\beta + 1) r_e$$

$$\alpha = \frac{\beta}{\beta + 1} \Rightarrow \beta = \frac{\alpha}{1 - \alpha} = \frac{0.99}{1 - 0.99} = 99$$

$$r_{\pi} = (\beta + 1) r_e \approx 100 r_e = 3.1 \text{ k}\Omega$$

4.58

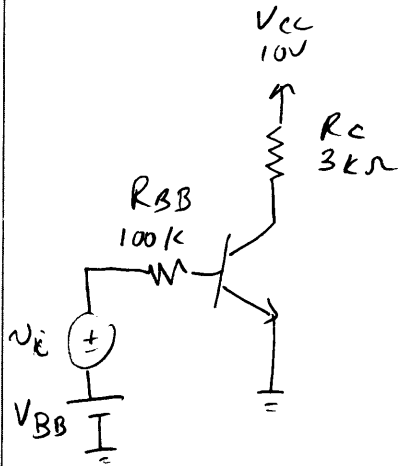

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = 0.023 \text{ mA}$$

$$V_C = V_{CC} - I_C R_C \\ = V_{CC} - \beta I_B R_C$$

Saturates when $V_i = 0.7 \text{ V} \Rightarrow V_{CC} - \beta I_B R_C = 0.7 \text{ V}$

$$\Rightarrow \beta = \frac{V_{CC} - 0.7 \text{ V}}{I_B R_C} = 135$$

For $\beta = 25$:

$$I_C = \beta I_B = 0.575 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = 23 \text{ mA/V}$$

$$r_e = \frac{\alpha}{g_m} = \frac{\beta / (\beta + 1)}{g_m} = 41.8 \Omega$$


$$r_{\pi} = (\beta + 1) r_e = 1.09 \text{ k}\Omega$$

$$v_o = -g_m v_{be} R_C$$

$$v_{be} = \frac{r_{\pi}}{r_{\pi} + R_{BB}} v_i$$

$$\frac{v_o}{v_i} = -g_m R_C \frac{r_{\pi}}{r_{\pi} + R_{BB}} \\ = -0.74 \text{ V/V}$$

4.61

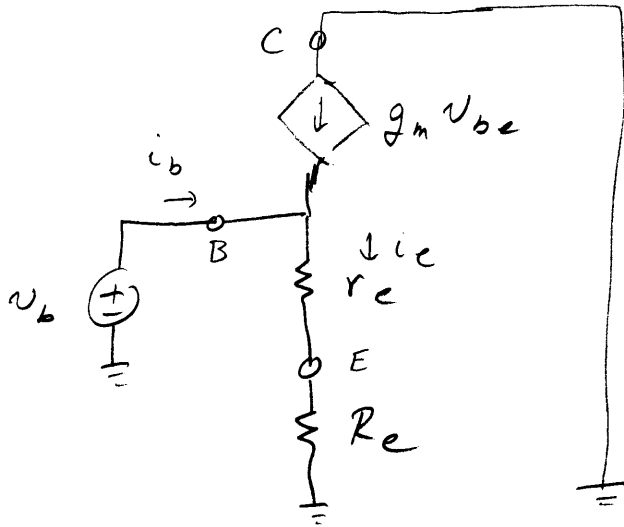

(a) Base voltage is v_b . Find v_e using resistor divider

$$v_e = \frac{R_e}{r_e + R_e} v_b$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

$$v_e/v_b = \frac{1 \text{ k}\Omega}{25 \Omega + 1 \text{ k}\Omega} = 0.976$$

(b)
$$i_e = \frac{v_b}{r_e + R_e}$$

$$g_m v_{be} + i_b = i_e \quad g_m = \frac{\alpha}{r_e} \quad v_{be} = v_b - v_e$$

$$\frac{\alpha}{r_e} (v_b - v_e) + i_b = \frac{v_b}{r_e + R_e}$$

$$\frac{\alpha}{r_e} \left(v_b - \frac{R_e}{r_e + R_e} v_b \right) + i_b = \frac{v_b}{r_e + R_e}$$

$$i_b = \frac{\alpha R_e v_b}{r_e (r_e + R_e)} - \frac{\alpha}{r_e} v_b + \frac{v_b}{r_e + R_e}$$


$$= \left[\frac{\alpha R_e}{r_e (r_e + R_e)} - \frac{\alpha (r_e + R_e)}{r_e (r_e + R_e)} + \frac{r_e}{r_e (r_e + R_e)} \right] v_b$$

$$= \frac{r_e (1 - \alpha)}{r_e (r_e + R_e)} v_b = \frac{1 - \frac{\beta}{\beta + 1}}{r_e + R_e} v_b = \frac{v_b}{(\beta + 1)(r_e + R_e)}$$


$$R_i = \frac{v_b}{i_b} = \frac{v_b}{\frac{v_b}{(\beta+1)(r_e+R_e)}} = (\beta+1)(r_e+R_e)$$

$$R_i = 101(25\Omega + 1k\Omega) = 104k\Omega$$

4.64

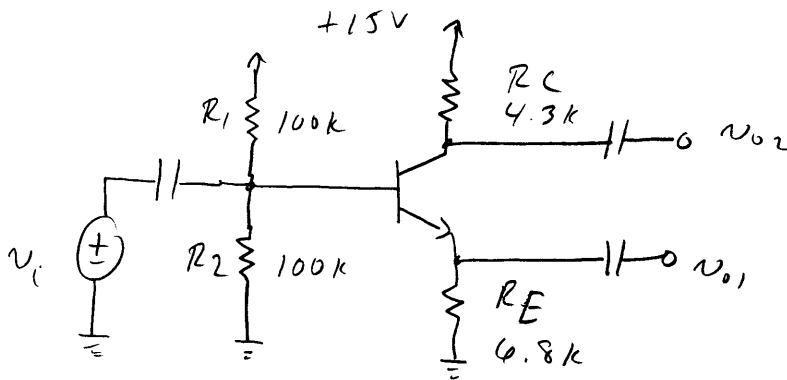

DC analysis

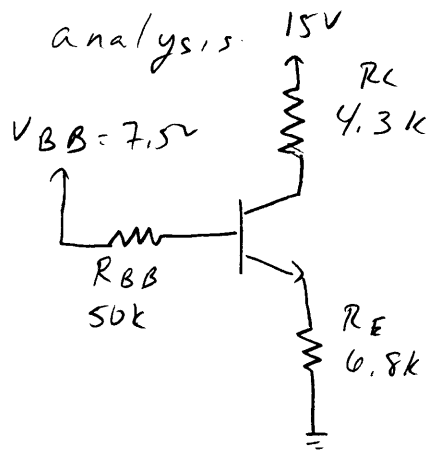

$$V_{BB} = \frac{R_2}{R_1+R_2} V_{CC} = \frac{1}{2} V_{CC} = 7.5V$$

$$R_{BB} = R_1 \parallel R_2 = 50k\Omega$$


For large β , $I_B = 0 \Rightarrow V_B = V_{BB} = 7.5V$

$$V_E = V_B - V_{BE} = 7.5V - 0.7V = 6.8V$$

$$I_E = \frac{V_E}{R_E} = \frac{6.8V}{6.8k} = 1mA$$

$$I_C = \frac{\beta}{\beta+1} I_E \approx I_E = 1mA$$

Small-signal analysis

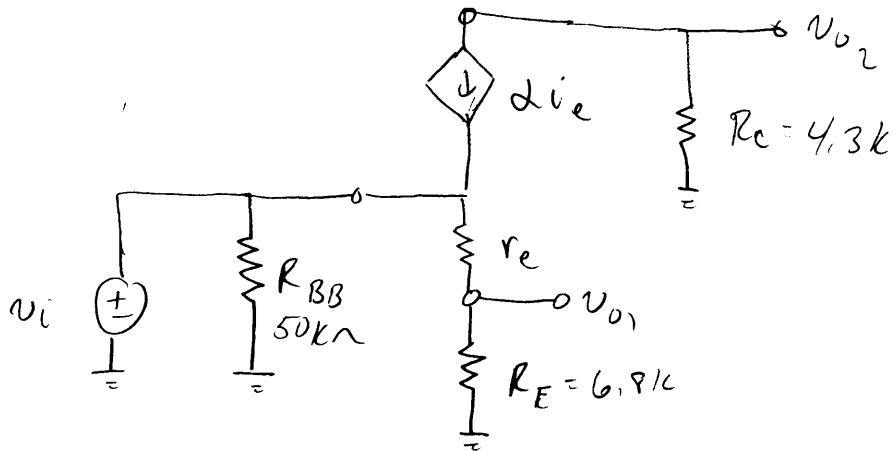

$$r_e = \frac{V_T}{I_E} = \frac{25\text{mV}}{1\text{mA}} = 25\Omega$$

$$i_e = \frac{v_i}{r_e + R_E}$$



$$v_{o1} = i_e R_E = \frac{R_E}{r_e + R_E} v_i$$

$$\frac{v_{o1}}{v_i} = \frac{R_E}{r_e + R_E} = \frac{6.8\text{k}}{25\Omega + 6.8\text{k}} = 0.996 \text{ V/V}$$

$$v_{o2} = -\beta i_e R_C = \frac{-\beta R_C}{r_e + R_E} v_i$$

$$\frac{v_{o2}}{v_i} = \frac{-\beta R_C}{r_e + R_E} = \frac{-1(4.3\text{k})}{25\Omega + 6.8\text{k}} = 0.63 \text{ V/V}$$

Gain of Fig 1 of Lab 8

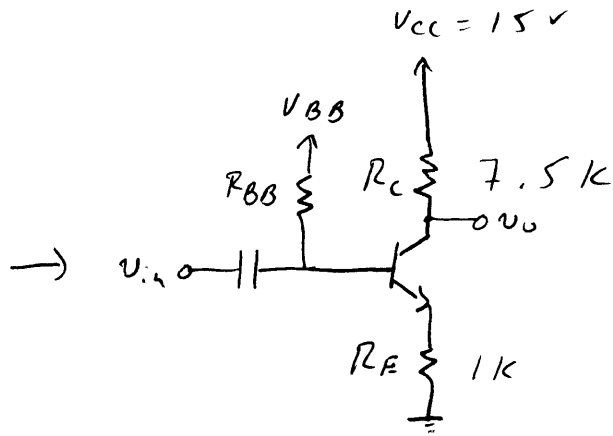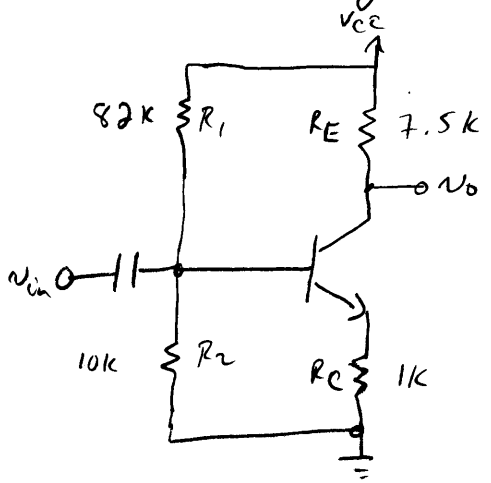


$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{10k}{10k + 82k} 15V = 1.63V$$

$$R_{BB} = R_1 || R_2 = 8.9k$$

Small signal model.

$$V_{BB} = I_B R_{BB} + V_{BE} + (\beta + 1) I_B R_E$$
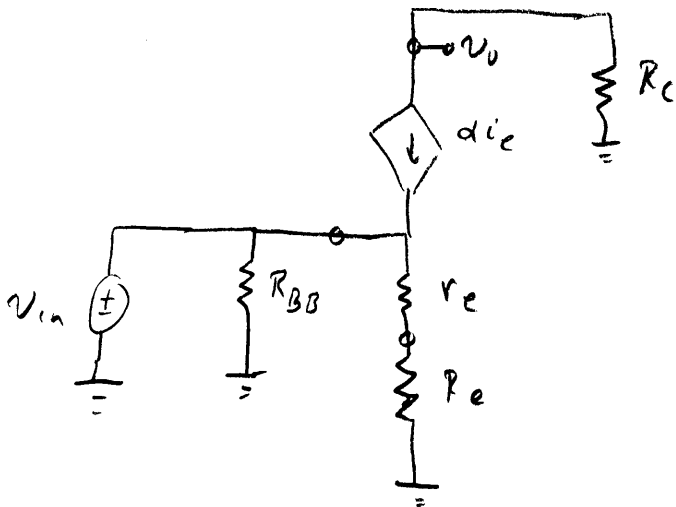
$$I_B = \frac{V_{BB} - V_{BE}}{R_{BB} + (\beta + 1) R_E} = 6.2 \mu A \text{ for } \beta = 150$$



$$v_o = -\alpha i_e R_C$$

$$i_e = \frac{v_b}{r_e + R_E} = \frac{v_{in}}{r_e + R_E}$$

$$\frac{v_o}{v_{in}} = \frac{-\alpha R_C}{r_e + R_E} \approx \frac{-R_C}{R_E}$$

$$\frac{v_o}{v_{in}} \approx -\frac{7.5k}{1k} = -7.5V/V$$

More exact:

$$r_e = \frac{V_T}{I_E} = \frac{V_T}{(\beta + 1) I_B} = 27 \Omega \text{ for } \beta = 150$$

$$\frac{v_o}{v_{in}} = \frac{-\alpha R_C}{r_e + R_E} = -7.25 \text{ for } \beta = 150$$

$$\frac{v_o}{v_{in}} \approx \frac{-R_C}{R_E} = -7.5$$

approximation is quite close