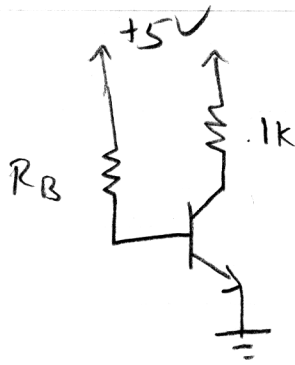


EE 321
Fall 2002

Homework #11

Solutions

4.97




$$I_C = \frac{5V - V_{CEsat}}{R_C} = \frac{5V - 0.2V}{1k} = 4.8mA$$

$$I_{B_{EUS}} = \frac{I_{C_{sat}}}{\beta} = \frac{4.8mA}{30} = 0.16mA$$

Want overdrive factor of 10, so $I_B = 10 I_{B_{EUS}} = 1.6mA$

$$R_B = \frac{5V - V_{BE}}{I_B} = \frac{5V - 0.7V}{1.6mA} = 2.7k\Omega$$

4.99

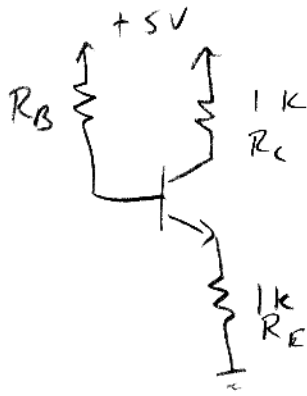

Assume active

$$5V = I_B R_B + V_{BE} + (\beta + 1) I_B R_E$$

$$I_B = \frac{5V - 0.7V}{R_B + (\beta + 1) R_E}$$

$$V_E = I_E R_E = (\beta + 1) I_B R_E$$

$$V_C = 5V - I_C R_C = 5V - \beta I_B R_E$$

$$V_{CE} = V_C - V_E$$

R_B	100k	10k	1k
I_B	0.021mA	0.039	0.042
V_E	2.2V	3.9V	4.3V
V_C	2.9V	1.1V	0.8V
V_{CE}	0.7V	-2.8V	-3.5V

For $R_B = 100k$, Q is active

$$V_E = (\beta + 1) I_B = 2.2V$$

$$V_B = V_{BE} + V_E = 2.9V$$

For $R_B = 10k$ and $1k$, Q is in saturation, so $V_{CE} = 0.2V$

$$5V = I_C R_C + V_{CE} + I_E R_E$$

$$5V = I_B R_B + V_{BE} + I_E R_E$$

$$I_E = I_C + I_B$$

$$4.8V = I_C + I_E$$

$$4.3V = I_B R_B + I_E$$

$$R_C = 1k$$

$$R_E = 1k$$

For $R_B = 10k$: $I_B = 0.18 \text{ mA}$ $I_C = 2.31 \text{ mA}$ $I_E = 2.49 \text{ mA}$

$$V_E = 2.49V$$


$$V_C = 2.69V$$

For $R_B = 1k$: $I_B = 1.27 \text{ mA}$ $I_C = 1.77 \text{ mA}$ $I_E = 3.03 \text{ mA}$

$$V_E = 3.03V$$

$$V_C = 3.23V$$

4.114

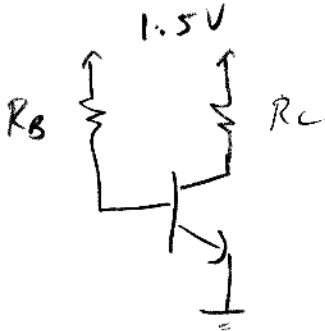

$$I_{C_{sat}} = \frac{1.5 - V_{CE_{sat}}}{R_C} = \frac{1.3V}{R_C}$$

$$I_B = \frac{1.5V - V_{BE}}{R_B} = \frac{0.8V}{R_B}$$

$$\beta_f = \frac{I_{C_{sat}}}{I_B} = 10$$

$$P = VI = 1.5V (I_B + I_{C_{sat}}) = 1mW$$

4 eqns, 4 unknowns

$$\frac{I_{C_{sat}}}{I_B} = 10 \Rightarrow \frac{\frac{1.3V}{R_C}}{\frac{0.8V}{R_B}} = 10 \Rightarrow \frac{R_B}{R_C} = 6.2 \Rightarrow R_B = 6.2 R_C$$

$$1.5V (I_B + I_{C_{sat}}) = 1mW \Rightarrow 1.5V \left(\frac{0.8}{R_B} + \frac{1.3}{R_C} \right) = 1mW$$

$$1.5V \left(\frac{0.8}{6.2 R_C} + \frac{1.3}{R_C} \right) = 1mW \Rightarrow R_C = 2.11k$$

$$R_B = 13.2k$$

5.4

$$k_n' = 50 \mu\text{A}/\text{V}^2 \quad V_t = 0.8\text{V} \quad W/L = 20 \quad V_{GS} = 5\text{V}$$

$$r_{DS} = \left[k_n' \frac{W}{L} (V_{GS} - V_t) \right]^{-1} = \left[(50 \mu\text{A}/\text{V}^2) (20) (5\text{V} - 0.8\text{V}) \right]^{-1}$$

$$r_{DS} = 240 \Omega$$

$$r_{DS} = \frac{V_{DS}}{i_D} \Rightarrow V_{DS} = r_{DS} i_D = (240 \Omega) (1\text{mA}) = 0.24\text{V}$$

$$\mu_p \approx 0.4 \mu_n \Rightarrow k_p' \approx 0.4 k_n'$$

To get same performance need $k_p' (W/L)_p = k_n' (W/L)_n$

$$(W/L)_p = \frac{k_n'}{k_p'} (W/L)_n = \frac{k_n'}{0.4 k_n'} \left(\frac{W}{L} \right)_n = 2.5 \left(\frac{W}{L} \right)_n$$

5.6

$$k_n' \mu_0 C_{ox} = 100 \mu A/V^2 \quad \text{for } L_{ox} = 20 \text{ nm (Table 5.1)}$$

$$V_t = 0.8 \text{ V} \quad W/L = 10$$

$$(a) \quad V_{GS} = 5 \text{ V} \quad V_{DS} = 1 \text{ V} \quad V_{GS} - V_t = 4.2 \text{ V}$$

$$V_{DS} < V_{GS} - V_t, \quad \text{so triode}$$

$$\begin{aligned} I_D &= k_n' \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \\ &= (0.1 \text{ mA/V}^2) (10) \left[(4.2)(1) - \frac{1}{2} (1)^2 \right] \\ &= 3.7 \text{ mA} \end{aligned}$$

$$(b) \quad V_{GS} = 2 \text{ V} \quad V_{DS} = 1.2 \text{ V} \quad V_{GS} - V_t = 1.2 \text{ V}$$

$$V_{DS} = V_{GS} - V_t; \quad \text{between triode and saturation}$$

$$\begin{aligned} I_D &= \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} (0.1 \text{ mA/V}^2) (10) (2 - 0.8)^2 = 0.72 \text{ mA} \end{aligned}$$

$$(c) \quad V_{GS} = 5 \text{ V} \quad V_{DS} = 0.2 \text{ V} \quad V_{GS} - V_t = 4.2 \text{ V}$$

$$V_{DS} < V_{GS} - V_t, \quad \text{so triode}$$

$$\begin{aligned} I_D &= (0.1 \text{ mA/V}^2) (10) \left[(4.2)(0.2) - \frac{1}{2} (0.2)^2 \right] \\ &= 0.82 \text{ mA} \end{aligned}$$

$$(d) \quad V_{GS} = 5 \text{ V} \quad V_{DS} = 5 \text{ V} \quad V_{GS} - V_t = 4.2 \text{ V}$$

$$V_{DS} > V_{GS} - V_t, \quad \text{so saturation}$$

$$\begin{aligned} I_D &= \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} (0.1 \text{ mA/V}^2) (10) (5 - 0.8)^2 \\ &= 8.82 \text{ mA} \end{aligned}$$

$$5.13 \quad i_D = k_n' \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$i_D \approx k_n' \frac{W}{L} (V_{GS} - V_t) V_{DS} \quad \text{for small } V_{DS}$$

$$i_{D1} = k_n' \frac{W}{L} (V_{GS1} - V_t) V_{DS}$$

$$i_{D2} = k_n' \frac{W}{L} (V_{GS2} - V_t) V_{DS}$$

$$\frac{i_{D2}}{i_{D1}} = \frac{(V_{GS2} - V_t)}{(V_{GS1} - V_t)}$$

$$\begin{aligned} \text{Solve for } V_t: \quad V_t &= \frac{i_{D1} V_{GS2} - i_{D2} V_{GS1}}{i_{D1} - i_{D2}} \\ &= \frac{(40 \mu A)(3V) - (80 \mu A)(2V)}{40 \mu A - 80 \mu A} \end{aligned}$$

$$\underline{V_t = 1V}$$

$$\frac{W}{L} = \frac{i_{D1}}{k_n' (V_{GS1} - V_t) V_{DS}} = \frac{40 \mu A}{(40 \mu A/V^2)(2V - 1V)(0.1V)}$$

$$\underline{\underline{\frac{W}{L} = 10}}$$

$$V_{DS} = 1.5V \quad V_{GS} = 2.5V \quad V_{GS} - V_t = 1.5V$$

$V_{DS} < V_{GS} - V_t$, so triode mode

$$i_D = k_n' \frac{W}{L} [(V_{GS} - V_t) V_{DS}] = 90 \mu A$$

Pinchoff when $V_{DS} = V_{GS} - V_t = 2.5V - 1V = 1.5V$

$$i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$i_D = 450 \mu A$$

5.15 $r_{DS} = \left[k_n' \frac{W}{L} (V_{GS} - V_{th}) \right]^{-1}$

For $V_{GS} = 1.1V$, $r_{DS} = \left[(20 \mu A/V^2) (100/5) (1.1V - 1V) \right]^{-1} = 25k\Omega$

For $V_{GS} = 11V$, $r_{DS} = \left[(20 \mu A/V^2) (100/5) (11V - 1V) \right]^{-1} = 250\Omega$

r_{DS} range: $25k\Omega \leftrightarrow 250\Omega$

(a) W is in the denominator of r_{DS} , so halving W doubles r_{DS}

r_{DS} range: $50k\Omega \leftrightarrow 500\Omega$


(b) L is in the numerator of r_{DS} , so halving L halves r_{DS}

r_{DS} range: $12.5k\Omega \leftrightarrow 125\Omega$

(c) W/L does not change so r_{DS} does not change

r_{DS} range: $25k\Omega \leftrightarrow 250\Omega$

8.

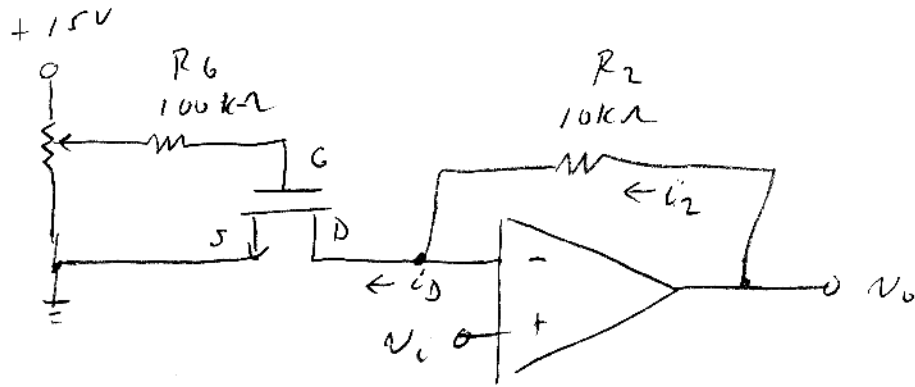

$$v_- = v_+ \Rightarrow v_- = v_i \quad \text{and} \quad i_2 = i_D$$

$$v_o = v_i + R_2 i_2 = v_i + R_2 i_D$$

$$v_o = v_i + R_2 k_n' \frac{W}{L} \left[(V_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

$$v_{DS} = v_D = v_- = v_i, \text{ so}$$

$$v_o = v_i + R_2 k_n' \frac{W}{L} \left[(V_{GS} - V_t) v_i - \frac{1}{2} v_i^2 \right]$$

For $v_i \ll (V_{GS} - V_t)$, can ignore $\frac{1}{2} v_i^2$


$$v_o = v_i + R_2 k_n' \frac{W}{L} (V_{GS} - V_t) v_i$$

$$\frac{v_o}{v_i} = 1 + R_2 k_n' \left(\frac{W}{L} \right) (V_{GS} - V_t)$$

$$= 1 + \frac{R_2}{r_{DS}}$$

v_{GS} is set by pot.

9.

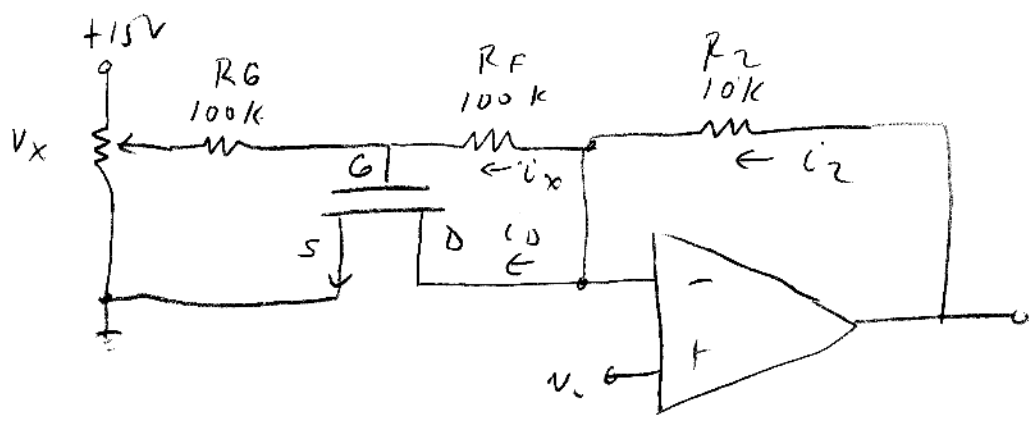

$$v_- = v_+ = v_i \quad i_z = i_D + i_x$$

v_x is set by pot

$$i_x = \frac{v_i - v_x}{200k}$$

$$i_D = \frac{v_i}{r_{os}} \quad r_{os} \text{ is a few } k\Omega, \text{ so } i_x \ll i_D$$

We will ignore i_x , so $i_z \approx i_D$

$$\text{Note that } V_{GS} = v_G = \frac{1}{2} v_x + \frac{1}{2} v_i$$

$$\begin{aligned} v_o &= v_i + i_D R_2 \\ &= v_i + k_n' \frac{W}{L} \left[(V_{GS} - V_t) v_i - \frac{1}{2} v_i^2 \right] R_2 \\ &= v_i + k_n' \frac{W}{L} \left[\left(\frac{1}{2} v_x + \frac{1}{2} v_i - V_t \right) v_i - \frac{1}{2} v_i^2 \right] R_2 \\ &= v_i + k_n' \frac{W}{L} \left[\left(\frac{1}{2} v_x - V_t \right) v_i \right] R_2 \end{aligned}$$

$$\frac{v_o}{v_i} = 1 + k_n' \frac{W}{L} \left(\frac{1}{2} v_x - V_t \right) R_2$$

and output is linear.

Note: v_x set by pot.

Note also: $v_{DS} = v_i$. If $v_{DS} > v_{GS} - V_t$, the MOSFET leaves the triode region and enters the saturation region. This circuit is linear only when $v_i < v_{GS} - V_t$.