


**EE 321**  
**Fall 2002**

**Homework #13**

**Solutions**

5.6.3

(a)

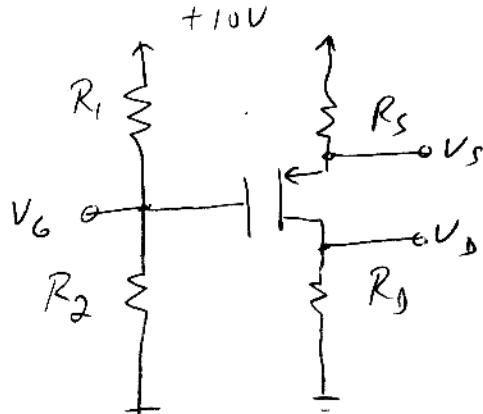Want  $10\mu A$  through $R_1 + R_2$ , so

$$R_1 + R_2 = \frac{10V}{10\mu A} = 1m\Omega$$

$$k_p' \frac{W}{L} = 0.5mA/V^2$$

$$V_T = -1V$$

Want  $I_D = 1mA$ 

$$V_D = 3V$$

$$V_D = I_D R_D \quad R_D = \frac{V_D}{I_D} = \frac{3V}{1mA} = 3k\Omega$$

$$I_D = \frac{1}{2} k_p' \frac{W}{L} (V_{GS} - V_T)^2$$

$$k_p' \frac{W}{L} = 0.5mA/V^2 \quad V_T = -1V$$

$$1mA = \frac{1}{2} (0.5mA/V^2) (V_{GS} - (-1V))^2$$

$$4V^2 = (V_{GS} + 1V)^2$$

$$V_{GS} = -3V \text{ or } +1V$$

For PMOS need  $V_{GS} < V_T$ , so  $V_{GS} = -3V$ 

$$\text{At triode, } V_{DS} = V_{GS} - V_T = -3V - (-1V) = -2V$$

To be 1V above triode, need  $V_{DS} = -3V$ 

$$V_S = V_D - V_{DS} = 3V - (-3V) = 6V$$

$$V_G = V_{GS} + V_S = -3V + 6V = 3V$$

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} \Rightarrow R_2 = \frac{V_G}{V_{DD}} (R_1 + R_2) = \frac{3V}{10V} 1m\Omega = 300k\Omega$$

$$V_S = V_{DD} - I_D R_S \Rightarrow R_S = \frac{V_{DD} - V_S}{I_D} = \frac{10V - 6V}{1mA} = 4k\Omega$$

$$\therefore R_1 = 300k \quad R_S = 4k\Omega$$

$$R_2 = 700k \quad R_D = 3k\Omega$$

$$(b) \text{ As in (a)} \quad R_1 + R_2 = 10 \text{ k}\Omega \quad R_D = 3 \text{ k}\Omega$$

$$I_D = \frac{1}{2} k_p \frac{w}{l} (V_{GS} - V_t)^2$$

$$|V_t| = 2V \Rightarrow V_t = +2V \quad (\text{Depletion P-MOS})$$

$$k_p \frac{w}{l} = 0.5 \text{ mA/V}^2$$

$$ImA = \frac{1}{2} (0.5 \text{ mA/V}^2) (V_{GS} - 2V)^2$$

$$4V^2 = (V_{GS} - 2V)^2$$

$$V_{GS} = 0V, 4V \quad \text{Now } V_{GS} < V_t, \text{ so } V_{GS} = 0V$$

$$\text{At triode, } V_{DS} = V_{GS} - V_t = 0 - 2V = -2V$$

$$\text{To be } 1V \text{ above triode need } V_{DS} = -3V$$

$$V_S = V_D - V_{DS} = 3V - (-3V) = 6V$$

$$V_S = I_{DD} - I_D R_S \Rightarrow R_S = \frac{V_{DD} - V_S}{I_D} = 4 \text{ k}\Omega$$


$$V_G = V_{GS} + V_S = 0 + 6V = 6V$$

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} \Rightarrow R_2 = \frac{V_G}{V_{DD}} (R_1 + R_2) = 600 \text{ k}\Omega$$

$$\therefore R_1 = 400 \text{ k}\Omega \quad R_S = 4 \text{ k}\Omega$$

$$R_2 = 600 \text{ k}\Omega \quad R_D = 3 \text{ k}\Omega$$

5.71

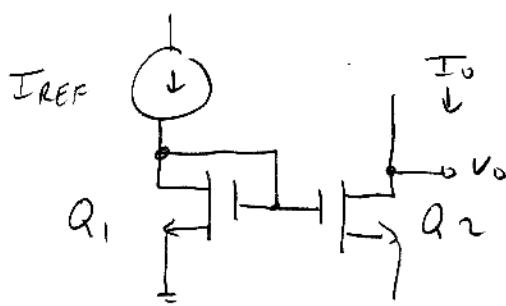

$$h_n' \frac{w}{l} = 40 \mu A/V^2$$

$$V_T = 0.8 V$$

$$V_A = 20 V$$

$$I_{REF} = 10 \mu A$$

$$I_{D1} = \frac{1}{2} h_n' \frac{w}{l} (V_{GS} - V_T)^2 = I_{REF}$$

$$10 \mu A = \frac{1}{2} (40 \mu A/V^2) (V_{GS} - 0.8 V)^2$$

$$\frac{1}{2} V^2 = (V_{GS} - 0.8 V)^2$$

$$V_{GS} = 0.8 V \pm \sqrt{\frac{1}{2} V^2} = 1.51 V, -0.93 V$$

$$\text{Need } V_{GS} > V_T \text{ so } V_{GS} = 1.51 V$$

$$\text{For } I_O = I_{REF} \text{ need } V_{DS2} = V_{DS1}$$

$$V_{D2} = V_{G2} \text{ so } V_{DS2} = 1.51 V \Rightarrow V_{DS1} = 1.51 V \Rightarrow V_{D2} = 1.51 V$$

$$V_0 = V_{D2} = 1.51 V$$


$$r_{o2} = \frac{V_A}{I_O} = \frac{20 V}{10 \mu A} = 2 m\Omega$$

$$\Delta V_{DS} = r_o \Delta i_D$$

$$\Delta i_D = \frac{\Delta V_{DS}}{r_o} = \frac{2 V}{2 m\Omega} = 1 \mu A$$

$I_O$  is  $11 \mu A$  when  $V_{DS}$  increases by  $2 V$

5.80

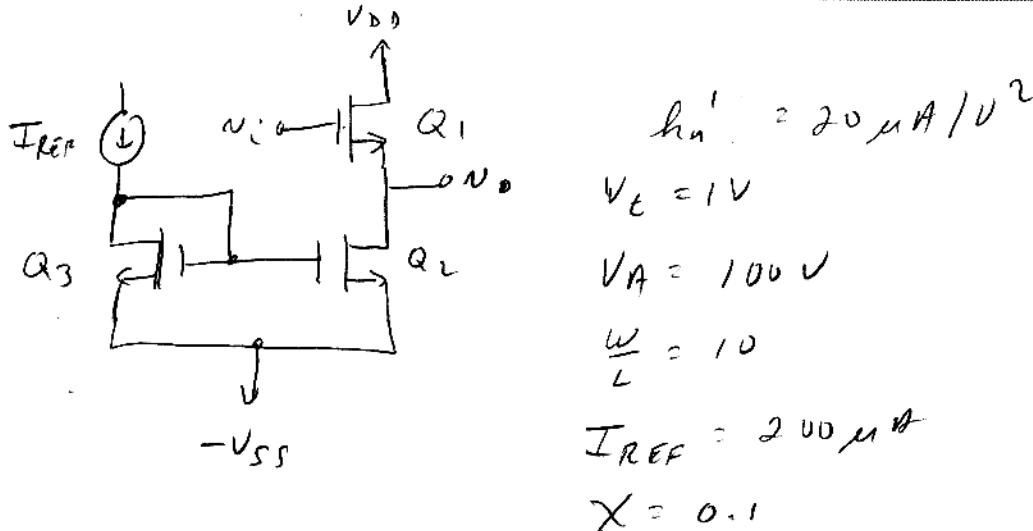

Because the transistors are identical,

$$I_{D2} : I_{D3} = 200 \mu A$$

$$I_{D1} = I_{D2} = 200 \mu A$$

$$g_{m1} = \sqrt{2h_n'} \sqrt{\frac{W}{L}} \sqrt{I_{D1}} = \sqrt{2(20 \mu A/V^2)(10)}(200 \mu A) \\ = 0.28 mA/V$$


$$r_{o1} = r_{o2} = \frac{V_A}{I_D} = \frac{100V}{200 \mu A} = 500 k\Omega$$

$$\begin{aligned} \text{eqn 5.70} \quad A_V &= \frac{g_{m1}}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} = \frac{g_{m1}}{g_{m1}(1+X) + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} \\ &= \frac{0.28 mA/V}{0.28 mA/V(1+0.1) + \frac{1}{500 k\Omega} + \frac{1}{500 k\Omega}} \\ &= 0.90 V/V \end{aligned}$$



eqn 5.73

$$R_o = \left(\frac{1}{g_{m1}}\right) || \left(\frac{1}{g_{mb1}}\right) || r_{o1} || r_{o2} = \frac{1}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$

$$= 3.2 k\Omega$$

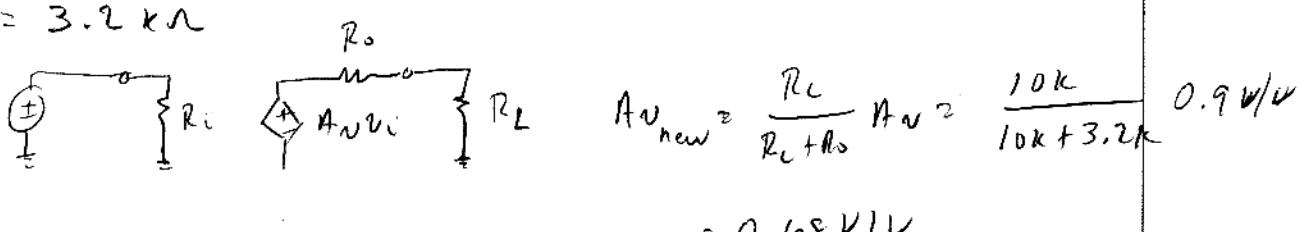


5.81

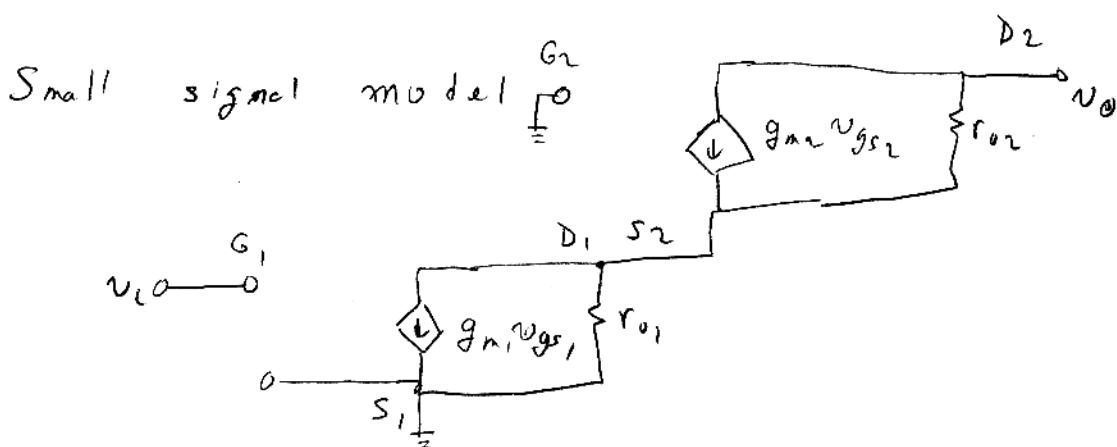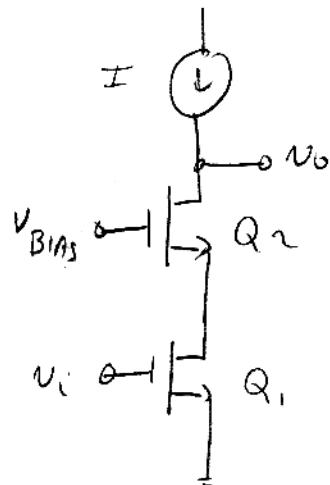


$$v_{gs1} = v_i \quad v_{gs2} = -v_{s1}$$

Redraw

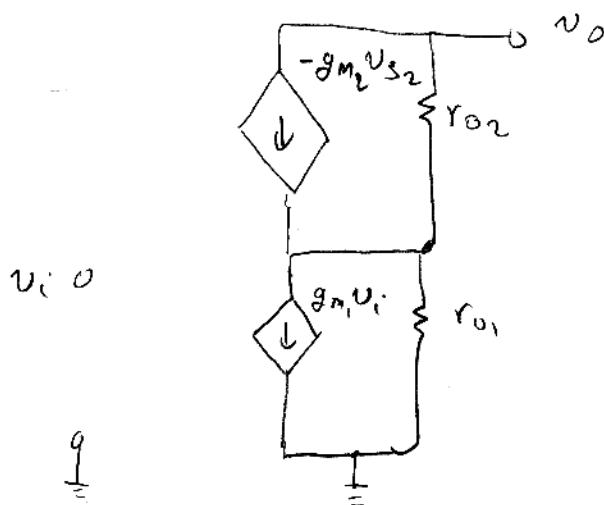

(a) Find short-circuit output current

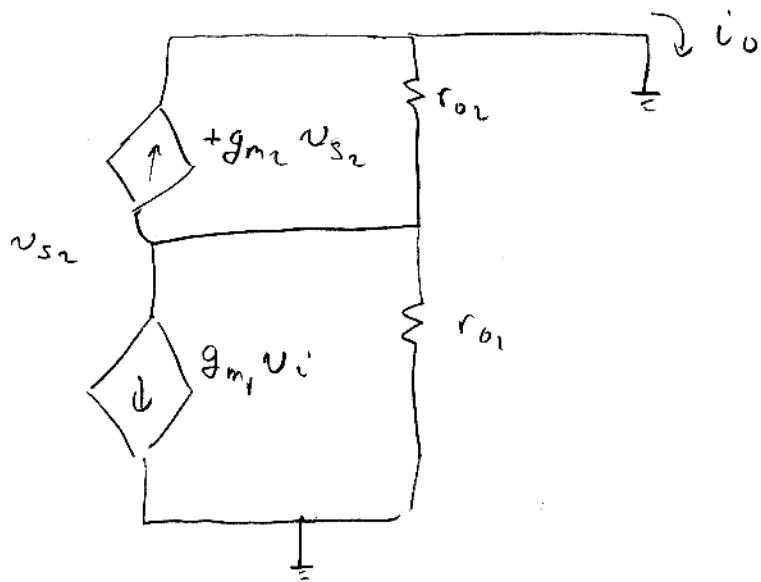

Node eqn at  $S_2$ :

$$g_{m1} v_i + g_{m2} v_{S2} + \frac{v_{S2}}{r_{o1}} + \frac{v_{S2}}{r_{o2}} = 0$$

$$v_{S2} = -\frac{g_{m1}}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} v_i$$

$$i_o = g_{m2} v_{S2} + \frac{v_{S2}}{r_{o2}}$$


$$= \frac{-g_{m1} \left( g_{m2} + \frac{1}{r_{o2}} \right)}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} v_i$$

$$\approx -g_{m1} v_i \quad (\text{for large } r_{o1}, r_{o2})$$

$$\frac{i_o}{v_i} \approx -g_{m1}$$

(b) With  $v_i$  shorted,  $v_i = 0 \Rightarrow g_m, v_i = 0$

Model becomes

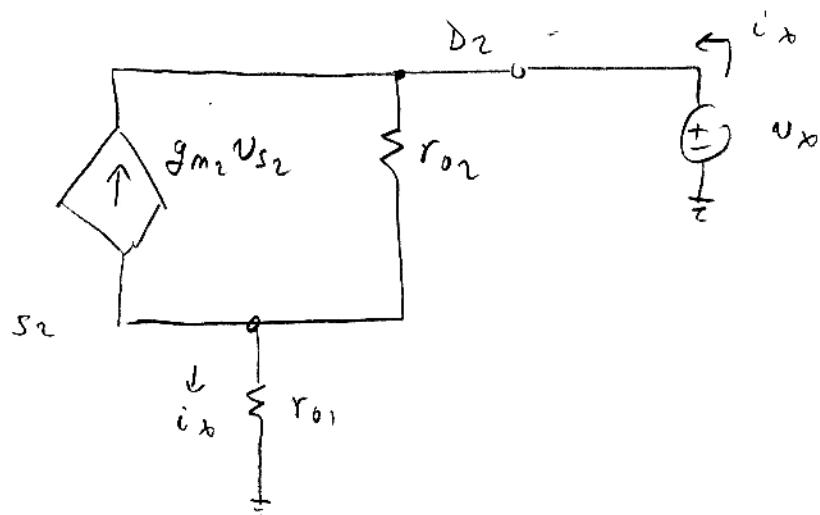

Node eqn at  $D_2$ :


$$i_x + g_{m2} v_{s2} + \frac{v_{s2} - v_x}{r_{o2}} = 0$$

$$\text{Also, } v_{s2} = i_x r_{o1}, \text{ so}$$

$$i_x + g_{m2} i_x r_{o1} + \frac{i_x r_{o1} - v_x}{r_{o2}} = 0$$

$$i_x \left( 1 + g_{m2} r_{o1} + \frac{r_{o1}}{r_{o2}} \right) = \frac{v_x}{r_{o2}}$$

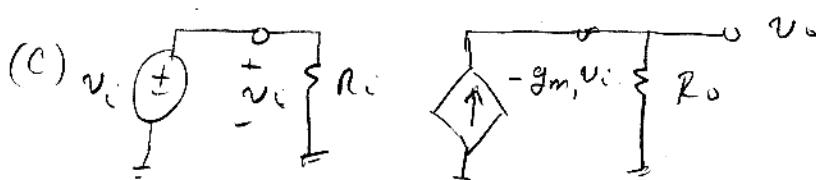
$$R_o = \frac{v_x}{i_x} = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2} \approx g_{m2} r_{o1} r_{o2}$$



$$v_o = -g_m R_o v_i \approx -g_m g_{m2} r_{o1} r_{o2} v_i$$

$$A_{v_o} \approx -g_m g_{m2} r_{o1} r_{o2}$$

5.84

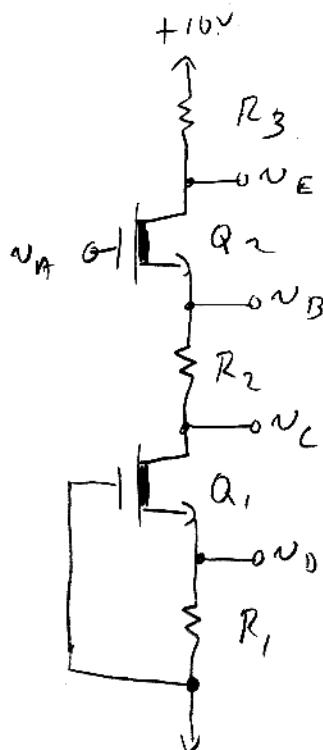

$$I_{DSS} = 4 \text{ mA}$$

$$|V_t| = 2 \text{ V} \Rightarrow V_t = -2 \text{ V} \quad (\text{Depletion NMOS})$$

$$I_{DSR} = \frac{1}{2} k_n \frac{W}{L} V_t^2$$

$$k_n \frac{W}{L} = \frac{2 I_{DSS}}{V_t^2} = \frac{2(4 \text{ mA})}{(-2 \text{ V})^2} = 2 \text{ mA/V}^2$$

$$I_D = \frac{1}{2} k_n \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$

$$1 \text{ mA} = \frac{1}{2} (2 \text{ mA/V}^2) (V_{GS} - (-2 \text{ V}))^2$$

$$1 \text{ V}^2 = (V_{GS} + 2 \text{ V})^2$$

$$V_{GS} = -1 \text{ V} \text{ or } -3 \text{ V}$$

$$\text{Need } V_{GS} > V_t, \text{ so } V_{GS} = -1 \text{ V}$$

$\therefore 1 \text{ V drop across } R_1$

$$R_1 = \frac{V_1}{I_D} = \frac{1 \text{ V}}{1 \text{ mA}} = 1 \text{ k}\Omega$$

$$R_2 = R_1 = 1 \text{ k}\Omega$$

$$V_E = V_{DD} - R_3 I_D \Rightarrow R_3 = \frac{10 \text{ V} - 6 \text{ V}}{1 \text{ mA}} = 4 \text{ k}\Omega$$

Because the transistors are equal, and have equal  $I_D$ ,

$$V_{GS2} = V_{GS1} = -1 \text{ V}$$

$$V_{GS2} = V_{G2} - V_{S2} = V_A - V_{S2} \Rightarrow V_{S2} = V_A - V_{GS2} = 0 - (-1 \text{ V}) = 1 \text{ V}$$

$$V_B = V_{S2} = 1 \text{ V}$$

$$V_C = V_B - R_2 I_D = 1 \text{ V} - (1 \text{ k})(1 \text{ mA}) = 0 \text{ V}$$

Note that  $V_{S2} = V_A - V_{GS2} = V_A + 1V$ ,  $V_B = V_{S2} = V_A + 1V$

$$V_C = V_B - I_D R_1 = V_A + 1V - (1mA)(1k\Omega) = V_A$$

$V_C = V_A$  as long as both transistors remain in saturation

$Q_2$  enters triode when

$$V_{DS2} = V_{GS2} - V_t = -1V - (-2V) = 1V$$

$$V_{D2} = V_E = 6V$$

$$\begin{aligned} V_A &= V_{S2} + V_{GS2} = V_{D2} - V_{DS2} + V_{GS2} \\ &= 6V - 1V - 1V = 4V \end{aligned}$$

$Q_1$  enters triode when

$$V_{DS1} = V_{GS1} - V_t = -1V - (-2V) = 1V$$

$$\begin{aligned} V_A &= V_{Dc} = V_{D1} = V_{DS1} + V_{S1} = V_{DS1} + I_D R_1 - 10V \\ &= 1V + (1mA)(1k\Omega) - 10V \\ &= -8V \end{aligned}$$

Circuit works as a follower with unity gain and no offset for  $-8V < V_A < 4V$