EE 352 Fall 2001


## **EE 352**

## Homework #4

Due September 28, 2001

Draw a schematic for your bi-directional parallel port:

## Bi-Directional Parallel Port

 


Use an Altera EPM7128 for your circuit. Show how to connect the pins of the EPM7128 to the 8-bit ISA bus and the 25-pin parallel port connector. Use the following pinout for the parallel port connector (your port will connect to the side labeled TEST):

EE 352 Fall 2001

STA	NDARD		TEST	
STB	C0	O 1	ິ 56	ACK
	D0	O 2	<b>D0</b>	
	D1	O 3	<b>D1</b>	
	D2	O 4	D2	
	D3	O <u>5</u>	<b>D3</b>	
	D4	6	D4	
	D5	7	) D5	
	D6	8	D6	
	D7	9	D7	
ACK	<b>S6</b>	<u> </u>	C0	STB
BSY	s7	<u> </u>		INI
PAP	<b>S</b> 5	<u>12</u>		ALF
ONOF	_	<u>13</u>	C3	DSL
ALF	C1	O 14	์ 55	PAP
ERR	<b>s</b> 3	15	) <b>53</b>	ERR
INI	C2	<u> </u>	) <b>s7</b>	BSY
DSL	C3	<u> </u>	) <b>54</b>	ONOF
	GND	<u>18</u>	GND	
	GND	19	GND	
	GND	<u>20</u>	GND	
	GND	<u>21</u>	GND	
	GND	22	GND	
	GND	<u>23</u>	GND	
	GND	24	GND	
	GND	<u>25</u>	GND	

The following is not due next week, but you need to start thinking about it:

 Start working on a program to transfer data from a PC with a regular parallel port to a PC using your bi-directional parallel port (with the data lines set up for input). Use a handshaking scheme like the one below:



You will have two programs: one running on the sending PC and one running on the receiving PC. You should start the program on the receiving PC, connect the cable, then start the program on the sending PC. The program on the sending PC should take a file name you specify, and send that file to the receiving PC. The program on the receiving PC should save the file from the sender with the same name.