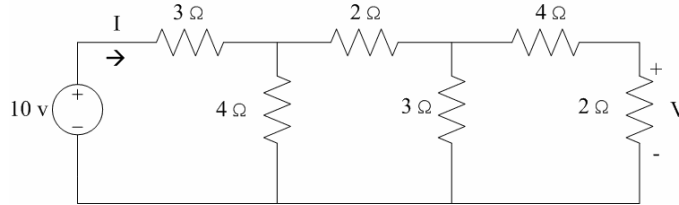



All the normal rules apply: Due next class, work on separate paper, start early, show your work, label everything, specify units, circle answers.

**For all these problems, keeping your work in fractions will produce easier, more accurate results!**


1. For the figure below, find  $I$  and  $V$  using circuit reduction and other techniques.



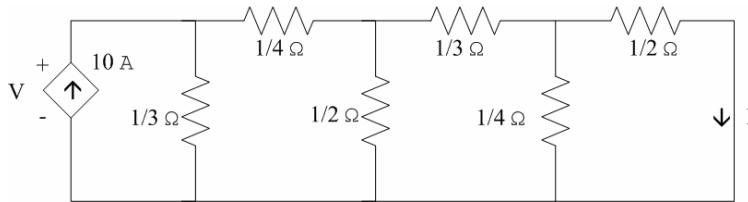
2. For the figure below, find  $V$  and  $I$  using circuit reduction and other techniques.



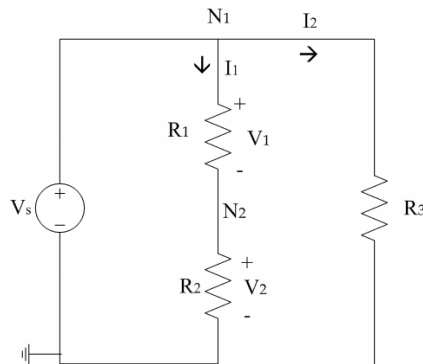
3. In the figure below,  $V_s = 5\text{ v}$ ,  $R_1 = 375\ \Omega$ ,  $R_3 = 25\ \Omega$ . With a multimeter we measure  $1.25\text{ v}$  at  $N_2$  with respect to ground. Find the voltage at  $N_1$  (w.r.t. Gnd),  $R_2$ ,  $V_1$ ,  $I_1$ , and  $I_2$  using nodal analysis and other techniques.



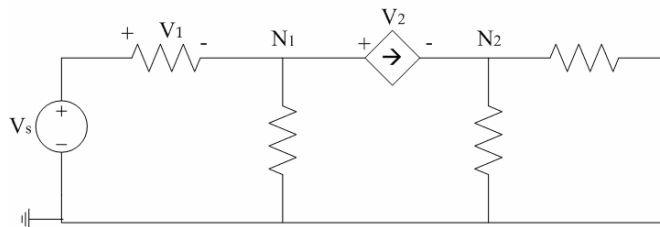
4. In the figure below,  $V_s = 10\text{ v}$ . With a multimeter we measure (w.r.t. Gnd)  $4\text{ v}$  at  $N_1$  and  $7\text{ v}$  at  $N_2$ . Find  $V_1$  and  $V_2$ .



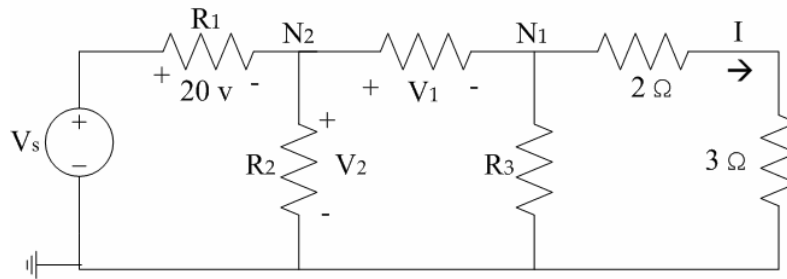
5. In the figure below,  $I = 8 \text{ A}$ . With a multimeter we measure (w.r.t. Gnd)  $60 \text{ v}$  at  $N_2$ . Using nodal analysis and other techniques, find  $V_s$ ,  $V_1$ ,  $V_2$ , and the measurement we would expect to get at  $N_1$  (w.r.t. Gnd).



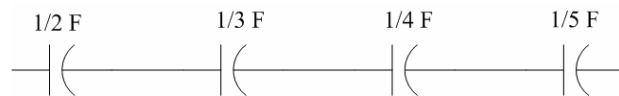
6. The figure below shows a number of capacitors connected in series. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ .



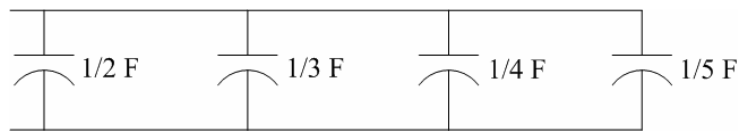7. The figure below shows a number of capacitors connected in parallel. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ .



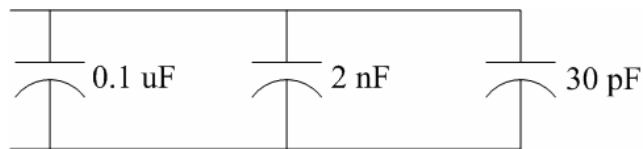8. The figure below shows a number of capacitors connected in parallel. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ . *Do not Round off your answer.*



9. The figure below shows a number of capacitors connected in series. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ .

