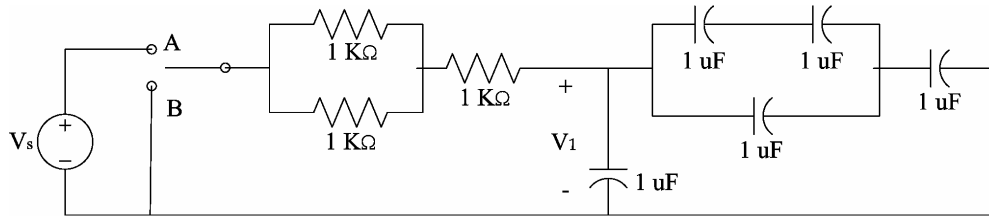


*All the normal rules apply: Due next class, work on separate paper, start early, show your work, label everything (especially on graphs -including axes, time/voltage divisions, function plots, values, etc.), specify units, circle answers.*

**Watch your units!**


1. For the figure below:



- Simplify the circuit and find the time constant  $\tau$ . Hint:  $\tau = R_{eq} \cdot C_{eq}$
  - Plot the charge and discharge curves for  $V_1$  using the 2/3 estimation method shown in class using at least four points. Your plot should go out to at least  $t = 4\tau$ . To plot the charge curve, assume the switch has been in position B for a long time and switches to position A at  $t = 0$ . For the discharge curve, assume that the switch has been at A for a long time, and switches to B at  $t = 0$ .
  - Assume  $V_s = 10$  v. Plot the charge and discharge curves for  $V_1$  using the exponential formula used in class. Your plot should go out to at least  $t = 4\tau$  using at least four points.
2. For the circuit below, assume  $V_s = 5$  v and  $R$  is unknown. In the lab we observe the charge curve for this circuit on an oscilloscope. We measure the following:


$$V_C = 0.5\text{v when } t = 50 \text{ us}$$
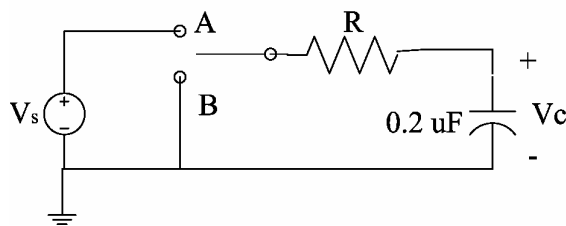
$$V_C = 4.5\text{v when } t = 1150 \text{ us.}$$



- Using the 10% - 90% rise time rule of thumb, calculate the time constant  $\tau$  for this circuit.
- Using your results from part a, determine the value of  $R$ .
- Assume the switch has been in position A for a long time and switches to B at  $t = 0$ . Plot  $V_C$  for  $0 < t < 4\tau$  using at least four points. Show all your work! Be sure to plot and confirm that your 10% values and 90% values match those used earlier. (Remember that the rule of thumb for the earlier calculation is an approximation).
- Assume the switch has been in position B for a long time and switches to A at  $t = 0$ . Plot  $V_C$  for  $0 < t < 4\tau$  using at least four points. Show all your work! Be sure to plot and confirm that your 10% values and 90% values match those used earlier. (Remember that the rule of thumb for the earlier calculation is an approximation).

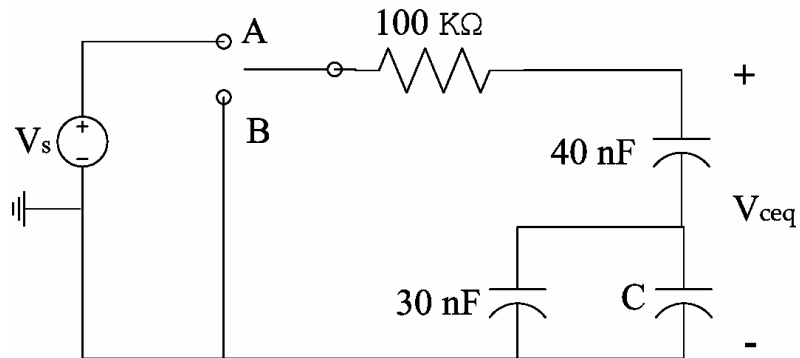3. For the figure below:  $\tau = 2 \text{ ms}$ ,  $V_s = 15 \text{ v}$ .



- Determine the value of C.
- Assume the switch has been in position A for a long time and switches to B at  $t = 0$ . Plot  $V_{ceq}$  for  $0 < t < 4\tau$  using at least four points. Show all your work!
- Assume the switch has been in position B for a long time and switches to A at  $t = 0$ . Plot  $V_{ceq}$  for  $0 < t < 4\tau$  using at least four points. Show all your work!