
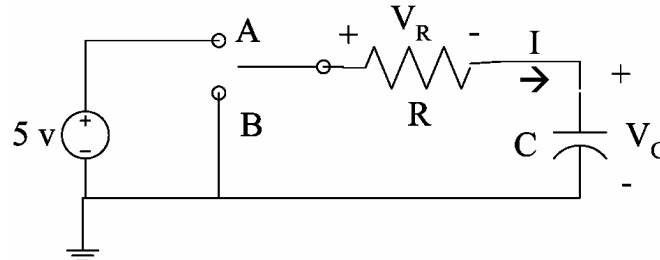


All the normal rules apply: Due next class, work on separate paper, start early, show your work, label everything (especially on graphs -including axes, time/voltage divisions, function plots, etc.), specify units, circle answers.

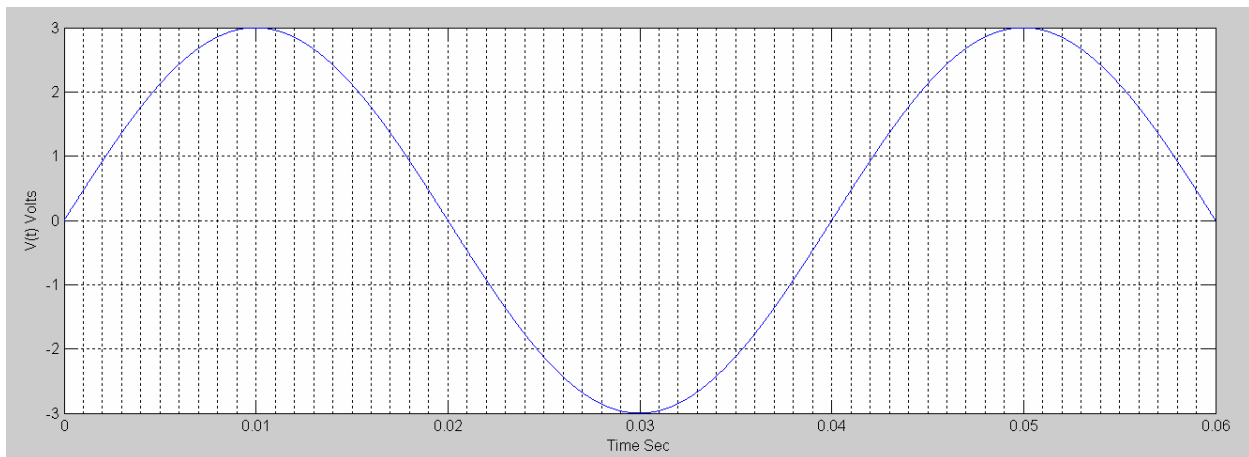The following diagram applies to problems 1 and 2 (do not reuse data between problems).




1. In a simple RC circuit shown in the diagram above, the switch has been in position B for a long time and switches to A at $t = 0$. We observe a capacitor charging with the standard exponential growth curve. At $t = 37.5 \text{ ms}$ we measure the resistor voltage V_R is 1.115 v . Determine the time constant τ for the circuit.
2. For the diagram above, we determine that the time constant τ is 7.00 us . We assume that the switch has been in position A for a long time and moves to position B at $t = 0$. At a particular time after the switch has moved to position B, we observe that $I = -9.1 \text{ mA}$, and $V_C = 0.725 \text{ v}$.
 - a. Determine what time these observations occur.
 - b. Solve for the capacitor value C.



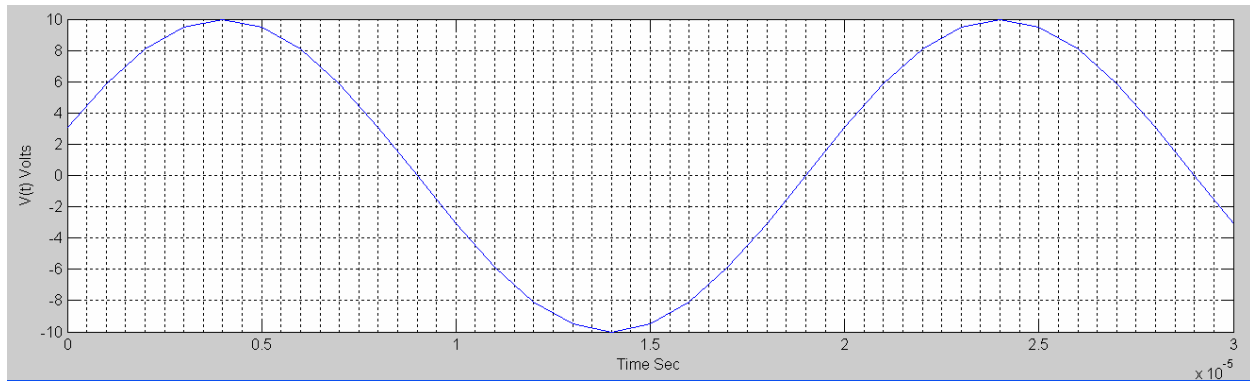3. For the figure above, find the indicated values and express the function $v(t)$ in equation form:

Find: Peak voltage V_p , peak-to-peak voltage V_{pp} , RMS voltage V_{rms} , Period T, frequency f, angular frequency ω , time shift t_{max} , and phase angle Θ .



4. For the figure above, find the indicated values and express the function $v(t)$ in equation form (*be careful to note that the units for time on this graph are in 10^{-5} seconds*).

Find: Peak voltage V_p , peak-to-peak voltage V_{pp} , RMS voltage V_{rms} , Period T , frequency f , angular frequency ω , time shift t_{max} , and phase angle Θ .

5. For the equation below, find V_p , V_{pp} , V_{rms} , T , f , ω , t_{max} , Θ ; and graph the function for $0 < t < 5/16$ seconds. Remember to label you axes, units, and all relevant points on the graph. *Hint: Try to keep your time divisions in terms of fractions rather than decimals, this will be easier to graph. This entire problem is easier without a calculator if you use fractions!*

$$v(t) = 25\cos(8\pi t - 30^\circ) \text{ volts}$$