

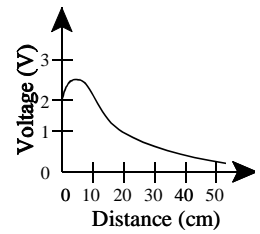
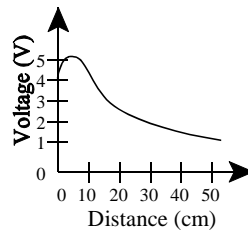
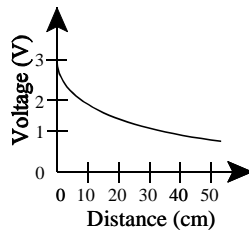


### QUIZ 3

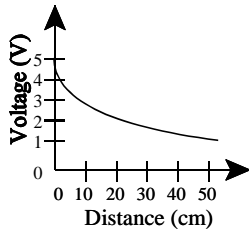
1. How does the microcontroller “understand” the Sharp GP2D12's output voltage?
2. Which of the following graphs most correctly shows the Sharp GP2D12's output voltage versus distance?



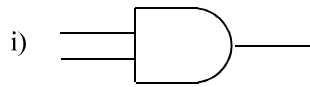
3. Construct a digital circuit that implements the following boolean equation.  
$$F = A\bar{B} + \bar{A}B$$
4. Match the following digital logic gates with their names.




a) NAND

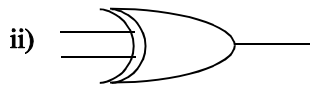


b) Inverter

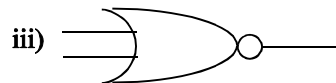

c) XOR

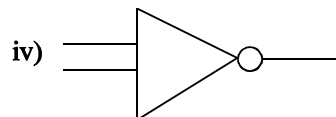

d) AND

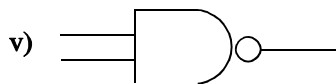

e) NOR

