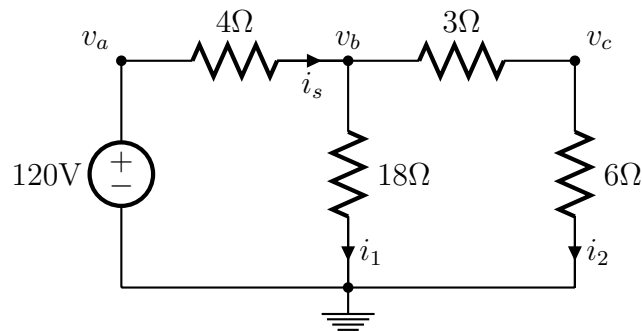
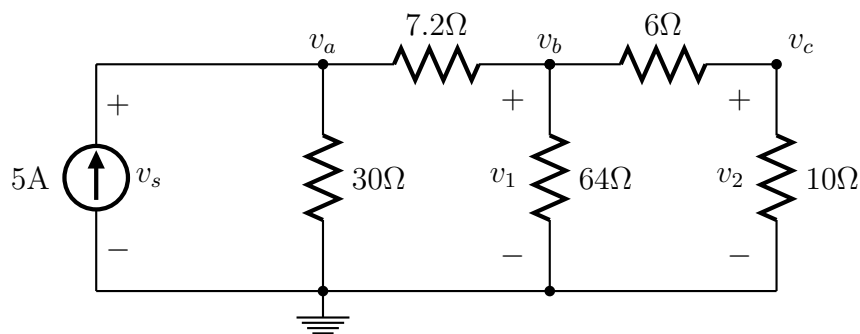


- Homework is due at the beginning of class
  - Start early and get help if you need it
  - Show all work neatly and clearly; redraw and/or rewrite problem if needed as work turned in should stand alone
  - Identify your answers (with units) using a box, circle or underline
  - Staple multiple pages together
1. Consider the circuit shown below with currents, node-voltages, and a reference labeled.



- Use series and parallel simplifications to find the currents  $i_s$ ,  $i_1$ , and  $i_2$  as labeled.
  - Calculate the power consumed by all elements (denote as  $p_{120V}$ ,  $p_{4\Omega}$ ,  $p_{18\Omega}$ ,  $p_{3\Omega}$ ,  $p_{6\Omega}$ ) in the circuit and confirm they sum to zero.
  - Determine the node-voltages  $v_a$ ,  $v_b$ , and  $v_c$  as labeled.
  - Show how an ammeter should be connected to measure the current  $i_1$ .
  - Show how an ohmmeter should be connected to measure the equivalent resistance connected to the voltage source.
2. Consider the circuit shown below with voltages, node-voltages and a reference labeled.



- Use series and parallel simplifications to find the voltages  $v_s$ ,  $v_1$ , and  $v_2$  as labeled.
- Calculate the power consumed by all elements (denote as  $p_{5A}$ ,  $p_{30\Omega}$ ,  $p_{7.2\Omega}$ ,  $p_{64\Omega}$ ,  $p_{6\Omega}$ ,  $p_{10\Omega}$ ) in the circuit and confirm they sum to zero.
- Determine the node-voltages  $v_a$ ,  $v_b$ , and  $v_c$  as labeled.
- Show how a voltmeter should be connected to measure the voltage  $v_1$ .
- Show how an ohmmeter should be connected to measure the resistance of only the 64Ω resistor.

3. The circuit shown below contains a 24V source and three lamps. The lamps are denoted by  $A$ ,  $B$ , and  $C$ , and are rated to consume  $p_A = 10\text{W}$ ,  $p_B = 15\text{W}$ , and  $p_C = 20\text{W}$  of power, respectively. If the voltage source consumes  $-30\text{W}$  of power, which lamp has burned out?

