
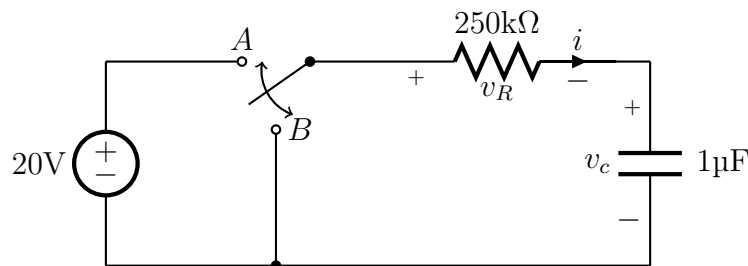


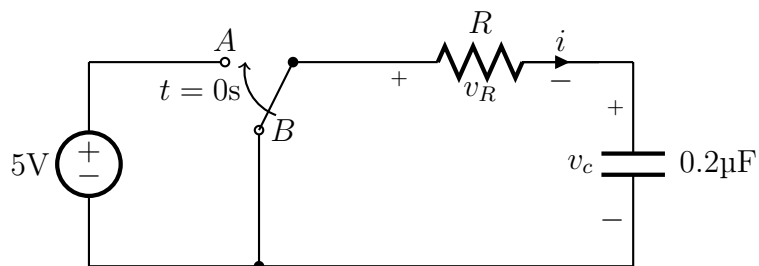- Homework is due at the beginning of class
 - Start early and get help if you need it
 - Show all work neatly and clearly; redraw and/or rewrite problem if needed as work turned in should stand alone
 - Identify your answers (with units) using a box, circle or underline
 - Staple multiple pages together
1. Consider the RC circuit shown below with a switch that moves between positions A and B .




- (a) Assume the switch has been connected to position B for a long time before it moves to position A at time $t = 0\text{s}$. For this “charging” circuit:
- Determine the time-constant, τ .
 - Using the time-constant, estimate the 10%-90% rise-time, t_r .
 - Write the mathematical expression for the capacitor’s voltage, v_c .
 - Sketch v_c versus time using values at multiples of the time-constant as a guide (use at least five points).
 - Label the rise-time on the sketch of v_c and check that your estimate of its value appears correct.
 - Find the mathematical expression for the resistor’s voltage, v_R .
 - Find the mathematical expression for the current, i .
 - Sketch i versus time using values at multiples of the time-constant as a guide (use at least five points).
- (b) Assume the switch has been connected to position A for a long time before it moves to position B at time $t = 0\text{s}$. For this “discharging” circuit:
- Write the mathematical expression for the capacitor’s voltage, v_c .
 - Sketch v_c versus time using values at multiples of the time-constant as a guide (use at least five points).
 - Find the mathematical expression for the resistor’s voltage, v_R .
 - Find the mathematical expression for the current, i .
 - Sketch i versus time using values at multiples of the time-constant as a guide (use at least five points).

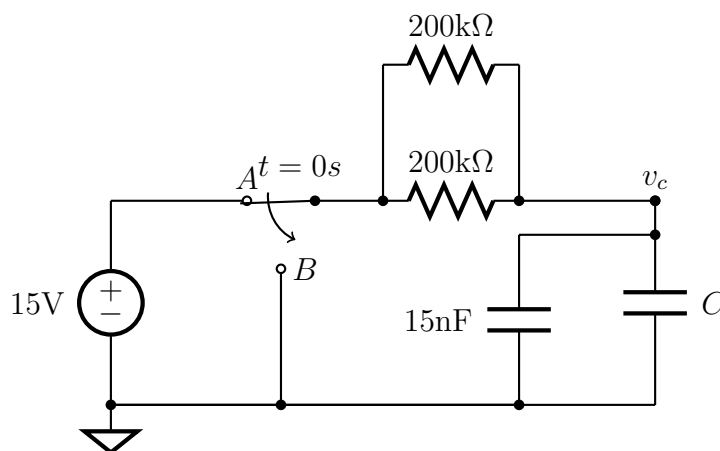2. Consider the RC circuit shown below with a switch that moves from position B to A at time $t = 0\text{s}$, i.e., this is a “charging” circuit.



Given $v_c = 0.5\text{V}$ at time $t = 0.5\text{ms}$ and $v_c = 4.5\text{V}$ at time $t = 11.5\text{ms}$, find the following:


- 10%-90% rise-time, t_r , of the circuit,
 - time-constant, τ , of the circuit,
 - value of the unknown resistor, R ,
 - mathematical expression for the capacitor's voltage, v_c ,
 - sketch of v_c versus time using values at multiples of the time-constant as a guide (use at least five points), and
 - label rise-time on the sketch.
3. Consider the RC circuit shown below with a switch that moves from position A (after being there for a long time) to position B at time $t = 0\text{s}$, i.e., this is a “discharging” circuit.



Given the circuit's time constant is $\tau = 2\text{ms}$ find the following:

- value of the capacitor, C ,
- mathematical expression for the voltage, v_c , and
- sketch of v_c versus time using values at multiples of the time-constant as a guide (use at least five points).

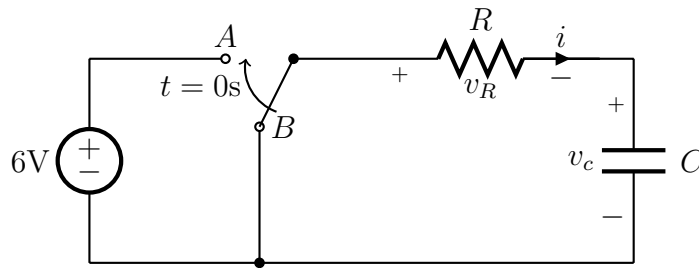4. Consider the RC circuit shown below with a switch that moves from position B (after being there a long time) to position A at time $t = 0$ s. Given that at time $t = 330\mu\text{s}$ the resistor's voltage is $v_R = 2\text{V}$, determine the time constant, τ , for the circuit.



5. Consider the RC circuit shown below with a switch that moves from position A (after being there for a long time) to position B at time $t = 0$ s. Given the circuit's time constant is $\tau = 7.5\mu\text{s}$ and at a particular time after the switch has moved the current is measured to be $i = -240\mu\text{A}$, find the time at which the measurement was taken.

