
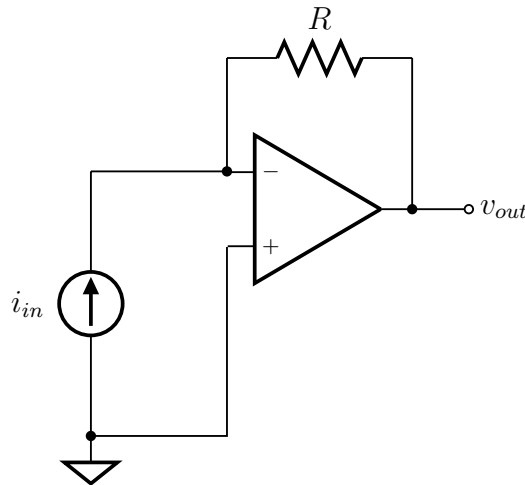


- Homework is due at the beginning of class
 - Start early and get help if you need it
 - Show all work neatly and clearly; redraw and/or rewrite problem if needed as work turned in should stand alone
 - Identify your answers (with units) using a box or circle
 - Staple multiple pages together
1. The circuit shown below is known as a transimpedance amplifier or current-to-voltage converter. Using ideal assumptions about the op-amp's behavior, solve for the following:
- (a) output voltage v_{out} in terms of R and i_{in} ,
 - (b) gain $\frac{v_{out}}{i_{in}}$ in terms of R , and
 - (c) largest magnitude of input current, $|i_{in}|$, that can be applied before the output saturates assuming supply voltages of $\pm V_S = \pm 12\text{V}$ and resistor $R = 1.2\text{k}\Omega$.

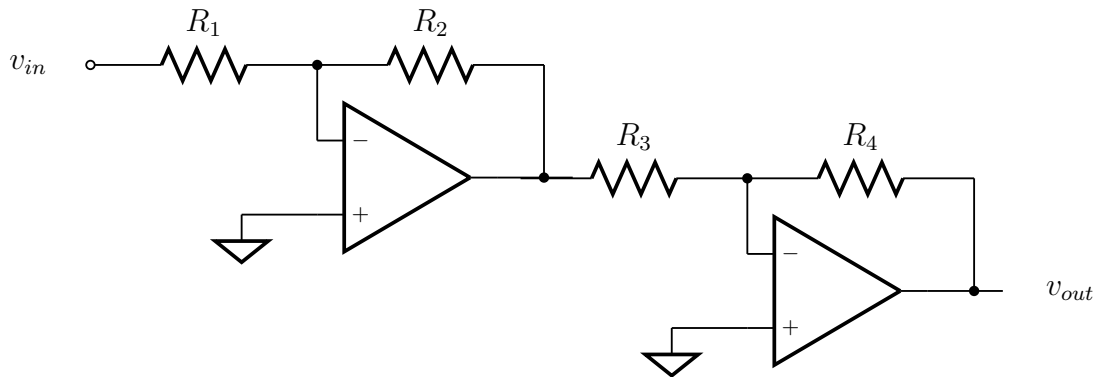

2. Consider the noninverting amplifier shown in Figure 8.12 on page 641, and use ideal assumptions about the op-amp's behavior in your analysis. Solve for the following:
- (a) output voltage V_{out} and gain $\frac{V_{out}}{V_{in}}$ in terms of resistors R_1 , R_2 ,
 - (b) output voltage V_{out} and gain $\frac{V_{out}}{V_{in}}$ using specific values given for resistors R_1 , R_2 , and
 - (c) largest magnitude of input voltage, $|V_{in}|$, that can be applied before the output saturates assuming supply voltages of $\pm V_S = \pm 15\text{V}$ and specified values for resistors.

3. Given the circuit shown and ideal assumptions about the op-amp's behavior, solve for the circuit's output voltage v_{out} and gain $\frac{v_{out}}{v_{in}}$.



4. An input signal that ranges between 0V and 50mV needs to be amplified to the range 0V and 5V.
- (a) What gain is needed to perform the desired amplification?
 - (b) Given you have op-amps and resistors of values $1\text{k}\Omega$, $9.9\text{k}\Omega$, $10\text{k}\Omega$, $99\text{k}\Omega$ and $100\text{k}\Omega$ design an op-amp-based circuit that can perform this amplification. Note some of the circuits you analyzed above may make good options.