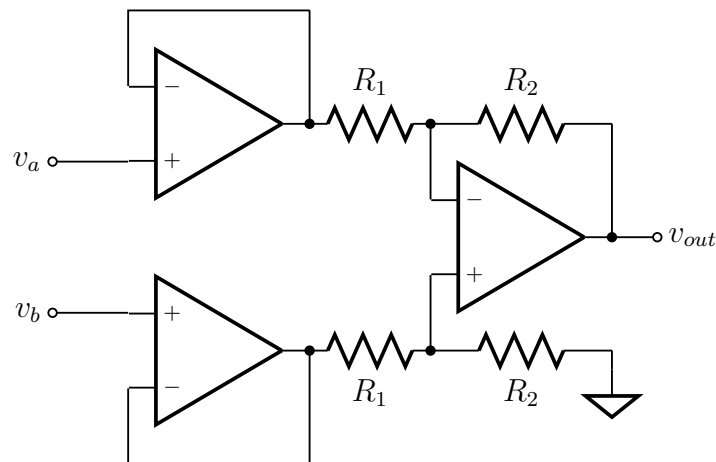


- Homework is due at the beginning of class
 - Start early and get help if you need it
 - Show all work neatly and clearly; redraw and/or rewrite problem if needed as work turned in should stand alone
 - Identify your answers (with units) using a box or circle
 - Staple multiple pages together
1. Using ideal assumptions for the op-amp, solve for the output voltage V_{out} in the two-input summing amplifier circuit shown at the top of page 642 of the book.
 2. Using ideal assumptions for the op-amps, solve for the output voltage V_{out} in the three-input summing amplifier circuit shown in Figure 8.13 on page 642 of the book.
 3. Consider the circuit shown below which is a basic instrumentation amplifier. Make ideal assumptions about the op-amps' behaviors and solve for the output voltage v_{out} .



4. Convert the following binary numbers to their decimal equivalent.
 - (a) $(110011)_2$
 - (b) $(10010100)_2$
5. Add $(101101)_2$ to $(101110)_2$ and give the answer in binary.