

- Homework is due at the beginning of class
 - Start early and get help if you need it
 - Show all work neatly and clearly; redraw and/or rewrite problem if needed as work turned in should stand alone
 - Identify your answers (with units) using a box or circle
 - Staple multiple pages together
1. Convert the following decimal numbers to their binary equivalent.
 - (a) $(111)_{10}$
 - (b) $(232)_{10}$
 2. Consider the table that counts up corresponding values of 4-bit binary numbers, octal numbers, decimal numbers and hexadecimal numbers.
 - (a) What are the octal, hexadecimal and binary equivalents of $(11)_{10}$?
 - (b) What are the octal, decimal and hexadecimal equivalents of $(0100)_2$?
 3. Consider the Boolean expression $Y = \bar{A}\bar{C} + \bar{B}C + AC$ where Y is the output and the three inputs are A, B, C .
 - (a) Use inverters and two-input AND and OR logic gates to construct the logic circuit that realizes the Boolean expression.
 - (b) Write the truth table that results from the Boolean expression.
 4. Consider the truth table given below for a two-bit adder with two inputs A, B and two outputs C, S .

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- (a) Find logical expressions for outputs C and S in the form of a sum-of-products (SOP), and
- (b) use inverters and two-input AND and OR logic gates to construct logic circuits that realize C and S .

5. Write a Boolean, sum-of-products (SOP) expression for the output Y in terms of inputs A, B, C, D for the following truth table.

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

6. Using the logic circuit shown below, find the Boolean expression for the output Y in terms of the four inputs A, B, C, D.

