

1. Problem 5.22 (apply method we've used on second order differential equations to solve the first order differential equation)
2. Problem 6.29
3. Problem 6.35
4. Find $v(t)$ in the following circuit for all t .

