

4.7 Connect a $5\text{-}\Omega$ resistor in parallel with the inductor in the circuit shown in Fig. P4.6. Suppose that $v_s(t) = 13 \cos(2t - 22.6^\circ) \text{ V}$. Find the voltage $v_o(t)$ across the inductor by using voltage division. Draw a phasor diagram. Is this circuit a lag network or a lead network?

4.8 Connect a $5\text{-}\Omega$ resistor in parallel with the inductor in the circuit shown in Fig. P4.6. Suppose that $v_s(t) = 13 \cos(2t - 22.6^\circ) \text{ V}$. Find the voltage $v_o(t)$ across the inductor by using nodal analysis. Draw a phasor diagram. Is this circuit a lag network or a lead network?

4.9 For the circuit given in Fig. P4.9, suppose that $i_s(t) = 5 \cos 3t \text{ A}$. Find $v_o(t)$ and $v_s(t)$ by using current division.

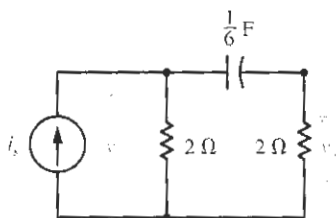


Fig. P4.9

4.10 For the circuit given in Fig. P4.9, suppose that $i_s(t) = 5 \cos 3t \text{ A}$. Find $v_o(t)$ and $v_s(t)$ by using nodal analysis.

4.11 A voltage of $v_s(t) = 10 \cos \omega t \text{ V}$ is applied to a series RLC circuit. If $R = 5 \text{ }\Omega$, $L = \frac{1}{5} \text{ H}$, and $C = \frac{1}{5} \text{ F}$, by how many degrees does $v_C(t)$ lead or lag $v_s(t)$ when (a) $\omega = 1 \text{ rad/s}$, (b) $\omega = 5 \text{ rad/s}$, and (c) $\omega = 10 \text{ rad/s}$?

4.12 A voltage of $v_s(t) = 10 \cos \omega t \text{ V}$ is applied to a series RLC circuit. If $R = 5 \text{ }\Omega$, $L = \frac{1}{5} \text{ H}$, and $C = \frac{1}{5} \text{ F}$, by how many degrees does $v_R(t)$ lead or lag $v_s(t)$ when (a) $\omega = 1 \text{ rad/s}$, (b) $\omega = 5 \text{ rad/s}$, and (c) $\omega = 10 \text{ rad/s}$?

4.13 For the RLC connection given in Fig. P4.13, find the impedance Z when ω is (a) 2, (b) 4, and (c) 8 rad/s.

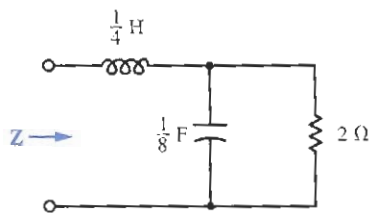


Fig. P4.13

4.14 For the RLC connection shown in Fig. P4.14, find the admittance Y when ω is: (a) 1, (b) 3, and (c) 7 rad/s.

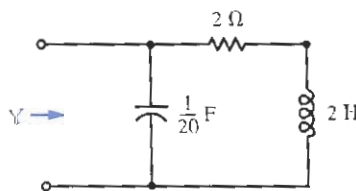


Fig. P4.14

4.15 Show that a general expression for the impedance Z depicted in Fig. P4.13 is

$$Z = \frac{32}{\omega^2 + 16} + j \frac{\omega(\omega^2 - 16)}{4(\omega^2 + 16)}$$

4.16 Show that a general expression for the admittance Y depicted in Fig. P4.14 is

$$Y = \frac{1}{2(\omega^2 + 1)} + j \frac{\omega(\omega^2 - 9)}{20(\omega^2 + 1)}$$

4.17 For the circuit shown in Fig. P4.17, find the Thévenin equivalent of the circuit in the shaded box when $v_s(t) = 4 \cos(4t - 60^\circ) \text{ V}$. Use this to determine $v_o(t)$.

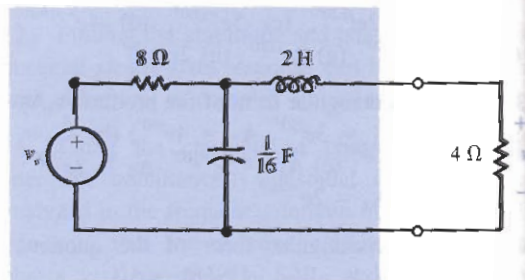


Fig. P4.17

4.18 For the Thévenin equivalent circuit shown in Fig. P4.18, find $v_o(t)$ when $v_s(t) = 10 \cos(2t - 30^\circ) \text{ V}$.

4.19 Find the Thévenin equivalent circuit for the circuit shown in Fig. P4.19. Express V_{oc} and I_{sc} in terms of V_s and R_s .

4.20 The Thévenin equivalent circuit for a circuit is $10 \text{ V} / -15.9^\circ \text{ V}$ and $1 \text{ }\Omega$. Find the corresponding circuit.

4.21 For the circuit shown in Fig. P4.21, find $v_o(t)$ when $v_s(t) = 10 \cos(2t - 30^\circ) \text{ V}$.

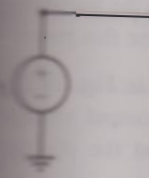


Fig. P4.21

4.22 For the circuit shown in Fig. P4.22, find $v_o(t)$ when $v_s(t) = 10 \cos(2t - 30^\circ) \text{ V}$.

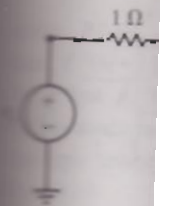


Fig. P4.22

4.18 For the circuit shown in Fig. P4.17, find the Thévenin equivalent of the circuit in the shaded box when $v_s(t) = 4 \cos(2t - 60^\circ)$ V. Use this to determine $v_o(t)$.

4.19 Find the frequency-domain Thévenin equivalent (to the left of terminals a and b) of the circuit shown in Fig. 4.20 on p. 211. (Hint: Use the fact that $R_o = V_{oc}/I_{sc}$.)

4.20 The frequency-domain Thévenin equivalent of a circuit having $\omega = 5$ rad/s has $V_{oc} = 17\angle -15.9^\circ$ V and $Z_o = 2.38 - j0.667 \Omega$. Determine a corresponding time-domain Thévenin-equivalent circuit.

4.21 For the op-amp circuit shown in Fig. P4.21, find $v_o(t)$ when $v_s(t) = 6 \sin 2t$ V.

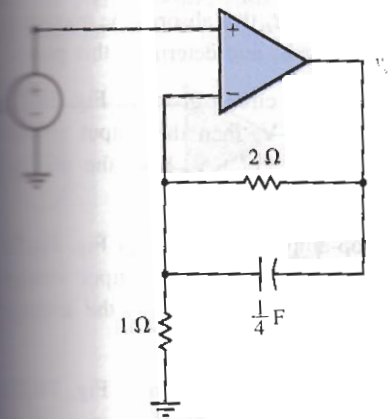


Fig. P4.21

4.22 For the op-amp circuit given in Fig. P4.22, find $v_o(t)$ when $v_s(t) = 3 \cos 2t$ V.

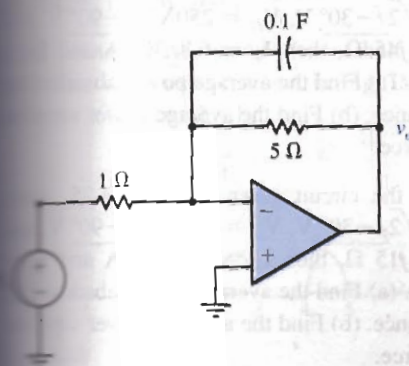


Fig. P4.22

4.23 For the op-amp circuit shown in Fig. P4.23, find $v_o(t)$ when $v_s(t) = 4 \cos(2t - 30^\circ)$ V. (See p. 258.)

4.24 For the circuit shown in Fig. P4.24, find the currents I_1 and I_2 when $V_{s1} = 250\sqrt{2}\angle -30^\circ$ V, $V_{s2} = 250\sqrt{2}\angle -90^\circ$ V, and $Z = 78 - j45 \Omega$.

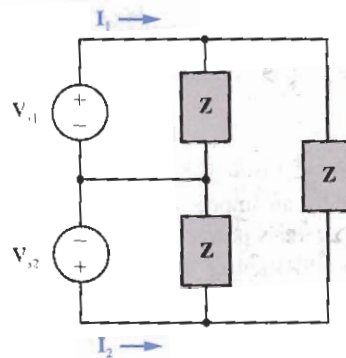


Fig. P4.24

4.25 Use mesh analysis to find I_1 and I_2 for the circuit given in Fig. P4.25 when $V_{s1} = 250\sqrt{2}\angle -30^\circ$ V, $V_{s2} = 250\sqrt{2}\angle -90^\circ$ V, and $Z = 26 - j15 \Omega$.

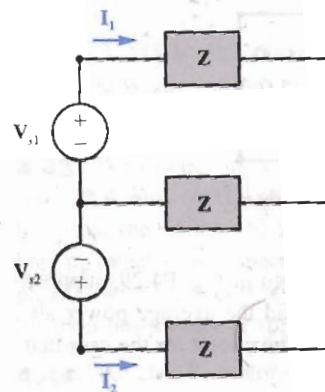


Fig. P4.25

4.26 For the circuit shown in Fig. P4.9, when $i_s(t) = 5 \cos 3t$ A then $v_o(t) = 4.47 \cos(3t + 26.6^\circ)$ V. Find the average power absorbed by each element in the circuit.

4.27 For the circuit shown in Fig. P4.17, when $v_s(t) = 10 \cos 4t$ V, then the Thévenin equivalent of the portion of the circuit in the shaded box is $V_{oc} =$

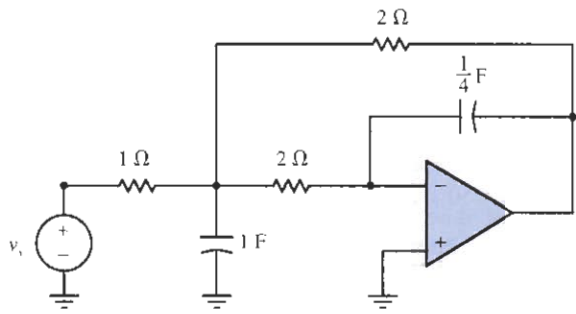


Fig. P4.23

4.47 $\angle -63.4^\circ$ V and $Z_L = 1.6 + j4.8 \Omega$. (a) Replace the $4\text{-}\Omega$ load resistor by an impedance Z_L that absorbs the maximum average power, and determine this maximum power. (b) Replace the $4\text{-}\Omega$ load resistor with a resistance R_L that absorbs the maximum power for resistive loads, and determine this power.

4.28 For the RLC circuit shown in Fig. P4.28, suppose that $v_s(t) = 10 \cos 3t$ V. Find the average power absorbed by the $4\text{-}\Omega$ resistor for the case that (a) $C = \frac{1}{6}$ F; (b) $C = \frac{1}{18}$ F; (c) $C = \frac{1}{9}$ F.

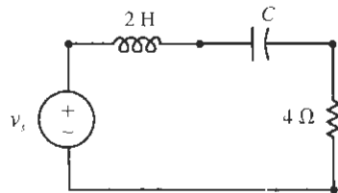


Fig. P4.28

4.29 For the circuit shown in Fig. P4.29, suppose that $v_s(t) = 8 \cos 2t$ V. Find the average power absorbed by each element in the circuit for the case that $Z_L = 1 \Omega$.

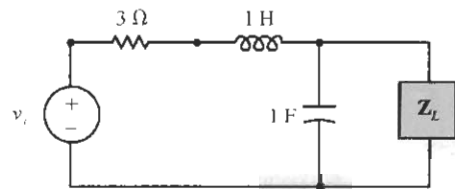


Fig. P4.29

4.30 For the circuit shown in Fig. P4.29, change the value of the resistor to 2Ω and the value of the capacitor to $\frac{1}{4}$ F. Suppose that $v_s(t) = 8 \cos 2t$ V. (a) Find the load impedance Z_L that absorbs the maximum average power, and determine this power. (b) Find the load resistance R_L that absorbs the maximum power for resistive loads, and determine this power.

4.31 For the op-amp circuit given in Fig. P4.21, when $v_s(t) = 6 \sin 2t$ V, then the output voltage $v_o(t) = 13.4 \cos(2t - 117^\circ)$ V. Find the average power absorbed by each element.

4.32 For the op-amp circuit given in Fig. P4.22, when $v_s(t) = 3 \cos 2t$ V, then the output voltage $v_o(t) = 10.6 \cos(2t + 135^\circ)$ V. Find the average power absorbed by each element.

4.33 For the op-amp circuit given in Fig. P4.23, when $v_s(t) = 4 \cos(2t - 30^\circ)$ V, then $v_1(t) = 1.6 \cos(2t - 66.9^\circ)$ V and $v_2(t) = 1.6 \cos(2t + 23.1^\circ)$ V. Find the average power absorbed by each element.

4.34 For the circuit given in Fig. P4.24, when $\mathbf{V}_{s1} = 250\sqrt{2}\angle -30^\circ$ V, $\mathbf{V}_{s2} = 250\sqrt{2}\angle -90^\circ$ V, and $\mathbf{Z} = 78 - j45 \Omega$, then $\mathbf{I}_1 = 6.8\angle 30^\circ$ A and $\mathbf{I}_2 = 6.8\angle -90^\circ$ A. (a) Find the average power absorbed by each impedance. (b) Find the average power supplied by each source.

4.35 For the circuit given in Fig. P4.25, when $\mathbf{V}_{s1} = 250\sqrt{2}\angle -30^\circ$ V, $\mathbf{V}_{s2} = 250\sqrt{2}\angle -90^\circ$ V, and $\mathbf{Z} = 26 - j15 \Omega$, then $\mathbf{I}_1 = 6.8\angle 30^\circ$ A and $\mathbf{I}_2 = 6.8\angle -90^\circ$ A. (a) Find the average power absorbed by each impedance. (b) Find the average power supplied by each source.

4.36 For the o...
and the average p...
the case that $v_s(t)$

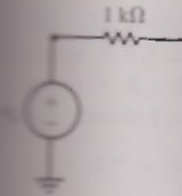


Fig. P4.36

4.37 For the op...
and the average p...
the case that $v_s(t)$

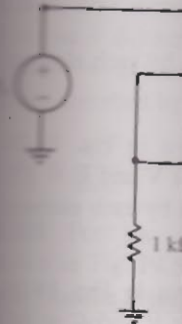


Fig. P4.37

4.38 Find the m...
Fig. P4.38. (See p.

4.39 Find the m...
and sine wave th...
 $\cos^2 x = \frac{1}{2}(1 + \cos 2x)$



Fig. P4.39