

If there are no cancellations of common poles and zeros, the poles of a network function indicate the natural response.

A linear system can be simulated with integrators, differentiators, and scalars (i.e., with an analog computer).

Block diagrams are often represented by block diagrams.

Feedback can improve system performance and is used for purposes of control.

The Laplace transform is a linear transformation that can be used to solve linear differential equations and analyze linear circuits.

12. The inverse Laplace transform can be found by using a table of transforms and various transform properties, as well as partial-fraction expansions.

13. The impedance of an R -ohm resistor is R , of an L -henry inductor is sL , and of a C -farad capacitor is $1/sC$.

14. An inductor (or a capacitor) with a nonzero initial condition can be modeled by an independent source and an inductor (or capacitor) with a zero initial condition.


15. Circuit analysis using Laplace transforms results in complete (both forced and natural) responses.

Problems

Sketch the phase response $\text{ang}(V_2/V_1)$ versus ω for the high-pass filter given in Fig. 5.5 on p. 269.

For the circuit given in Fig. 5.5 on p. 269, sketch the amplitude response $\text{mag}(V_2/V_1)$ versus ω for the low-pass filter.

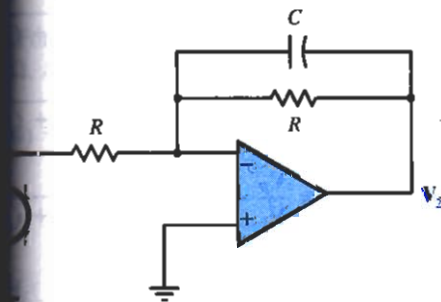Sketch the amplitude response of V_2/V_1 for the circuit shown in Fig. P5.3. Determine the half-power frequency. What type of filter is this circuit?



Show that for the circuit given in Fig. P5.4 the transfer function is

$$H(s) = \frac{V_2}{V_1} = \frac{R_2(1 + j\omega R_1 C_1)}{(R_1 + R_2) + j\omega R_1 R_2 (C_1 + C_2)}$$

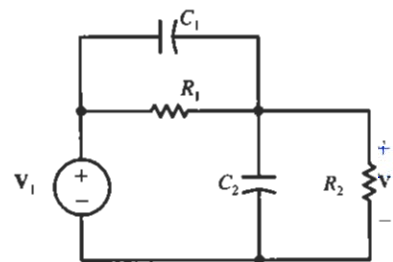


Fig. P5.4

5.5 For the circuit shown in Fig. P5.4, suppose that $R_1 = R_2 = R$ and $C_1 = C_2 = C$. Sketch the amplitude response and the phase response of V_2/V_1 .

5.6 For the circuit shown in Fig. P5.4, suppose that $R_1 = R_2 = R$, $C_1 = C$ and $C_2 = 0$ F. Sketch the amplitude response of V_2/V_1 . What is the half-power frequency?

5.7 For the circuit shown in Fig. P5.4, suppose that $R_1 = R_2 = R$, $C_1 = 0$ F and $C_2 = C$. Sketch the amplitude response of V_2/V_1 . What is the half-power frequency?

5.8 For the op-amp circuit shown in Fig. P5.8, sketch the amplitude response of V_2/V_1 , indicating the half-power frequency. What type of filter is this circuit?