

Example 1.11

Let us now consider the circuit given. A dependent current source is specified. The value of the source is $0.5v$ amperes, where v is the voltage across the 4Ω resistor (also the 4Ω resistor in this case). The unit of the source is A/V, or mhos—so it is a conductance source.

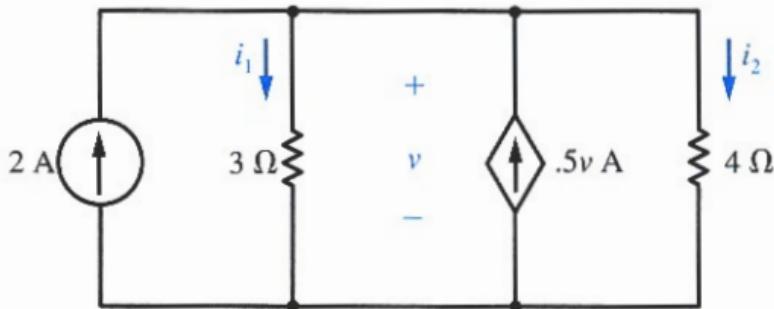


Fig. 1.52 Circuit with voltage-dependent current source.

100 Circuits

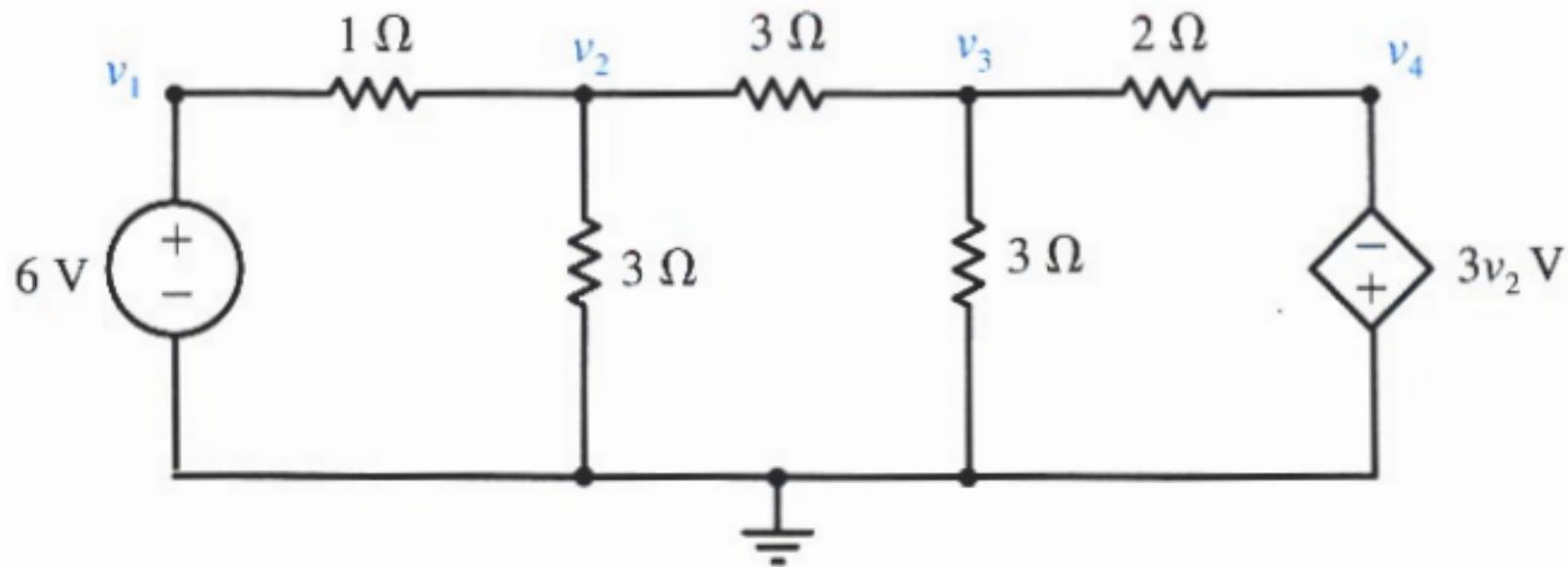


Fig. P2.7

2.5 Find the node voltages for the circuit shown in Fig. P2.5.

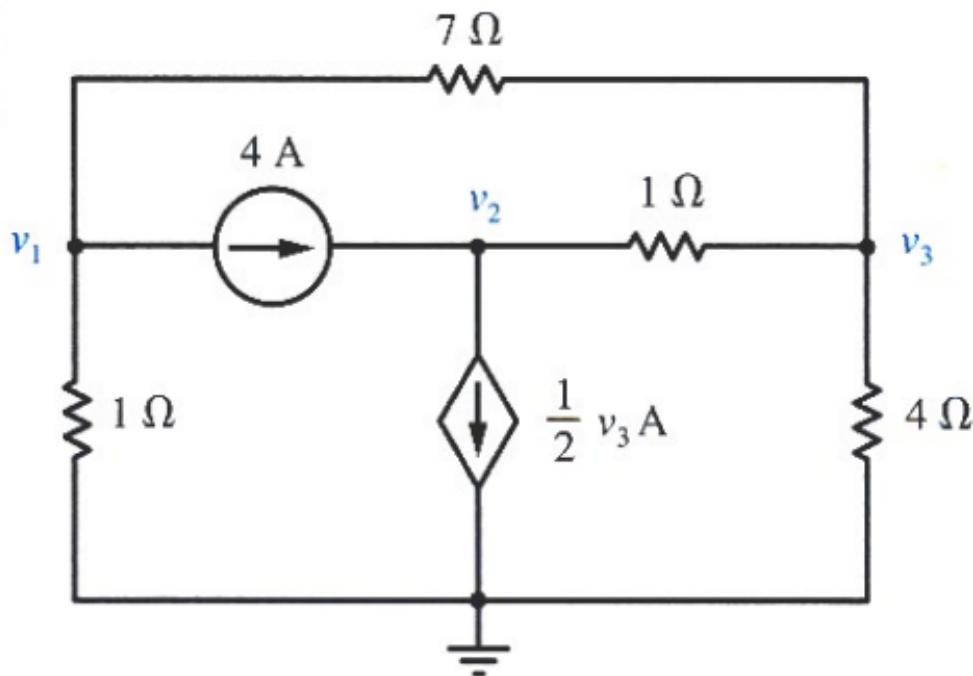


Fig. P2.5

Fig. P2.8

2.9 Find the node voltages for the circuit shown in Fig. P2.9.

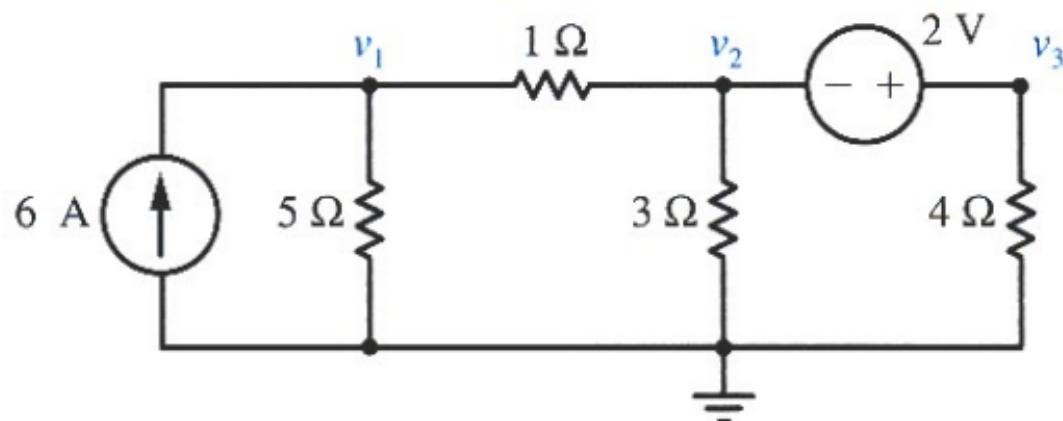


Fig. P2.9