

- 1.12** Consider the circuit shown in Fig. P1.12. (a) Given $i_1 = -4 \text{ A}$, find v_1 . (b) Given $i_2 = 1 \text{ A}$, find v_2 . (c) Given $i_3 = 1 \text{ A}$, find v_3 . (d) Given $i_4 = 2 \text{ A}$, find v_4 .

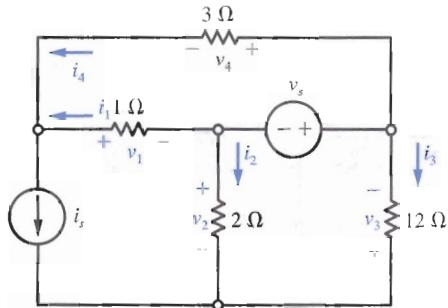


Fig. P1.12

- 1.13** Consider the circuit in Fig. P1.12. (a) Given $v_1 = -2 \text{ V}$, find i_1 . (b) Given $v_2 = -1 \text{ V}$, find i_2 . (c) Given $v_3 = -6 \text{ V}$, find i_3 . (d) Given $v_4 = 3 \text{ V}$, find i_4 .

- 1.14** Consider the circuit in Fig. P1.14. (a) Given $i_1 = 3 \text{ A}$ and $v_1 = 6 \text{ V}$, find R_1 . (b) Given $i_2 = 3 \text{ A}$ and $v_2 = -15 \text{ V}$, find R_2 . (c) Given $i_3 = -2 \text{ A}$ and $v_3 = 6 \text{ V}$, find R_3 . (d) Given $i_4 = -1 \text{ A}$ and $v_3 = 6 \text{ V}$, find R_4 .

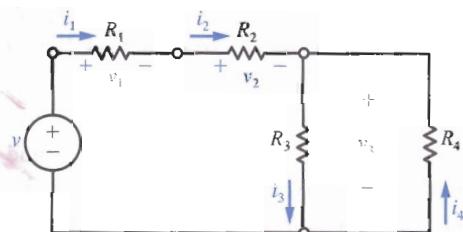


Fig. P1.14

- 1.15** Consider the circuit in Fig. P1.14. (a) Given $i_1 = 6 \text{ A}$ and $v_1 = 18 \text{ V}$, find R_1 . (b) Given $i_2 = 6 \text{ A}$ and $v_2 = -36 \text{ V}$, find R_2 . (c) Given $i_3 = 4 \text{ A}$ and $v_3 = 16 \text{ V}$, find R_3 . (d) Given $i_4 = -2 \text{ A}$ and $v_3 = 16 \text{ V}$, find R_4 .

- 1.16** For the circuit shown in Fig. P1.16, find v when (a) $i_s = 1 \text{ A}$, (b) $i_s = 2 \text{ A}$, (c) $i_s = 3 \text{ A}$.

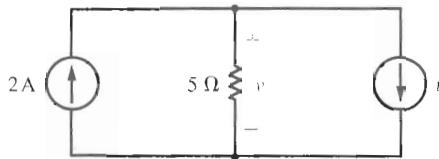


Fig. P1.16

- 1.17** For the circuit shown in Fig. P1.17, find i when (a) $v_s = 1 \text{ V}$, (b) $v_s = 2 \text{ V}$, (c) $v_s = 3 \text{ V}$.

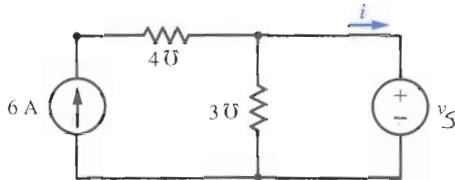


Fig. P1.17

- 1.18** For the circuit shown in Fig. P1.18, find v_4 when (a) $v_s = 2 \text{ V}$, (b) $v_s = 4 \text{ V}$, (c) $v_s = 6 \text{ V}$.

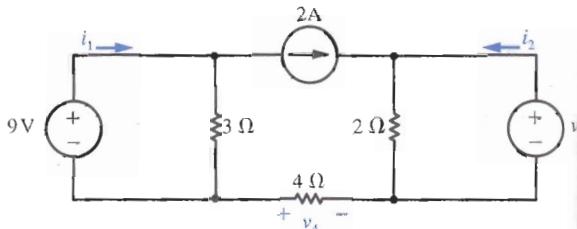


Fig. P1.18

- 1.19** For the circuit shown in Fig. P1.19, suppose that $i_1 = 6 \text{ A}$. Use the current-divider formula to determine i_2 , i_3 , i_4 , and i_5 .

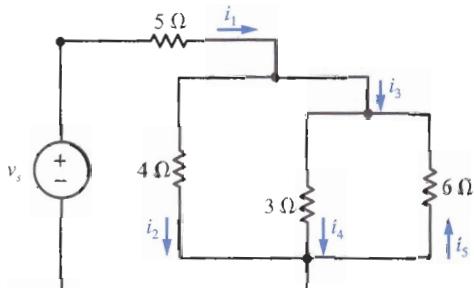


Fig. P1.19

- 1.20** For the circuit shown in Fig. P1.19, suppose that $i_4 = 4 \text{ A}$. Use the current-divider formula to determine i_1 , i_2 , i_3 , and i_5 .

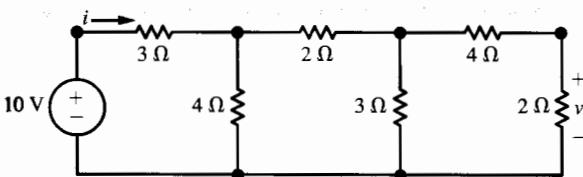


Fig. P1.30

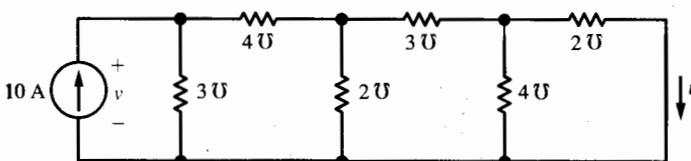


Fig. P1.31

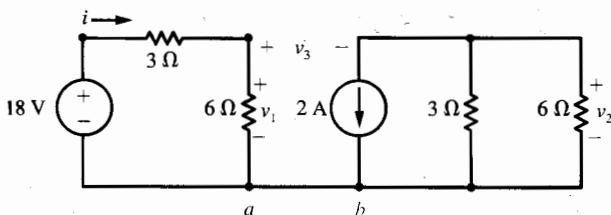


Fig. P1.32

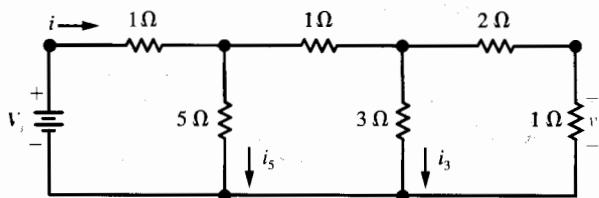


Fig. P1.33

1.34 Consider the nonseries-parallel circuit shown in Fig. P1.34. (a) When $R = \frac{1}{2} \Omega$, then $v_1 = 6$ V. Determine the resistance $R_{eq} = V_s/i$ loading the battery.

1.35 Consider the nonseries-parallel circuit shown in Fig. P1.34. When $R = 4 \Omega$, then $v_1 = 4$ V. Determine the resistance $R_{eq} = V_s/i$ loading the battery.

36 Consider the nonseries-parallel circuit shown in Fig. P1.34. Determine R and the resistance $R_{eq} = V_s/i$ loading the battery when $v_1 = 3$ V.

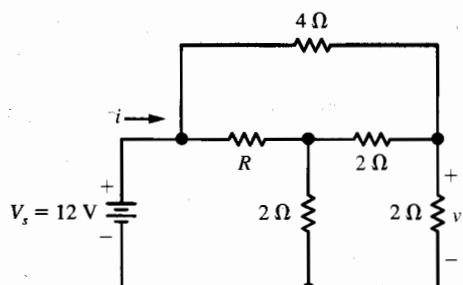


Fig. P1.34

1.37 The nonseries-parallel circuit shown in Fig. P1.37 is known as a **twin-T network**. (a) When $R_1 = 1 \Omega$ and $R_2 = 3 \Omega$, then $v_2 = 6$ V. Determine the resistance $R_{eq} = V_s/i$ loading the battery.

1.38 For the twin-T network shown in Fig. P1.37, suppose that $R_2 = \frac{3}{4} \Omega$ and $v_2 = 3$ V. Determine R_1 and the resistance $R_{eq} = V_s/i$ loading the battery.

1.39 Shown in Fig. P1.39 is a nonseries-parallel connection known as a **bridge circuit**. When $R_1 = 10 \Omega$ and $R_2 = 1 \Omega$, then $v_1 = 10$ V. Find v_2 , i , v_3 , and the resistance $R_{eq} = V_s/i_s$ loading the voltage source.

1.40 For the bridge circuit shown in Fig. P1.39, when $R_1 = 2 \Omega$ and $R_2 = 4 \Omega$, then $v_1 = 4$ V. Find v_2 , i , v_3 , and the resistance $R_{eq} = V_s/i_s$ loading the voltage source.

1.41 For the bridge circuit shown in Fig. P1.39, when the current $i = 0$ A, we say that the bridge

is **balanced**. Under what condition (find an expression relating R_1 and R_2) will this bridge be balanced?

1.42 For the circuit shown in Fig. P1.42, find i_1 when (a) $K = 2$, (b) $K = 3$, and (c) $K = 4$.

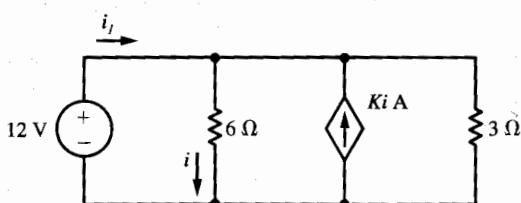


Fig. P1.42

1.43 The circuit shown in Fig. P1.43 contains a **voltage-dependent voltage source** as well as a current-dependent current source. Find i_1 when (a) $K = -3$, (b) $K = -1.5$, and (c) $K = 1.5$.

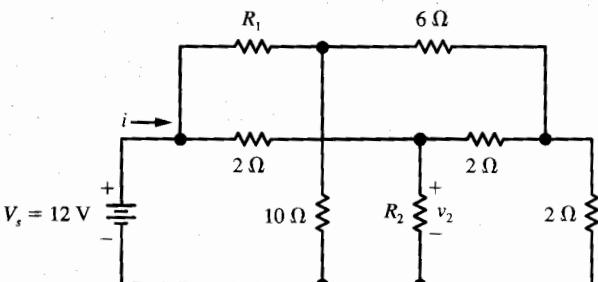


Fig. P1.37

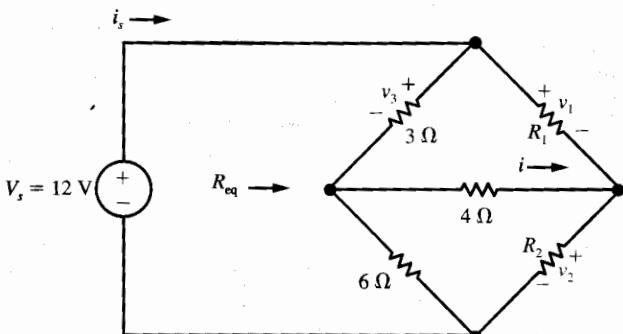


Fig. P1.39

1.44 Consider the circuit shown in Fig. P1.44. Find v when (a) $K = 2$, and (b) $K = 4$.

1.45 Consider the circuit shown in Fig. P1.45. Find i when (a) $K = 2$, and (b) $K = 4$.

1.46 Consider the circuit shown in Fig. P1.46. (a) Find the resistance $R_{eq} = v_1/i_1$. (b) Find the voltage v_2 in terms of the applied voltage v_1 .

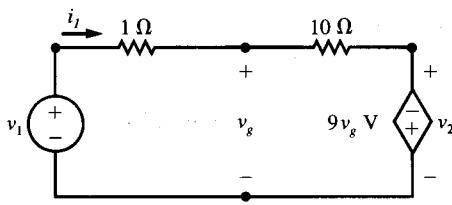


Fig. P1.46

1.47 Consider the circuit shown in Fig. P1.47. (a) Find the resistance $R_{eq} = v_1/i_1$. (b) Use voltage division to find v in terms of v_g . (c) Find the voltage v_2 in terms of the applied voltage v_1 .

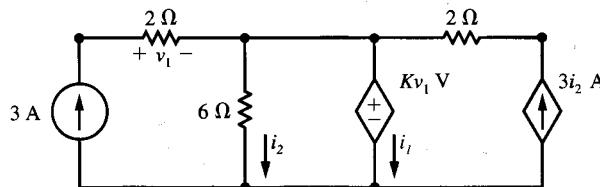


Fig. P1.47

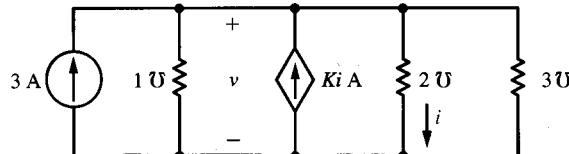


Fig. P1.48

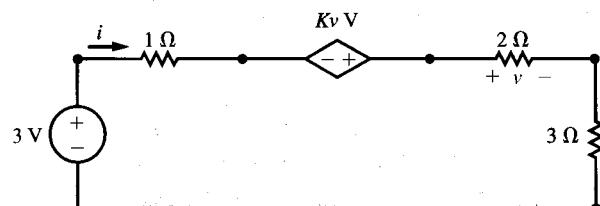


Fig. P1.49

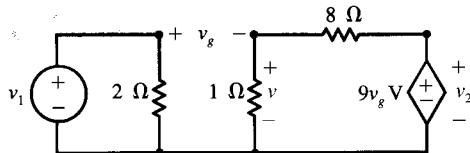


Fig. P1.47

1.48 For the circuit shown in Fig. P1.48, suppose that $R = 10 \Omega$. Determine (a) v_s , and (b) $R_{eq} = v_s/i_s$.

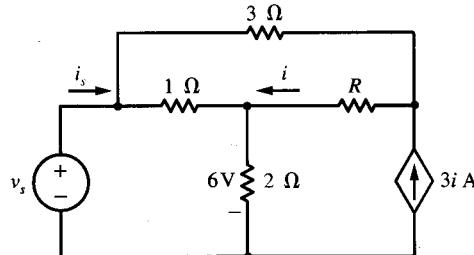


Fig. P1.48

1.49 For the circuit shown in Fig. P1.49, suppose that $R = 8 \Omega$. Determine (a) v_s , and (b) $R_{eq} = v_s/i_s$.