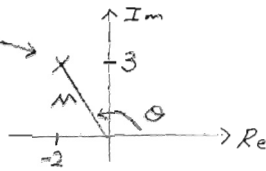


E5332

## HW 10 SOLN

1/2

P4.1 (c)  $-2 + j3$



$$M = \sqrt{(-2)^2 + (3)^2} = \sqrt{13}$$


$$\theta = \tan^{-1}\left(\frac{3}{-2}\right) = 2.16 \text{ rad} = 123.7^\circ$$

↑  
be careful of quadrant

$$\sqrt{13} e^{j2.16}$$

$$= \underline{\underline{3.61 \angle 123.7^\circ}}$$

(d)  $-1 - j6$

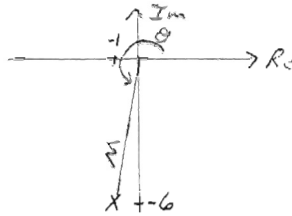

$$M = \sqrt{(-1)^2 + (6)^2} = \sqrt{37}$$

$$\theta = \tan^{-1}\left(\frac{-6}{-1}\right) = -1.736 \text{ rad} = -99.5^\circ$$

↑  
careful of quadrant

$$\sqrt{37} e^{-j1.736}$$

$$= \underline{\underline{6.08 \angle -99.5^\circ}}$$

can add  $2\pi, 360^\circ$  to angles  
to get 4.55 rad,  $260.5^\circ$

P4.2 (c)  $5e^{j60^\circ} = 5(\cos(-60^\circ) + j\sin(-60^\circ))$ 

$$= 5\left(\frac{1}{2} + j\left(-\frac{\sqrt{3}}{2}\right)\right)$$

$$\underline{\underline{\frac{5}{2} - j\frac{5\sqrt{3}}{2} = 2.5 - j4.33}}$$

(d)  $4e^{-j150^\circ} = 4(\cos(-150^\circ) + j\sin(-150^\circ))$ 

$$= 4\left(-\frac{\sqrt{3}}{2} - j\frac{1}{2}\right)$$

$$= -2\sqrt{3} - j2$$

$$\underline{\underline{-2\sqrt{3} - j2 = -3.46 - j2}}$$

ES332

HW10 SOLN

P4.3 (c)  $\hat{A}_1 \hat{A}_2 = 5e^{-j60^\circ} 2e^{j120^\circ} = 10e^{j60^\circ}$   
 $= 10(\cos 60^\circ + j \sin 60^\circ)$   
 $= 10(\frac{1}{2} + j\frac{\sqrt{3}}{2})$   
 $= \underline{\underline{5 + j5\sqrt{3} = 5 + j8.66}}$

(d)  $\hat{A}_1 \hat{A}_2 = 4e^{j45^\circ} 2e^{-j90^\circ} = 8e^{-j45^\circ}$   
 $= 8(\cos(-45^\circ) + j \sin(-45^\circ))$   
 $= 8(\frac{\sqrt{2}}{2} - j\frac{\sqrt{2}}{2})$   
 $= \underline{\underline{4\sqrt{2} - j4\sqrt{2} = 5.66 - j5.66}}$


P4.4 (c)  $\frac{\hat{A}_1}{\hat{A}_2} = \frac{5e^{-j60^\circ}}{2e^{j120^\circ}} = \frac{5}{2}e^{-j180^\circ} = \frac{5}{2}(\cos(-180^\circ) + j \sin(-180^\circ))$   
 $= \frac{5}{2}(-1 + j0)$   
 $= \underline{\underline{-\frac{5}{2} + j0 = -2.5}}$

(d)  $\frac{\hat{A}_1}{\hat{A}_2} = \frac{4e^{j45^\circ}}{2e^{-j90^\circ}} = \frac{4}{2}e^{j135^\circ} = 2(\cos 135^\circ + j \sin 135^\circ)$   
 $= 2(-\frac{\sqrt{2}}{2} + j\frac{\sqrt{2}}{2})$   
 $= \underline{\underline{-\sqrt{2} + j\sqrt{2} = -1.414 + j1.414}}$


P4.5 (c)  $\hat{A}_1 + \hat{A}_2 = 5e^{-j60^\circ} + 2e^{j120^\circ}$   
 $= 5(\cos(-60^\circ) + j \sin(-60^\circ)) + 2(\cos(120^\circ) + j \sin(120^\circ))$   
 $= \frac{5}{2} - j\frac{5\sqrt{3}}{2} + 2(-\frac{1}{2}) + j2(\frac{\sqrt{3}}{2})$   
 $= \underline{\underline{\frac{3}{2} - j\frac{3\sqrt{3}}{2} = 1.5 - j2.60}}$

(d)  $\hat{A}_1 + \hat{A}_2 = 4e^{j45^\circ} + 2e^{-j90^\circ}$   
 $= 4(\cos 45^\circ + j \sin 45^\circ) + 2(\cos(-90^\circ) + j \sin(-90^\circ))$   
 $= 4(\frac{\sqrt{2}}{2} + j\frac{\sqrt{2}}{2}) + 2(0 - j)$   
 $= (2\sqrt{2} + 0) + j(2\sqrt{2} - 2)$   
 $= \underline{\underline{2\sqrt{2} + j(2\sqrt{2} - 2) = 2.83 + j0.83}}$

DE 4.6

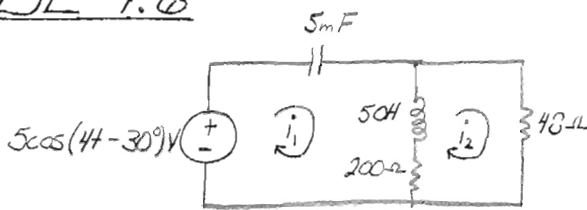

convert to freq-domain

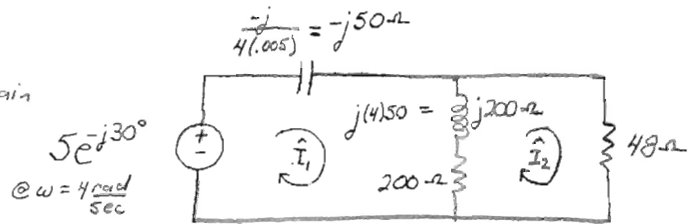

mesh analysis

$$\begin{aligned}
 \text{e } \hat{I}_1: & -5e^{-j30^\circ} - j50\hat{I}_1 + (j200 + 200)(\hat{I}_1 - \hat{I}_2) = 0 \\
 \Rightarrow & (200 + j150)\hat{I}_1 - (200 + j200)\hat{I}_2 = 5e^{-j30^\circ} \\
 \Rightarrow & (40 + j30)\hat{I}_1 - (40 + j48)\hat{I}_2 = 1e^{-j30^\circ} \quad \times 1/5
 \end{aligned}$$

$$\begin{aligned}
 \text{e } \hat{I}_2: & (200 + j200)(\hat{I}_1 - \hat{I}_2) + 48\hat{I}_2 = 0 \\
 \Rightarrow & -(200 + j200)\hat{I}_1 + (248 + j200)\hat{I}_2 = 0
 \end{aligned}$$

matrix-vector form

$$\begin{bmatrix} 40 + j30 & -40 - j40 \\ -200 - j200 & 248 + j200 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} 1e^{-j30^\circ} \\ 0 \end{bmatrix}$$

Cramer's Rule

$$\hat{I}_1 = \frac{\begin{vmatrix} 1e^{-j30^\circ} & -40 - j40 \\ 0 & 248 + j200 \end{vmatrix}}{\begin{vmatrix} 40 + j30 & -40 - j40 \\ -200 - j200 & 248 + j200 \end{vmatrix}} = \frac{314.8 + j49.2}{3920 - j560} = 0.0769 + j0.0235 = 0.0805 e^{j0.297} = 0.0805 \angle 17^\circ$$

$$\hat{I}_2 = \frac{\begin{vmatrix} 40 + j30 & 1e^{-j30^\circ} \\ -200 - j200 & 0 \end{vmatrix}}{\begin{vmatrix} 40 + j30 & -40 - j40 \\ -200 - j200 & 248 + j200 \end{vmatrix}} = \frac{273.2 + j73.2}{3920 - j560} = 0.0657 + j0.0281 = 0.0714 e^{j0.404} = 0.0714 \angle 23.1^\circ$$

Back to time



$$\underline{i_1(t) = 0.0805 \cos(4t + 17.0^\circ) \text{ A} = 0.0805 \cos(4t + 0.297) \text{ A}}$$

$$\underline{i_2(t) = 0.0714 \cos(4t + 23.1^\circ) \text{ A} = 0.0714 \cos(4t + 0.404) \text{ A}}$$

E5332

HW11 SOLN

P4.8

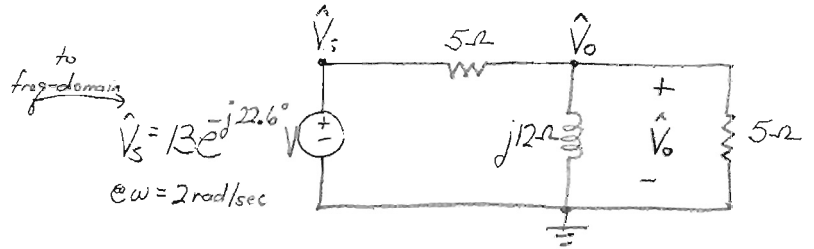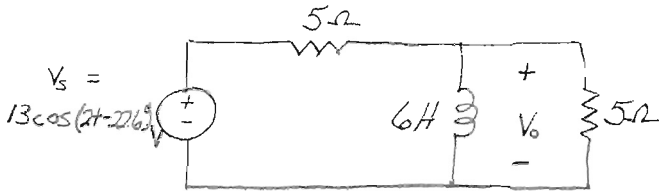

nodal analysis

@  $\hat{V}_s$ :  $\hat{V}_s = 13 \angle -22.6^\circ$  V known

@  $\hat{V}_o$ :  $\frac{\hat{V}_o - \hat{V}_s}{5} + \frac{\hat{V}_o}{j12} + \frac{\hat{V}_o}{5} = 0$

$j12\hat{V}_o - j12\hat{V}_s + 5\hat{V}_o + j12\hat{V}_o = 0$   $\times j60$

$\Rightarrow \hat{V}_o (j12 + 5 + j12) = j12\hat{V}_s$

$\Rightarrow \hat{V}_o (5 + j24) = 12e^{j90^\circ} 13e^{-j22.6^\circ}$

$\Rightarrow \hat{V}_o = \frac{156 e^{j67.4^\circ}}{5 + j24}$

$= \frac{156 e^{j67.4^\circ}}{24.5 e^{j78.2^\circ}}$


$= 6.25 - j1.196$  V

$= 6.36 e^{-j0.189} \text{ V} = 6.36 \angle -10.83^\circ \text{ V}$

back to time

$v_o(t) = 6.36 \cos(2t - 10.83^\circ) \text{ V} = 6.36 \cos(2t - 0.189) \text{ V}$


phasor diagram

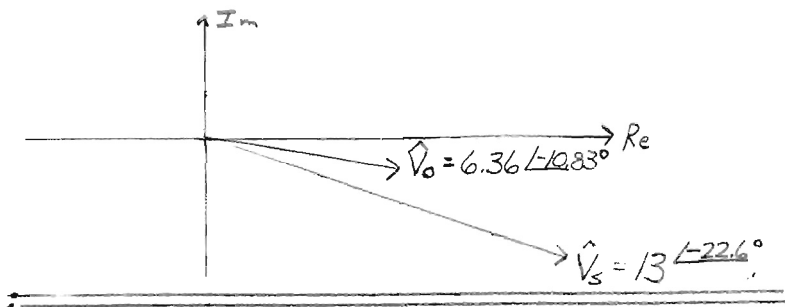

$V_o$  leads  $V_s$

P4.13

in freq-domain:

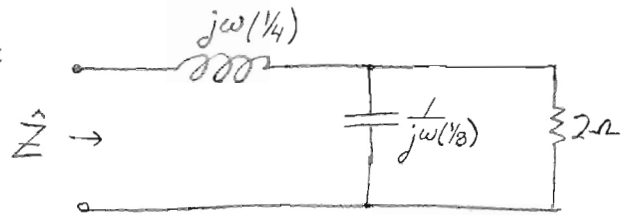

$$\begin{aligned} \hat{Z} &= j\omega\left(\frac{1}{4}\right) + \frac{\frac{1}{j\omega(1/8)} \cdot 2}{\frac{1}{j\omega(1/8)} + 2} \\ &= j\omega\left(\frac{1}{4}\right) + \frac{\frac{16}{j\omega}}{\frac{8}{j\omega} + 2} \quad \left. \begin{array}{l} \times \frac{j\omega}{j\omega} \\ \times \frac{1/2}{1/2} \end{array} \right\} \\ &= j\omega\left(\frac{1}{4}\right) + \frac{16}{8 + j\omega 2} \quad \left. \begin{array}{l} \times \frac{4-j\omega}{4-j\omega} \\ \times \frac{1/2}{1/2} \end{array} \right\} \\ &= j\omega\left(\frac{1}{4}\right) + \frac{8}{4 + j\omega} \\ &= j\omega\left(\frac{1}{4}\right) + \frac{32 - j\omega 8}{16 + \omega^2} \\ &= \frac{32}{16 + \omega^2} + j\omega\left(\frac{1}{4} - \frac{8}{16 + \omega^2}\right) \end{aligned}$$

$$\begin{aligned} \text{(a) } \omega = 2 \frac{\text{rad}}{\text{sec}} &\Rightarrow \hat{Z} = \frac{32}{16 + 2^2} + j2\left(\frac{1}{4} - \frac{8}{16 + 2^2}\right) = 1.6 - j0.3 \Omega \\ &= 1.628 e^{-j0.185} \Omega \\ &= \underline{\underline{1.628 \angle -10.62^\circ \Omega}} \end{aligned}$$


$$\begin{aligned} \text{(b) } \omega = 4 \frac{\text{rad}}{\text{sec}} &\Rightarrow \hat{Z} = \frac{32}{16 + 4^2} + j4\left(\frac{1}{4} - \frac{8}{16 + 4^2}\right) \\ &= \underline{\underline{1 \Omega}} \end{aligned}$$

$$\begin{aligned} \text{(c) } \omega = 8 \frac{\text{rad}}{\text{sec}} &\Rightarrow \hat{Z} = \frac{32}{16 + 8^2} + j8\left(\frac{1}{4} - \frac{8}{16 + 8^2}\right) \\ &= 0.4 + j1.2 \Omega \\ &= 1.265 e^{j1.249} \Omega \\ &= \underline{\underline{1.265 \angle 71.6^\circ \Omega}} \end{aligned}$$

E5332

HW12 SOLN

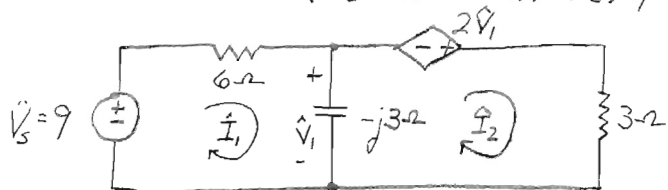Example 4.7 (looking for  $P, Q, \hat{S}$ ; can use  $P = \frac{1}{2} VI \cos(\phi_1 - \phi_2)$ ,  
 $Q = \frac{1}{2} VI \sin(\phi_1 - \phi_2)$  for  $\hat{S} = \frac{1}{2} \hat{V} \hat{I}^* = P + jQ$ )



$\hat{I}_1 = 1.30 \angle 12.49^\circ, \hat{I}_2 = 1.24 \angle -15.9^\circ$

indep source:  $\hat{S}_s = -\frac{1}{2} 9 \hat{I}_1^* = -\frac{1}{2} 9 (1.30 \angle 12.49^\circ)^* = \underline{\underline{-5.84 + j0.254 \text{ VA}}}$

$\Rightarrow \underline{\underline{P_s = -5.84 \text{ W}, Q_s = 0.254 \text{ VAR}}}$

6 ohm resistor:  $\hat{S}_{6\Omega} = \frac{1}{2} (6 \hat{I}_1) \hat{I}_1^* = \frac{1}{2} 6 I_1^2 = 3 (1.3)^2 = \underline{\underline{5.07 + j0 \text{ VA}}}$

$\underline{\underline{P_6 = 5.07 \text{ W}, Q_6 = 0 \text{ VAR}}}$

-j3 capacitor:  $\hat{S}_c = \frac{1}{2} (-j3)(\hat{I}_1 - \hat{I}_2)(\hat{I}_1 - \hat{I}_2)^*$   
 $= \frac{-j3}{2} (1.30 \angle 12.49^\circ - 1.24 \angle -15.9^\circ)(1.30 \angle 12.49^\circ - 1.24 \angle -15.9^\circ)^*$   
 $= \underline{\underline{0 - j0.252 \text{ VA}}} \Rightarrow \underline{\underline{P_c = 0 \text{ W}, Q_c = -0.252 \text{ VAR}}}$

dep source:  $\hat{S}_d = \frac{1}{2} (2\hat{V}_1)(-\hat{I}_2)^* = \frac{1}{2} (2)(-j3)(\hat{I}_1 - \hat{I}_2)(-\hat{I}_2)^*$   
 $= +j3 (1.30 \angle 12.49^\circ - 1.24 \angle -15.9^\circ)(1.24 \angle -15.9^\circ)^*$   
 $= \underline{\underline{-1.526 - j0.0238 \text{ VA}}} \Rightarrow \underline{\underline{P_d = -1.526 \text{ W}, Q_d = -0.0238 \text{ VAR}}}$

3 ohm resistor:  $\hat{S}_{3\Omega} = \frac{1}{2} (3 \hat{I}_2) \hat{I}_2^* = \frac{3}{2} I_2^2$   
 $= \frac{3}{2} (1.24)^2 = \underline{\underline{2.31 + j0 \text{ VA}}}$   
 $\Rightarrow \underline{\underline{P_3 = 2.31 \text{ W}, Q_3 = 0 \text{ VAR}}}$

not required, but good check is  $\sum \hat{S} = \sum P + j \sum Q = 0$


$\sum P: -5.84 + 5.07 + 0 - 1.526 + 2.31 = 0.006 \approx 0$   
roundoff from  $\hat{I}_1, \hat{I}_2$

$\sum Q: 0.254 + 0 - 0.252 - 0.0238 + 0 = 0.022 \approx 0$

E5332

HW12 Soln

P4.24

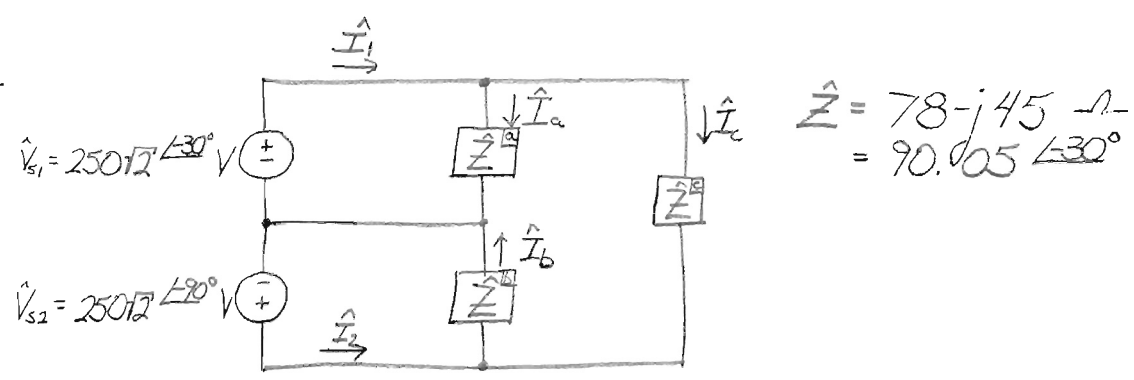

$$\hat{I}_a = \frac{\hat{V}_{s1}}{Z} = \frac{250\sqrt{2} \angle 30^\circ}{78 - j45} = 3.93 \angle -0.184^\circ = 3.93 e^{-j0.184} \text{ A}$$

$$\hat{I}_b = \frac{\hat{V}_{s2}}{Z} = \frac{250\sqrt{2} \angle 90^\circ}{78 - j45} = 3.93 \angle -60^\circ = 3.93 e^{-j1.047} \text{ A}$$

$$\hat{I}_c = \frac{\hat{V}_{s1} - \hat{V}_{s2}}{Z} = \frac{250\sqrt{2} \angle 30^\circ - 250\sqrt{2} \angle 90^\circ}{78 - j45} = 3.93 \angle 60^\circ = 3.93 e^{j1.047} \text{ A}$$

$$\hat{S}_a = \frac{1}{2} \hat{V}_{s1} \hat{I}_a^* = \frac{1}{2} (250\sqrt{2} \angle 30^\circ) (3.93 \angle -0.184^\circ)^* = 601.2 - j346.8 \text{ VA}$$

$\Rightarrow P_a = 601.2 \text{ W}, Q_a = -346.8 \text{ VAR}$

$$\hat{S}_b = \frac{1}{2} \hat{V}_{s2} \hat{I}_b^* = \frac{1}{2} (250\sqrt{2} \angle 90^\circ) (3.93 \angle -60^\circ)^* = 601.2 - j346.8 \text{ VA}$$

$\Rightarrow P_b = 601.2 \text{ W}, Q_b = -346.8 \text{ VAR}$

$$\hat{S}_c = \frac{1}{2} (\hat{V}_{s1} - \hat{V}_{s2}) \hat{I}_c^* = \frac{1}{2} (250\sqrt{2} \angle 30^\circ - 250\sqrt{2} \angle 90^\circ) (3.93 \angle 60^\circ)^*$$

$= 601.2 - j346.8 \text{ VA} \Rightarrow P_c = 601.2 \text{ W}, Q_c = -346.8 \text{ VAR}$

$$\hat{S}_{s1} = -\frac{1}{2} \hat{V}_{s1} \hat{I}_1^* = -\frac{1}{2} \hat{V}_{s1} (\hat{I}_a + \hat{I}_c)^* = -\frac{1}{2} (250\sqrt{2} \angle 30^\circ) (3.93 \angle -0.184^\circ + 3.93 \angle 60^\circ)^*$$

$= -601.4 + j1040.9 \text{ VA}$   
 $\Rightarrow P_{s1} = -601.4 \text{ W}, Q_{s1} = 1040.9 \text{ VAR}$


$$\hat{S}_{s2} = -\frac{1}{2} \hat{V}_{s2} \hat{I}_2^* = -\frac{1}{2} \hat{V}_{s2} (+\hat{I}_b - \hat{I}_c) = -\frac{1}{2} (250\sqrt{2} \angle 90^\circ) (3.93 \angle -60^\circ - 3.93 \angle 60^\circ)^*$$

$= -1202.1 - j38.5 \text{ VA}$   
 $\Rightarrow P_{s2} = -1202.1 \text{ W}, Q_{s2} = -38.5 \text{ VAR}$

not required, but good check is  $\sum \hat{S} = \sum P + j \sum Q = 0$  ✓

ES 332

HW12 SOLN

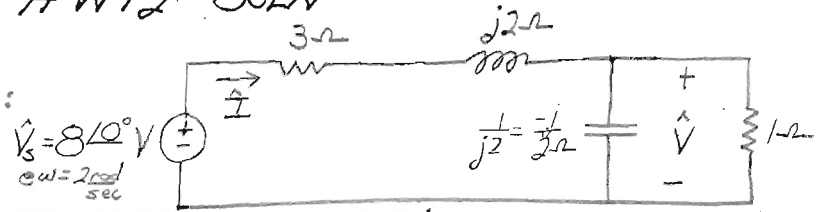P4.29 in freq-domain:

$$\hat{I} = \frac{8}{3 + j2 + 0.2 - j0.4} = \frac{8}{3.2 + j1.6} = 15 \angle -26.6^\circ = 2.236 \angle -26.6^\circ \text{ A}$$

$$\text{in //: } \frac{-j/2 \cdot 1}{1 - j/2} \cdot \frac{1 + j/2}{1 + j/2} = \frac{-j/2 + 1/4}{1 + 1/4} = \frac{1 - j2}{5} = 0.2 - j0.4 \Omega$$

$$\underline{\underline{\hat{S}_s}} = \frac{1}{2} \hat{V}_s \hat{I}^* = \frac{1}{2} 8 (15 \angle 26.6^\circ) = \underline{\underline{-8 - j4 \text{ VA}}}$$

$$\Rightarrow \underline{\underline{P_s = -8 \text{ W}, Q_s = -4 \text{ VAR}}}$$

$$\underline{\underline{\hat{S}_{3\Omega}}} = \frac{1}{2} (3\hat{I}) \hat{I}^* = \frac{3}{2} (15)^2 = \underline{\underline{7.5 + j0 \text{ VA}}}$$

$$\Rightarrow \underline{\underline{P_{3\Omega} = 7.5 \text{ W}, Q_{3\Omega} = 0 \text{ VAR}}}$$

$$\underline{\underline{\hat{S}_j}} = \frac{1}{2} (j2\hat{I}) \hat{I}^* = (15)^2 j = \underline{\underline{0 + j5 \text{ VA}}}$$

$$\Rightarrow \underline{\underline{P_j = 0 \text{ W}, Q_j = 5 \text{ VAR}}}$$

$$\underline{\underline{\hat{S}_c}} = \frac{1}{2} \hat{V} \left( \frac{\hat{V}}{j2} \right)^* = \frac{1}{2} (\hat{I} \times 0.2 - j0.4) \left( \frac{\hat{I} (0.2 - j.4)}{j2} \right)^*$$

$$= \frac{1}{2} (-j2) (0.2^2 + 0.4^2) 15^2$$

$$= \underline{\underline{0 - j1 \text{ VA}}} \Rightarrow \underline{\underline{P_c = 0 \text{ W}, Q_c = -1 \text{ VAR}}}$$

$$\underline{\underline{\hat{S}_{1\Omega}}} = \frac{1}{2} \hat{V} \left( \frac{\hat{V}}{1} \right)^* = \frac{1}{2} \hat{I} (0.2 - j.4) \left( \frac{\hat{I} (0.2 - j.4)}{1} \right)^*$$

$$= \frac{1}{2} (0.2^2 + 0.4^2) 15^2$$

$$= \underline{\underline{0.5 + j0 \text{ VA}}} \Rightarrow \underline{\underline{P_{1\Omega} = 0.5 \text{ W}, Q_{1\Omega} = 0 \text{ VAR}}}$$

not required, but as a check  $\sum \hat{S} = \sum P + j \sum Q = 0$  ✓



E5332

HW 13 SOLN

1/2

P4.42  $V_e = 115 \text{ V}_{\text{rms}}, f = 60 \text{ Hz}, P = 500 \text{ W}, \text{pf} = 0.95 \text{ lag}$

$$P = V_e I_e \cos \theta = V_e I_e \text{pf}$$

$$\Rightarrow \underline{I_e} = \frac{P}{V_e \text{pf}} = \frac{500}{(115)0.95} = \underline{4.58 \text{ A}_{\text{rms}}}$$

P4.43  $V_e = 220 \text{ V}_{\text{rms}}, I_e = 20 \text{ A}_{\text{rms}}, f = 60 \text{ Hz}, P = 2200 \text{ W}$

(a)  $P = V_e I_e \text{pf} \Rightarrow \underline{\text{pf}} = \frac{P}{V_e I_e} = \frac{2200}{(220)(20)} = \underline{0.5}$

(b)  $Q_{\text{motor}} = V_e I_e \sin \theta = V_e I_e \sin(\cos^{-1}(0.5)) = (220)(20) \sin(\frac{1.047 \text{ rad}}{60^\circ})$   
 $= 3810.5 \text{ VAR}$

want total  $Q$  (C//motor) to be 0  $= Q = Q_m + Q_{\text{cap}}$

$$\Rightarrow \text{want } Q_c = -Q_m = -3810.5 \text{ VAR}$$

where  $Q_c = -\omega C V_e^2$

$$\Rightarrow \underline{C} = \frac{Q_c}{-\omega V_e^2} = \frac{-Q_m}{-\omega V_e^2} = \frac{+3810.5}{+(2\pi \cdot 60)(220)^2}$$
$$= \underline{2.09 \times 10^{-4} \text{ F}} = \underline{209 \mu\text{F}}$$

ES332

HW 13 SOLN

P 4.44  $V_e = 220V_{rms}, f = 60Hz, I_e = 20A_{rms}, pf = 0.75 lag$

(a)  $\underline{P} = V_e I_e \cos \theta = P_e I_e pf = (220)(20) 0.75 = \underline{\underline{3300W}}$

(b)  $Q_m = V_e I_e \sin \theta = V_e I_e \sin(\cos^{-1}(0.75))$   
 $= (220)(20) \sin(\underbrace{0.723}_{41.4^\circ} rad)$   
 $= \underline{\underline{2910 VAR}}$

want total Q (C+motor) = 0 =  $Q_m + Q_c$

$\Rightarrow Q_c = -Q_m = -2910 VAR$

where  $Q_c = -\omega C V_e^2$

$\Rightarrow \underline{C} = \frac{-Q_c}{\omega V_e^2} = \frac{Q_m}{\omega V_e^2} = \frac{2910}{(2\pi \cdot 60)(220)^2}$   
 $= \underline{\underline{1.595 \times 10^{-4} F = 159.5 \mu F}}$

P 4.48  $V_e = 220V_{rms}, I_e = 5A_{rms}, pf = 0.95 lag \Rightarrow \theta = \cos^{-1}(0.95) = 0.318 rad = 18.2^\circ$

(a)  $\underline{\hat{S}} = V_e I_e \angle \theta = (220)(5) \angle 18.2^\circ = \underline{\underline{1100 \angle 18.2^\circ VA = 1100 e^{j0.318} VA = 1045 + j343 VA}}$

(b)  $\underline{P} = Re\{\hat{S}\}$  or  $= V_e I_e \cos \theta = \underline{\underline{1045W}}$

(c)  $\underline{Q} = Im\{\hat{S}\}$  or  $= V_e I_e \sin \theta = \underline{\underline{343VAR}}$

(d)  $|\hat{S}| = V_e I_e = \underline{\underline{1100 VA}}$

(e)  $\underline{\hat{Z}} = \frac{\underline{\hat{V}}}{\underline{\hat{I}}} = \frac{V_e \angle \theta}{I_e} = \frac{220 \angle 18.2^\circ}{5} = \underline{\underline{44 \angle 18.2^\circ \Omega = 44 e^{j0.318} \Omega}}$   
 $= \underline{\underline{41.8 + j13.74 \Omega}}$