

Fig. P1.26 a-d

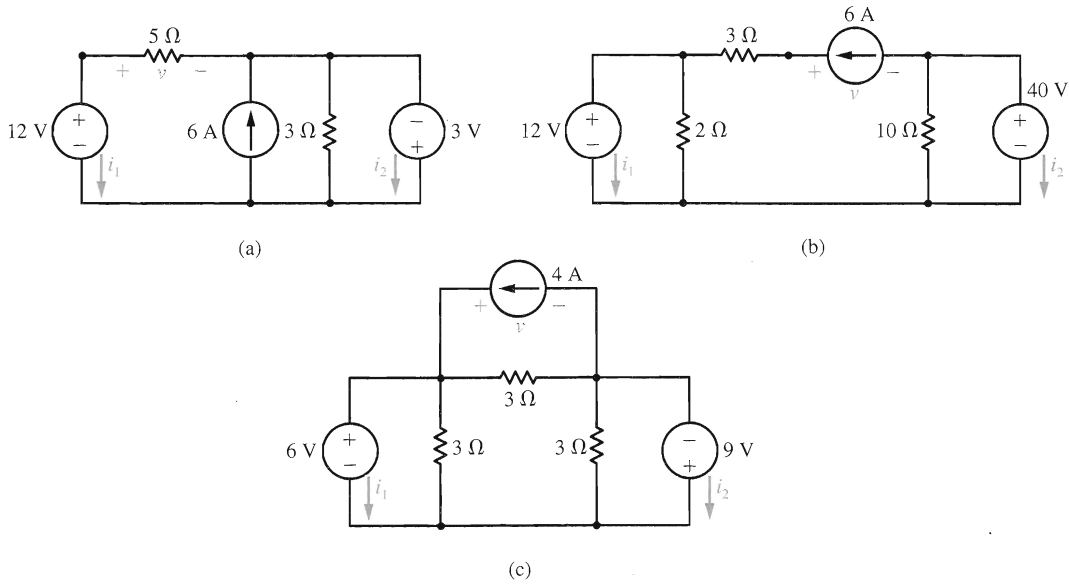


Fig. P1.27 a-c

- 1.30** Find  $v$  and  $i$  for the series-parallel circuit shown in Fig. P1.30.
- 1.31** Find  $v$  and  $i$  for the series-parallel circuit shown in Fig. P1.31.
- 1.32** Consider the circuit shown in Fig. P1.32. (a) Find  $i$ ,  $v_1$ ,  $v_2$ , and  $v_3$ . (b) Remove the short circuit between  $a$  and  $b$  (erase it), and find  $i$ ,  $v_1$ , and  $v_2$ . (Don't try to find  $v_3$ —it can't be done!)
- 1.33** Consider the series-parallel circuit shown in Fig. P1.33. (a) Find  $V_s$  when  $v_1 = 2$  V. (b) Find  $V_s$  when  $i_3 = 3$  A. (c) Find  $V_s$  when  $i_5 = 4$  A. (d) What is the resistance  $R_{eq} = V_s/i$  loading the battery for part (a)? For part (b)? For part (c)?

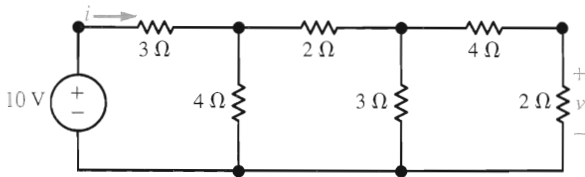


Fig. P1.30

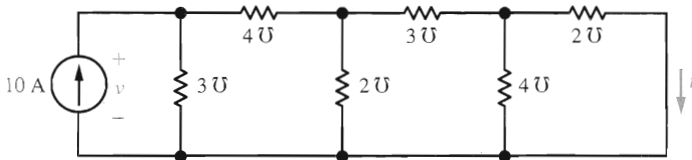


Fig. P1.31

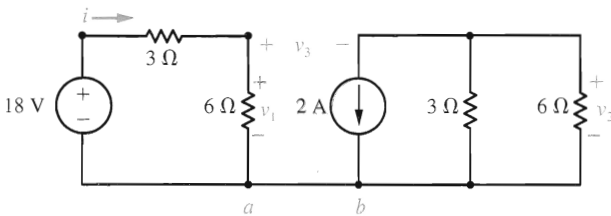


Fig. P1.32

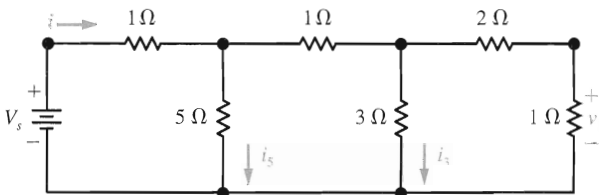


Fig. P1.33

**1.34** Consider the nonseries-parallel circuit shown in Fig. P1.34. (a) When  $R = \frac{1}{2} \Omega$ , then  $v_1 = 6 \text{ V}$ . Determine the resistance  $R_{\text{eq}} = V_s/i$  loading the battery.

**1.35** Consider the nonseries-parallel circuit shown in Fig. P1.34. When  $R = 4 \Omega$ , then  $v_1 = 4 \text{ V}$ . Determine the resistance  $R_{\text{eq}} = V_s/i$  loading the battery.

**1.36** Consider the nonseries-parallel circuit shown in Fig. P1.34. Determine  $R$  and the resistance  $R_{\text{eq}} = V_s/i$  loading the battery when  $v_1 = 3 \text{ V}$ .

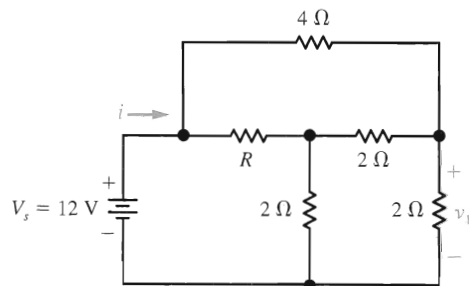


Fig. P1.34

**1.37** The nonseries-parallel circuit shown in Fig. P1.37 is known as a **twin-T network**. (a) When  $R_1 = 1 \Omega$  and  $R_2 = 3 \Omega$ , then  $v_2 = 6 \text{ V}$ . Determine the resistance  $R_{\text{eq}} = V_s/i$  loading the battery.

**1.38** For the twin-T network shown in Fig. P1.37, suppose that  $R_2 = \frac{3}{4} \Omega$  and  $v_2 = 3 \text{ V}$ . Determine  $R_1$  and the resistance  $R_{\text{eq}} = V_s/i$  loading the battery.

**1.39** Shown in Fig. P1.39 is a nonseries-parallel connection known as a **bridge circuit**. When  $R_1 = 10 \Omega$  and  $R_2 = 1 \Omega$ , then  $v_1 = 10 \text{ V}$ . Find  $v_2$ ,  $i$ ,  $v_3$ , and the resistance  $R_{\text{eq}} = V_s/i_s$  loading the voltage source.

**1.40** For the bridge circuit shown in Fig. P1.39, when  $R_1 = 2 \Omega$  and  $R_2 = 4 \Omega$ , then  $v_1 = 4 \text{ V}$ . Find  $v_2$ ,  $i$ ,  $v_3$ , and the resistance  $R_{\text{eq}} = V_s/i_s$  loading the voltage source.

**1.41** For the bridge circuit shown in Fig. P1.39, when the current  $i = 0 \text{ A}$ , we say that the bridge

is **balanced**. Under what condition (find an expression relating  $R_1$  and  $R_2$ ) will this bridge be balanced?

**1.42** For the circuit shown in Fig. P1.42, find  $i_1$  when (a)  $K = 2$ , (b)  $K = 3$ , and (c)  $K = 4$ .

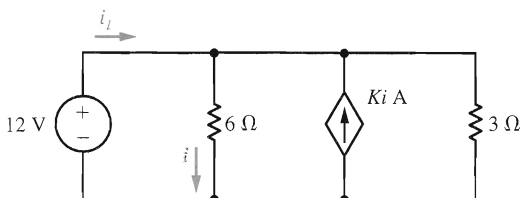


Fig. P1.42

**1.43** The circuit shown in Fig. P1.43 contains a **voltage-dependent voltage source** as well as a **current-dependent current source**. Find  $i_1$  when (a)  $K = -3$ , (b)  $K = -1.5$ , and (c)  $K = 1.5$ .

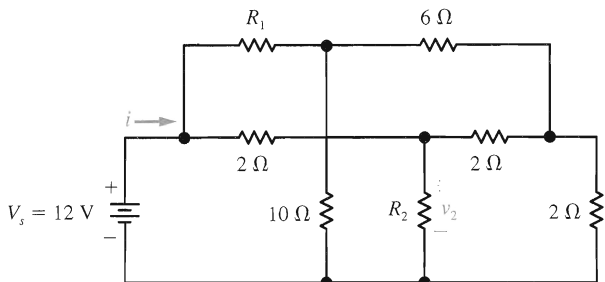


Fig. P1.37

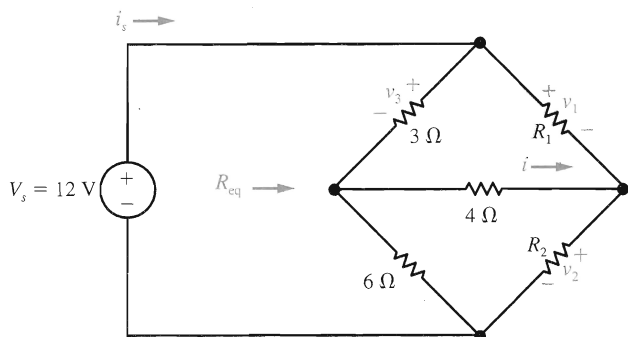


Fig. P1.39

**1.44** Consider the circuit shown in Fig. P1.44. Find  $v$  when (a)  $K = 2$ , and (b)  $K = 4$ .

**1.45** Consider the circuit shown in Fig. P1.45. Find  $i$  when (a)  $K = 2$ , and (b)  $K = 4$ .

**1.46** Consider the circuit shown in Fig. P1.46. (a) Find the resistance  $R_{eq} = v_1/i_1$ . (b) Find the voltage  $v_2$  in terms of the applied voltage  $v_1$ .

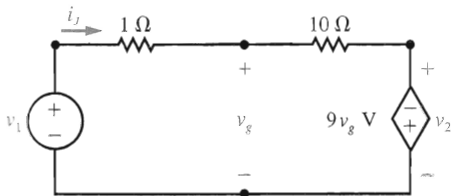


Fig. P1.46

**1.47** Consider the circuit shown in Fig. P1.47. (a) Find the resistance  $R_{eq} = v_1/i_1$ . (b) Use voltage division to find  $v$  in terms of  $v_g$ . (c) Find the voltage  $v_2$  in terms of the applied voltage  $v_1$ .

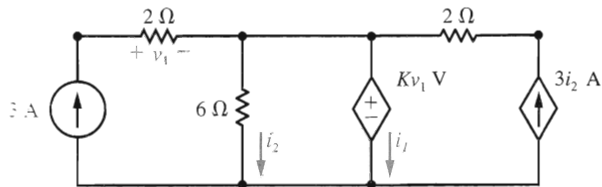


Fig. P1.43

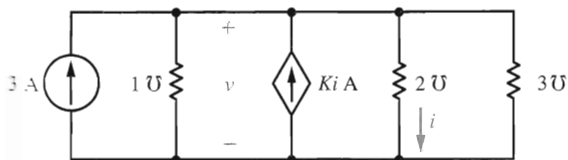


Fig. P1.44

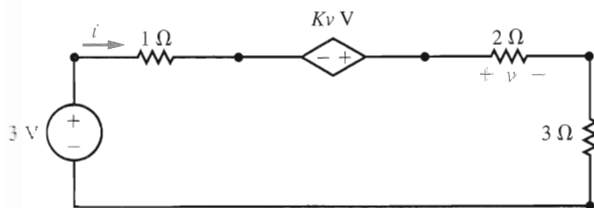


Fig. P1.45

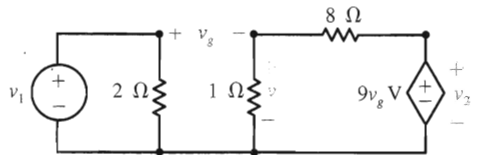


Fig. P1.47

**1.48** For the circuit shown in Fig. P1.48, suppose that  $R = 10 \Omega$ . Determine (a)  $v_s$ , and (b)  $R_{eq} = v_s/i_s$ .

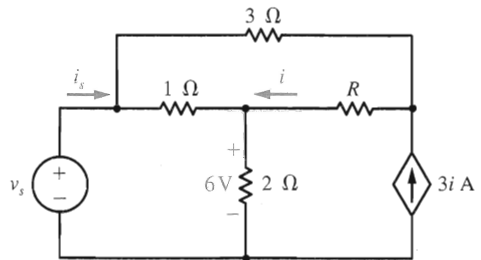


Fig. P1.48

**1.49** For the circuit shown in Fig. P1.48, suppose that  $R = 8 \Omega$ . Determine (a)  $v_s$ , and (b)  $R_{eq} = v_s/i_s$ .