

Fig. P2.17 a,b

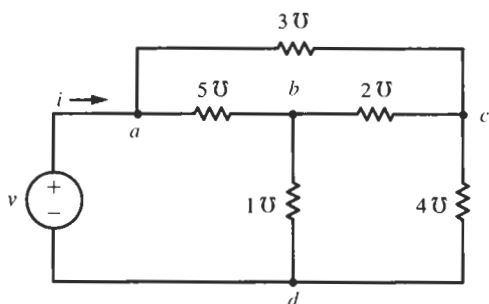


Fig. P2.17 c

$$R_A = \frac{R_{AB}R_{AC}}{R_{AB} + R_{AC} + R_{BC}} \quad R_B = \frac{R_{AB}R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_C = \frac{R_{AC}R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$

where  $R = 1/G$ . Such a process is called a  $\Delta$ -Y (delta-wye) transformation.

The circuit shown in Fig. P2.18 is identical to the circuit given in Fig. P2.16. Use a  $\Delta$ -Y transformation on the  $2\text{-}\mathcal{U}$ ,  $3\text{-}\mathcal{U}$ , and  $5\text{-}\mathcal{U}$  conductances, and then combine elements in series and parallel to determine  $G = i/v$ .

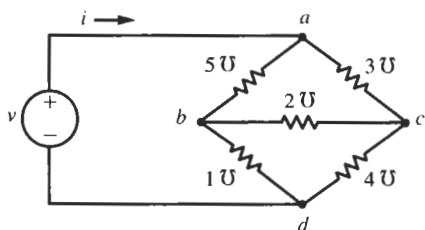


Fig. P2.18

**2.19** Find the mesh currents for the circuit shown in Fig. P2.19.

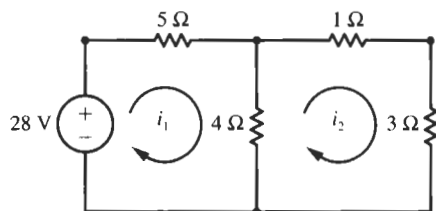


Fig. P2.19

**2.20** Assume clockwise mesh currents for the circuit shown in Fig. 2.9 on p. 64. Use mesh analysis to find these mesh currents.

**2.21** Assume clockwise mesh currents for the circuit shown in Fig. P2.7. Use mesh analysis to find these mesh currents.

**2.22** Assume clockwise mesh currents for the circuit shown in Fig. P2.9. Use mesh analysis to find these mesh currents.

**2.23** Assume clockwise mesh currents for the circuit shown in Fig. P2.10. Use mesh analysis to find these mesh currents.

**2.24** Use mesh analysis to find the conductance  $G = i/v$  for the circuit given in Fig. P2.18.

**2.25** Assume clockwise mesh currents for the circuit shown in Fig. P2.8. Use mesh analysis to find these mesh currents.

**2.26** Assume clockwise mesh currents for the circuit shown in Fig. P2.26 (below). Use mesh analysis to find these mesh currents.

**2.27** For the circuit shown in Fig. P2.27, find  $v_o$  when the ideal amplifier (a) is an op amp, and (b) has finite gain  $A$ .

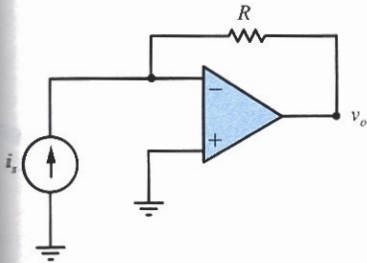


Fig. P2.27

**2.28** For the op-amp circuit shown in Fig. P2.28, find (a)  $v_o$ , and (b)  $i_o$ .

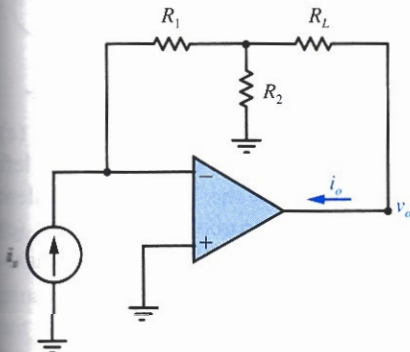


Fig. P2.28

**2.29** For the op-amp circuit shown in Fig. P2.29, find (a)  $v_o$ , and (b)  $i_o$ .

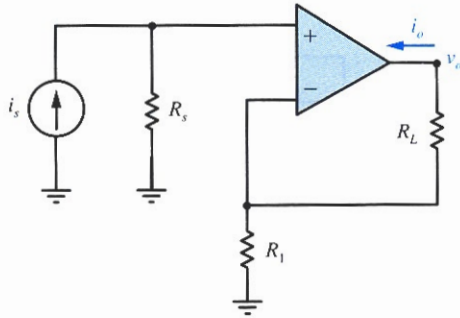


Fig. P2.29

**2.30** The op-amp circuit shown in Fig. P2.30 is known as a **negative-impedance converter**. For this circuit, find (a)  $v_o$ , and (b) the resistance  $v_s/i_s$ .

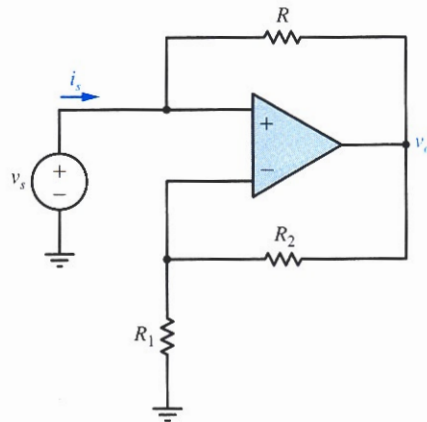


Fig. P2.30

**2.31** For the op-amp circuit shown in Fig. P2.31, find (a)  $v_o$ , and (b) the resistance  $v_s/i_s$ . (See p. 104.)

**2.32** For the op-amp circuit shown in Fig. P2.31, interchange the 1- $\Omega$  and 2- $\Omega$  resistors, and find (a)  $v_o$ , and (b) the resistance  $v_s/i_s$ . (See p. 104.)

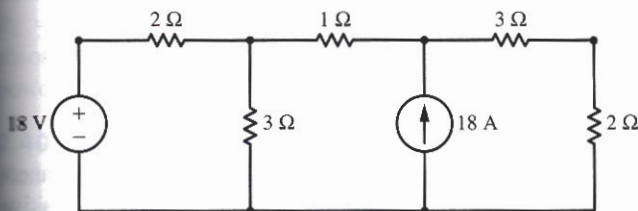


Fig. P2.26