

Fig. P3.60

**3.63** For the series  $RLC$  circuit shown in Fig. P3.63, suppose that  $R = 7 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 0.1 \text{ F}$ ,  $v_s(t) = 12 \text{ V}$  for  $t < 0 \text{ s}$  and  $v_s(t) = 0 \text{ V}$  for  $t \geq 0 \text{ s}$ . Find  $v(t)$  and  $i(t)$  for all time.

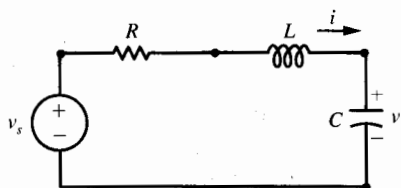


Fig. P3.63

**3.64** For the series  $RLC$  circuit shown in Fig. P3.63, suppose that  $R = 2 \Omega$ ,  $L = 0.25 \text{ H}$ ,  $C = 0.2 \text{ F}$ ,  $v_s(t) = 10 \text{ V}$  for  $t < 0 \text{ s}$  and  $v_s(t) = 0 \text{ V}$  for  $t \geq 0 \text{ s}$ . Find  $v(t)$  and  $i(t)$  for all time.

**3.65** For the series  $RLC$  circuit shown in Fig. P3.63, suppose that  $R = 2 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1 \text{ F}$ ,  $v_s(t) = 6 \text{ V}$  for  $t < 0 \text{ s}$  and  $v_s(t) = 0 \text{ V}$  for  $t \geq 0 \text{ s}$ . Find  $v(t)$  and  $i(t)$  for all time.

**3.66** For the circuit shown in Fig. P3.66, suppose that  $v_s(t) = 6 \text{ V}$  for  $t < 0 \text{ s}$  and  $v_s(t) = 0 \text{ V}$  for  $t \geq 0 \text{ s}$ . Find  $v_2(t)$  and  $v_1(t)$  for all time.

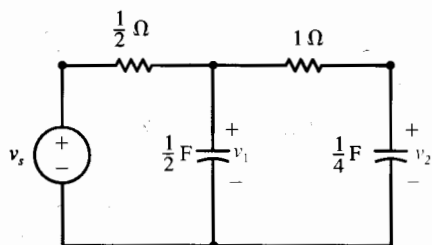


Fig. P3.66

**3.67** For the circuit shown in Fig. P3.67, suppose that  $v_s(t) = 6 \text{ V}$  for  $t < 0 \text{ s}$  and  $v_s(t) = 0 \text{ V}$  for  $t \geq 0 \text{ s}$ . Find  $i(t)$  and  $v(t)$  for all time.

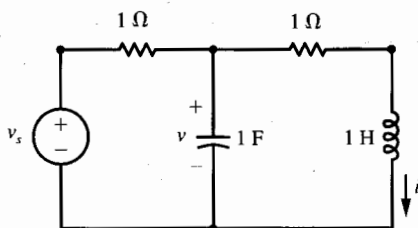


Fig. P3.67

**3.68** For the circuit shown in Fig. P3.67, interchange the inductor and the capacitor. Suppose that  $v_s(t) = 6 \text{ V}$  for  $t < 0 \text{ s}$  and  $v_s(t) = 0 \text{ V}$  for  $t \geq 0 \text{ s}$ . Find the capacitor voltage  $v(t)$  and the inductor current  $i(t)$  for all time.

**3.69** For the parallel  $RLC$  circuit shown in Fig. P3.69, suppose that  $R = 0.5 \Omega$ ,  $L = 0.2 \text{ H}$ ,  $C = 0.25 \text{ F}$  and  $i_s(t) = 2u(t) \text{ A}$ . Find the step responses  $i(t)$  and  $v(t)$ .

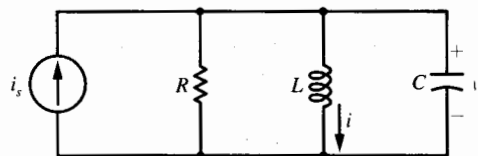


Fig. P3.69

**3.70** For the parallel  $RLC$  circuit shown in Fig. P3.69, suppose that  $R = 3 \Omega$ ,  $L = 3 \text{ H}$ ,  $C = \frac{1}{12} \text{ F}$  and  $i_s(t) = 4u(t) \text{ A}$ . Find the step responses  $i(t)$  and  $v(t)$ .

**3.71** For the series  $RLC$  circuit shown in Fig. P3.63, suppose that  $R = 7 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 0.1 \text{ F}$  and  $v_s(t) = 12u(t) \text{ V}$ . Find the step responses  $v(t)$  and  $i(t)$ .

**3.72** For the series  $RLC$  circuit shown in Fig. P3.63, suppose that  $R = 2 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 1 \text{ F}$

and  $v_s(t) = 12u(t)$  V. Find the step responses  $v(t)$  and  $i(t)$ .


**3.73** For the  $RLC$  circuit shown in Fig. 3.43 on p. 172, suppose that  $R = \frac{1}{2} \Omega$ ,  $L = \frac{1}{3}$  H,  $C = \frac{1}{4}$  F, and  $V = 1$  V. Find the unit step responses  $i(t)$  and  $v(t)$ .

**3.74** For the  $RLC$  circuit shown in Fig. 3.43 on p. 172, suppose that  $R = \frac{1}{2} \Omega$ ,  $L = \frac{1}{4}$  H,  $C = \frac{1}{2}$  F, and  $V = 1$  V. Find the unit step responses  $i(t)$  and  $v(t)$ .


**3.75** For the circuit shown in Fig. P3.66, suppose  $v_s(t) = 9u(t)$  V. Find the step response  $v_2(t)$ .

**3.76** For the circuit shown in Fig. P3.67, suppose  $v_s(t) = 6u(t)$  V. Find the step responses  $i(t)$  and  $v(t)$ .

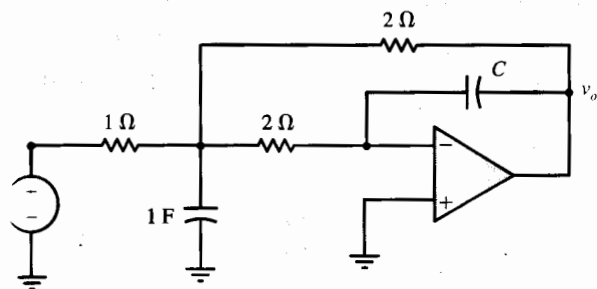**3.77** Find the step response  $v_o(t)$  for the op-amp circuit shown in Fig. P3.77 when  $C = \frac{1}{3}$  F and  $v_s(t) = 4u(t)$  V.



**P3.77**

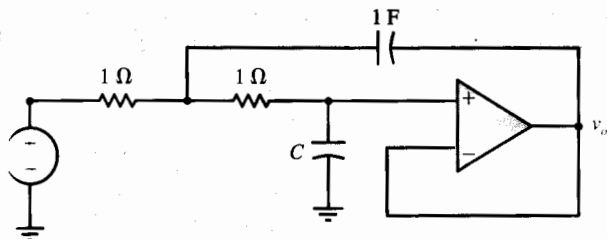

**P3.80**

**3.78** Find the step response  $v_o(t)$  for the op-amp circuit shown in Fig. P3.77 when  $C = \frac{1}{8}$  F and  $v_s(t) = 8u(t)$  V.

**3.79** Find the step response  $v_o(t)$  for the op-amp circuit shown in Fig. P3.77 when  $C = \frac{1}{4}$  F and  $v_s(t) = 6u(t)$  V.

**3.80** Find the step response  $v_o(t)$  for the op-amp circuit shown in Fig. P3.80 when  $C = \frac{4}{3}$  F and  $v_s(t) = 4u(t)$  V.

**3.81** Find the step response  $v_o(t)$  for the op-amp circuit shown in Fig. P3.80 when  $C = 1$  F and  $v_s(t) = 3u(t)$  V.

**3.82** Find the step response  $v_o(t)$  for the op-amp circuit shown in Fig. P3.80 when  $C = \frac{1}{5}$  F and  $v_s(t) = 2u(t)$  V.