

4. Important circuit concepts such as the principle of superposition and Thévenin's theorem are also applicable in the frequency domain.

5. The instantaneous power absorbed by an element is equal to the product of the voltage across it and the current through it.

6. The average power absorbed by a resistance R carrying a sinusoidal current of amplitude I and voltage of amplitude V is

$$P_R = \frac{1}{2}VI = \frac{1}{2}RI^2 = \frac{1}{2}\frac{V^2}{R}$$

7. The average power absorbed by a capacitance or an inductance is zero.

8. A circuit whose Thévenin-equivalent (output) impedance is Z_o transfers maximum power to a load Z_L when Z_L is equal to the complex conjugate of Z_o .

9. For the case in which Z_L is restricted to be purely resistive, maximum power is transferred when Z_L equals the magnitude of Z_o .

10. The effective or rms value of a sinusoid of amplitude A is $A/\sqrt{2}$.

Problems

4.1 Find the exponential form of the following complex numbers given in rectangular form: (a) $4 + j7$, (b) $3 - j5$, (c) $-2 + j3$, (d) $-1 - j6$, (e) $4j$, (f) -5 , (g) $j7$, (h) $-j2$.

4.2 Find the rectangular form of the following complex numbers given in exponential form:

(a) $3e^{j70^\circ}$, (b) $2e^{j120^\circ}$, (c) $5e^{-j60^\circ}$, (d) $4e^{-j150^\circ}$, (e) $6e^{j90^\circ}$, (f) e^{-j90° , (g) $2e^{j180^\circ}$, (h) $2e^{-j180^\circ}$.

4.3 Find the rectangular form of the product A_1A_2 given that: (a) $A_1 = 3e^{j30^\circ}$, $A_2 = 4e^{j60^\circ}$, (b) $A_1 = 5e^{j45^\circ}$, $A_2 = 4e^{-j30^\circ}$, (c) $A_1 = 5e^{-j60^\circ}$, $A_2 = 2e^{j120^\circ}$, (d) $A_1 = 4e^{j45^\circ}$, $A_2 = 2e^{-j90^\circ}$.

4.4 Find the rectangular form of the quotient A_2/A_1 for A_1 and A_2 given in Problem 4.3.

12. The average power absorbed by a resistance R having a current whose effective value is I_e and a voltage whose effective value is V_e is

$$P_R = VI_e = RI_e^2 = \frac{V_e^2}{R}$$

13. The power factor (pf) is the ratio of average power to apparent power:

14. If current lags voltage, the pf is lagging. If current leads voltage, the pf is leading.

15. Average or real power can be generalized with the notion of complex power:

16. The ordinary household uses a single-phase, three-wire electrical system.

17. The most common polyphase electrical system is the balanced three-phase system.

18. Three-phase sources are generally Y connected, and three-phase loads are generally Δ connected.

19. The device commonly used to measure power is the wattmeter.

20. Three-phase load power measurements can be taken with the two-wattmeter method.

4.5 Find the rectangular form of the sum $A_1 + A_2$ for A_1 and A_2 given in Problem 4.3.

4.6 For the ac circuit shown in Fig. P4.6, suppose that $v_s(t) = 13 \cos(2t - 22.6^\circ)$ V. Find $v_o(t)$ by using voltage division. Draw a phasor diagram. Is this circuit a lag network or a lead network?

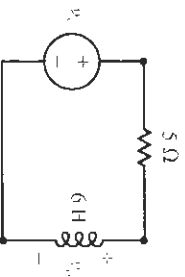


Fig. P4.6

4.7 Connect a $5\text{-}\Omega$ resistor in parallel with the inductor in the circuit shown in Fig. P4.6. Suppose that $v_s(t) = 13 \cos(2t - 22.6^\circ)$ V. Find the voltage $v_o(t)$ across the inductor by using voltage division. Draw a phasor diagram. Is this circuit a lag network or a lead network?

4.8 Connect a $5\text{-}\Omega$ resistor in parallel with the inductor in the circuit shown in Fig. P4.6. Suppose that $v_s(t) = 13 \cos(2t - 22.6^\circ)$ V. Find the voltage $v_o(t)$ across the inductor by using nodal analysis. Draw a phasor diagram. Is this circuit a lag network or a lead network?

4.9 For the circuit given in Fig. P4.9, suppose that $i_s(t) = 5 \cos 3t$ A. Find $v_o(t)$ and $v_s(t)$ by using current division.

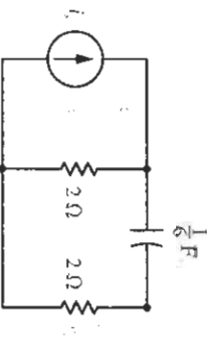


Fig. P4.9

4.10 For the circuit given in Fig. P4.9, suppose that $i_s(t) = 5 \cos 3t$ A. Find $v_o(t)$ and $v_s(t)$ by using nodal analysis.

4.11 A voltage of $v_s(t) = 10 \cos \omega t$ V is applied to a series RLC circuit. If $R = 5 \text{ }\Omega$, $L = \frac{1}{3}$ H, and $C = \frac{1}{3}$ F, by how many degrees does $v_c(t)$ lead or lag $v_s(t)$ when (a) $\omega = 1 \text{ rad/s}$, (b) $\omega = 5 \text{ rad/s}$, and (c) $\omega = 10 \text{ rad/s}$?

4.12 A voltage of $v_s(t) = 10 \cos \omega t$ V is applied to a series RLC circuit. If $R = 5 \text{ }\Omega$, $L = \frac{1}{3}$ H, and $C = \frac{1}{3}$ F, by how many degrees does $v_R(t)$ lead or lag $v_s(t)$ when (a) $\omega = 1 \text{ rad/s}$, (b) $\omega = 5 \text{ rad/s}$, and (c) $\omega = 10 \text{ rad/s}$?

4.13 For the RLC connection given in Fig. P4.13, find the impedance Z when ω is (a) 2, (b) 4, and (c) 8 rad/s.

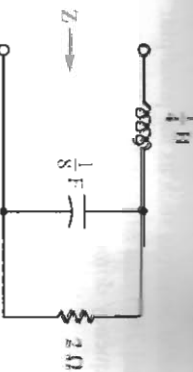


Fig. P4.13

4.14 For the RLC connection shown in Fig. P4.14, find the admittance Y when ω is: (a) 1, (b) 3, and (c) 7 rad/s.

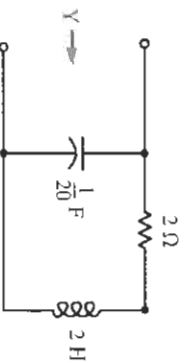


Fig. P4.14

4.15 Show that a general expression for the impedance Z depicted in Fig. P4.13 is

$$Z = \frac{32}{\omega^2 + 16} + j \frac{\omega(\omega^2 - 16)}{4(\omega^2 + 16)}$$

4.16 Show that a general expression for the admittance Y depicted in Fig. P4.14 is

$$Y = \frac{1}{2(\omega^2 + 1)} + j \frac{\omega(\omega^2 - 9)}{20(\omega^2 + 1)}$$

4.17 For the circuit shown in Fig. P4.17, find the Thévenin equivalent of the circuit in the shaded box when $v_s(t) = 4 \cos(4t - 60^\circ)$ V. Use this to determine $v_o(t)$.

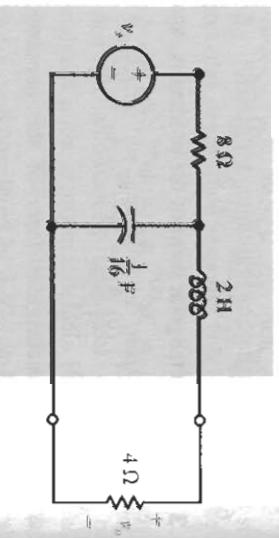


Fig. P4.17

4.18 For the circuit shown in Fig. P4.17, find the Thévenin equivalent of the circuit in the shaded box when $v_o(t) = 4 \cos(2t - 60^\circ)$ V. Use this to determine $v_o(t)$.

4.19 Find the frequency-domain Thévenin equivalent (to the left of terminals a and b) of the circuit shown in Fig. 4.20 on p. 211. (Hint: Use the fact that $Z_{oc} = V_{oc}/I_{sc}$.)

4.20 The frequency-domain Thévenin equivalent of a circuit having $\omega = 5$ rad/s has $V_{oc} = 3.7\sqrt{-15.9^\circ}$ V and $Z_{oc} = 2.38 - j0.667 \Omega$. Determine a corresponding time-domain Thévenin-equivalent circuit.

4.21 For the op-amp circuit shown in Fig. P4.21, find $v_o(t)$ when $v_s(t) = 6 \sin 2t$ V.

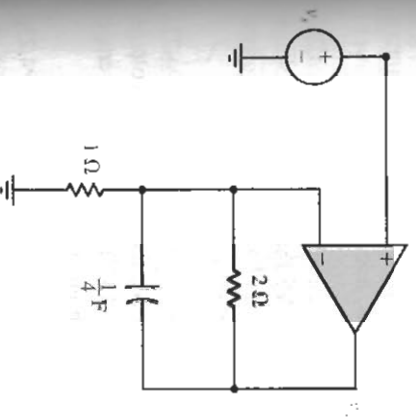


Fig. P4.21

4.22 For the op-amp circuit given in Fig. P4.22, find $v_o(t)$ when $v_s(t) = 3 \cos 2t$ V.

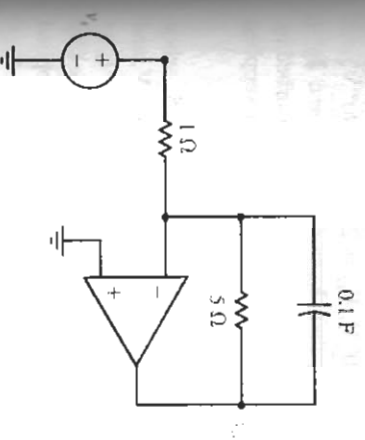


Fig. P4.22

4.23 For the op-amp circuit shown in Fig. P4.23, find $v_o(t)$ when $v_s(t) = 4 \cos(2t - 30^\circ)$ V. (See p. 258.)

4.24 For the circuit shown in Fig. P4.24, find the currents I_1 and I_2 when $V_{s1} = 250\sqrt{2}/\angle -30^\circ$ V, $V_{s2} = 250\sqrt{2}/\angle -90^\circ$ V, and $Z = 78 - j45 \Omega$.

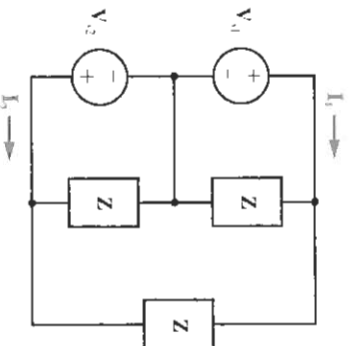


Fig. P4.24

4.25 Use mesh analysis to find I_1 and I_2 for the circuit given in Fig. P4.25 when $V_{s1} = 250\sqrt{2}/\angle -30^\circ$ V, $V_{s2} = 250\sqrt{2}/\angle -90^\circ$ V, and $Z = 26 - j15 \Omega$.

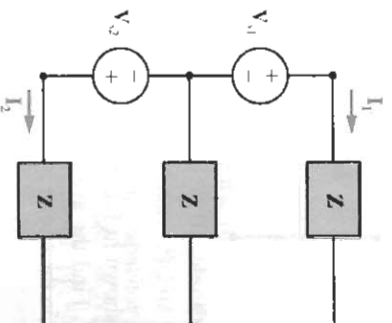


Fig. P4.25

4.26 For the circuit shown in Fig. P4.9, when $i_s(t) = 5 \cos 3t$ A then $v_o(t) = 4.47 \cos(3t + 26.6^\circ)$ V. Find the average power absorbed by each element in the circuit.

4.27 For the circuit shown in Fig. P4.17, when $v_s(t) = 10 \cos 4t$ V, then the Thévenin equivalent of the portion of the circuit in the shaded box is $V_{oc} =$

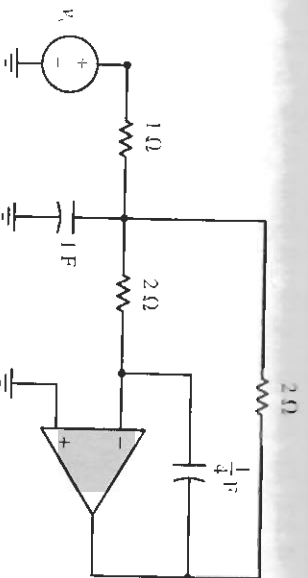


Fig. P4.23

4.47/−63.4° V and $Z_{L_0} = 1.6 + j4.8 \Omega$. (a) Replace the $4\text{-}\Omega$ load resistor by an impedance Z_{L_1} that absorbs the maximum average power, and determine this maximum power. (b) Replace the $4\text{-}\Omega$ load resistor with a resistance R_L that absorbs the maximum power for resistive loads, and determine this power.

4.28 For the RLC circuit shown in Fig. P4.28, suppose that $v_s(t) = 10 \cos 3t$ V. Find the average power absorbed by the $4\text{-}\Omega$ resistor for the case that (a) $C = \frac{1}{6}$ F; (b) $C = \frac{1}{18}$ F; (c) $C = \frac{1}{30}$ F.

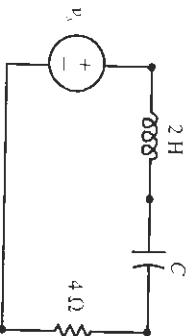


Fig. P4.28

4.29 For the circuit shown in Fig. P4.29, suppose that $v_s(t) = 8 \cos 2t$ V. Find the average power absorbed by each element in the circuit for the case that $Z_{L_0} = 1 \Omega$.

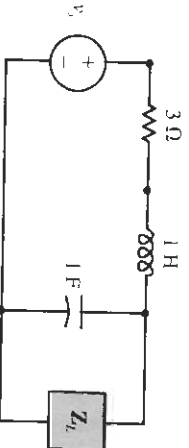


Fig. P4.29

4.30 For the circuit shown in Fig. P4.29, change the value of the resistor to 2Ω and the value of the capacitor to $\frac{1}{4}$ F. Suppose that $v_s(t) = 8 \cos 2t$ V. (a) Find the load impedance Z_L that absorbs the maximum average power, and determine this power. (b) Find the load resistance R_L that absorbs the maximum power for resistive loads, and determine this power.

4.31 For the op-amp circuit given in Fig. P4.21, when $v_s(t) = 6 \sin 2t$ V, then the output voltage $v_o(t) = 13.4 \cos(2t - 117^\circ)$ V. Find the average power absorbed by each element.

4.32 For the op-amp circuit given in Fig. P4.22, when $v_s(t) = 3 \cos 2t$ V, then the output voltage $v_o(t) = 10.6 \cos(2t + 135^\circ)$ V. Find the average power absorbed by each element.

4.33 For the op-amp circuit given in Fig. P4.23, when $v_s(t) = 4 \cos(2t - 30^\circ)$ V, then $v_1(t) = 1.6 \cos(2t - 66.9^\circ)$ V and $v_o(t) = 1.6 \cos(2t + 23.1^\circ)$ V. Find the average power absorbed by each element.

4.34 For the circuit given in Fig. P4.24, when $V_{s1} = 250\sqrt{2}/\angle -30^\circ$ V, $V_{s2} = 250\sqrt{2}/\angle -90^\circ$ V, and $Z = 78 - j45 \Omega$, then $I_1 = 6.8/\angle 30^\circ$ A and $I_2 = 6.8/\angle -90^\circ$ A. (a) Find the average power absorbed by each impedance. (b) Find the average power supplied by each source.

4.35 For the circuit given in Fig. P4.25, when $V_{s1} = 250\sqrt{2}/\angle -30^\circ$ V, $V_{s2} = 250\sqrt{2}/\angle -90^\circ$ V, and $Z = 26 - j15 \Omega$, then $I_1 = 6.8/\angle 30^\circ$ A and $I_2 = 6.8/\angle -90^\circ$ A. (a) Find the average power absorbed by each impedance. (b) Find the average power supplied by each source.