

Problems


1 An ideal voltage source is described by the function $v(t) = 10e^{-t}$ V. Find the value of this voltage source when (a) $t = 0$ s, (b) $t = 1$ s, (c) $t = 2$ s, (d) $t = 3$ s, (e) $t = 4$ s.

2 An ideal voltage source is described by the function $v(t) = 5 \sin(\pi/2)t$ V. Find the value of this voltage source when (a) $t = 0$ s, (b) $t = 1$ s, (c) $t = 2$ s, (d) $t = 3$ s, and (e) $t = 4$ s.

3 An ideal voltage source is described by the function $v(t) = 3 \cos(\pi/2)t$ V. Find the value of this voltage source when (a) $t = 0$ s, (b) $t = 1$ s, (c) $t = 2$ s, (d) $t = 3$ s, and (e) $t = 4$ s.

4 Find the current in a region when the total charge in the region is described by the function $q(t) = 4e^{-2t}$ C, (b) $q(t) = 3 \sin \pi t$ C, (c) $q(t) = -2\pi t$ C, and (d) $q(t) = 5e^{-4t} \cos 3t$ C.

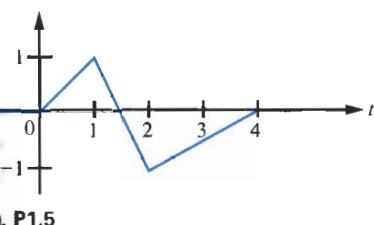5 An ideal voltage source is described by the function shown in Fig. P1.5. Find the value of this voltage source when (a) $t = 0$ s, (b) $t = 1$ s, (c) $t = 2$ s, (d) $t = 3$ s, and (e) $t = 4$ s.



6 The total charge $q(t)$ in some region is described by the function shown in Fig. P1.5. Sketch the current $i(t)$ in this region.

1.7 Consider the circuit shown in Fig. P1.7. (a) Given $i_1 = 4$ A, find v_1 . (b) Given $i_2 = -2$ A, find v_2 . (c) Given $i_3 = 2$ A, find v_3 . (d) Given $i_4 = -2$ A, find v_4 .

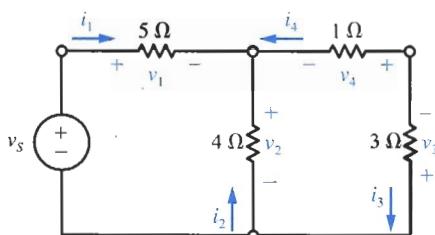


Fig. P1.7

1.8 Consider the circuit in Fig. P1.7. (a) Given $v_1 = 30$ V, find i_1 . (b) Given $v_2 = 12$ V, find i_2 . (c) Given $v_3 = -9$ V, find i_3 . (d) Given $v_4 = -3$ V, find i_4 .

1.9 Consider the circuit shown in Fig. P1.7. (a) Given $v_1 = -10$ V, find i_1 . (b) Given $i_2 = 1$ A, find v_2 . (c) Given $v_3 = 3$ V, find i_3 . (d) Given $i_4 = 1$ A, find v_4 .

1.10 Consider the circuit in Fig. P1.10. (a) Given $v_1 = -6$ V, find i_1 . (b) Given $v_2 = 24$ V, find i_2 . (c) Given $v_3 = 11$ V, find i_3 . (d) Given $v_4 = 21$ V, find i_4 . (e) Given $v_5 = -14$ V, find i_5 .

1.11 Consider the circuit shown in Fig. P1.10. (a) Given $i_1 = 1.5$ A, find v_1 . (b) Given $i_2 = -4$ A, find v_2 . (c) Given $i_3 = 5.5$ A, find v_3 . (d) Given $i_4 = 3.5$ A, find v_4 . (e) Given $i_5 = 3.5$ A, find v_5 .

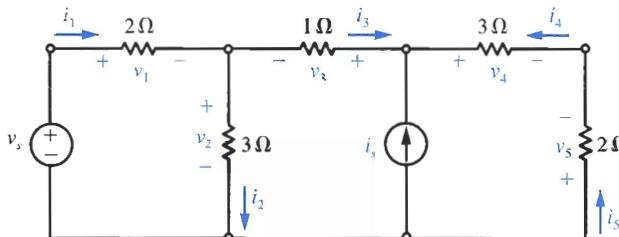


Fig. P1.10

- 1.12** Consider the circuit shown in Fig. P1.12. (a) Given $i_1 = -4 \text{ A}$, find v_1 . (b) Given $i_2 = 1 \text{ A}$, find v_2 . (c) Given $i_3 = 1 \text{ A}$, find v_3 . (d) Given $i_4 = 2 \text{ A}$, find v_4 .

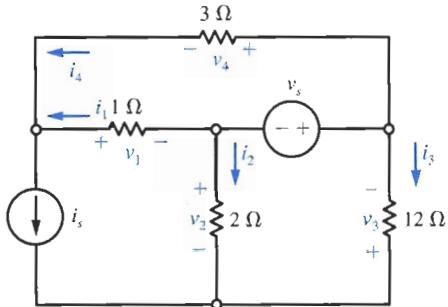


Fig. P1.12

- 1.13** Consider the circuit in Fig. P1.12. (a) Given $v_1 = -2 \text{ V}$, find i_1 . (b) Given $v_2 = -1 \text{ V}$, find i_2 . (c) Given $v_3 = -6 \text{ V}$, find i_3 . (d) Given $v_4 = 3 \text{ V}$, find i_4 .

- 1.14** Consider the circuit in Fig. P1.14. (a) Given $i_1 = 3 \text{ A}$ and $v_1 = 6 \text{ V}$, find R_1 . (b) Given $i_2 = 3 \text{ A}$ and $v_2 = -15 \text{ V}$, find R_2 . (c) Given $i_3 = -2 \text{ A}$ and $v_3 = 6 \text{ V}$, find R_3 . (d) Given $i_4 = -1 \text{ A}$ and $v_3 = 6 \text{ V}$, find R_4 .

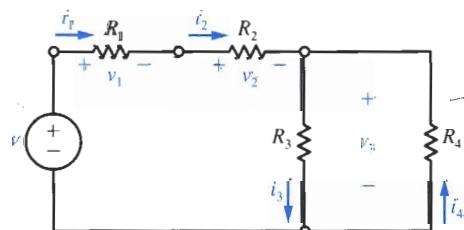


Fig. P1.14

- 1.15** Consider the circuit in Fig. P1.14. (a) Given $i_1 = 6 \text{ A}$ and $v_1 = 18 \text{ V}$, find R_1 . (b) Given $i_2 = 6 \text{ A}$ and $v_2 = -36 \text{ V}$, find R_2 . (c) Given $i_3 = 4 \text{ A}$ and $v_3 = 16 \text{ V}$, find R_3 . (d) Given $i_4 = -2 \text{ A}$ and $v_3 = 16 \text{ V}$, find R_4 .

- 1.16** For the circuit shown in Fig. P1.16, find v when (a) $i_s = 1 \text{ A}$, (b) $i_s = 2 \text{ A}$, (c) $i_s = 3 \text{ A}$.

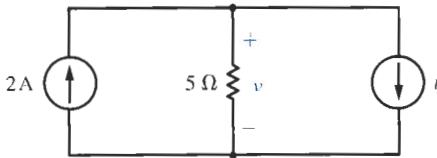


Fig. P1.16

- 1.17** For the circuit shown in Fig. P1.17, find i when (a) $v_s = 1 \text{ V}$, (b) $v_s = 2 \text{ V}$, (c) $v_s = 3 \text{ V}$.

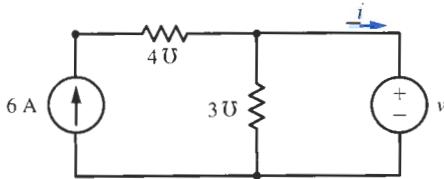


Fig. P1.17

- 1.18** For the circuit shown in Fig. P1.18, find v_4 when (a) $v_s = 2 \text{ V}$, (b) $v_s = 4 \text{ V}$, (c) $v_s = 6 \text{ V}$.

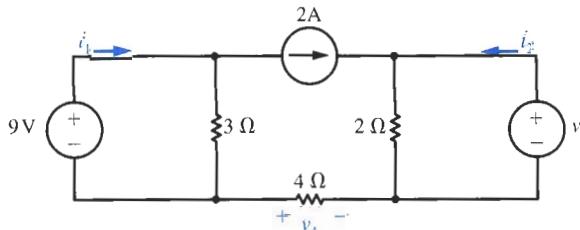


Fig. P1.18

- 1.19** For the circuit shown in Fig. P1.19, suppose that $i_1 = 6 \text{ A}$. Use the current-divider formula to determine i_2 , i_3 , i_4 , and i_5 .

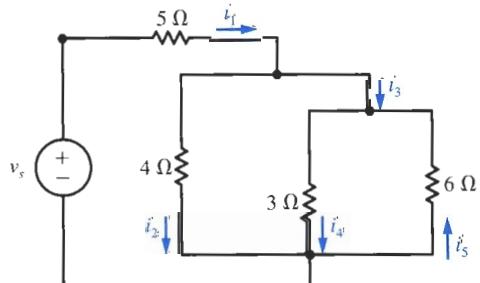


Fig. P1.19

- 1.20** For the circuit shown in Fig. P1.19, suppose that $i_4 = 4 \text{ A}$. Use the current-divider formula to determine i_1 , i_2 , i_3 , and i_5 .