

## Problems

**3.1** For the circuit shown in Fig. P3.1a, suppose that  $i(t)$  is described by the function given in Fig. P3.1b. Sketch (a)  $v(t)$ , (b)  $w_L(t)$ , (c)  $p_R(t)$ , (d)  $v_R(t)$ , and (e)  $v_s(t)$ .

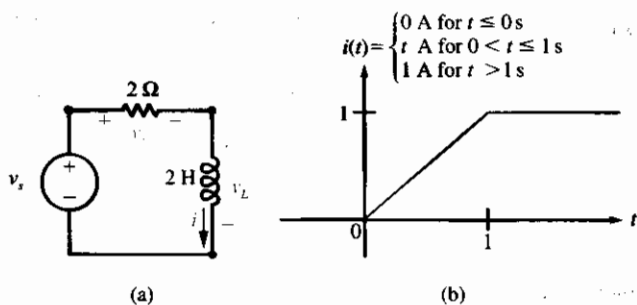


Fig. P3.1

**3.2** For the circuit shown in Fig. P3.1a, suppose that  $i(t)$  is described by the function given in Fig. P3.2. Sketch (a)  $v(t)$ , (b)  $w_L(t)$ , (c)  $p_R(t)$ , (d)  $v_R(t)$ , and (e)  $v_s(t)$ .

**3.3** For the circuit shown in Fig. P3.3, suppose that  $i(t)$  is described by the function given in Fig. P3.1b. Sketch (a)  $v(t)$ , (b)  $w_L(t)$ , (c)  $p_R(t)$ , (d)  $i_R(t)$ , and (e)  $i_s(t)$ .

**3.4** For the circuit shown in Fig. P3.3, suppose that  $i(t)$  is described by the function given in Fig. P3.2. Sketch (a)  $v(t)$ , (b)  $w_L(t)$ , (c)  $p_R(t)$ , (d)  $i_R(t)$ , and (e)  $i_s(t)$ .

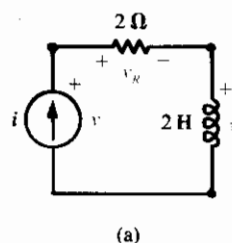


Fig. P3.5

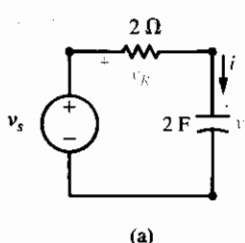


Fig. P3.7

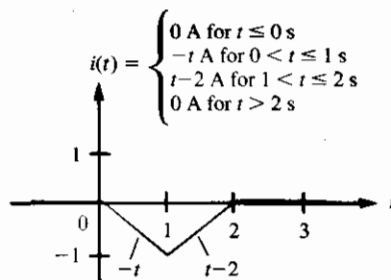


Fig. P3.2

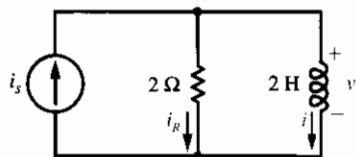



Fig. P3.3

**3.5** For the circuit shown in Fig. P3.5, suppose that  $i(t)$  is described by the function given in Fig. P3.1b. Sketch (a)  $v_R(t)$ , (b)  $v_L(t)$ , and (c)  $v(t)$ .

**3.6** For the circuit shown in Fig. P3.5, suppose that  $i(t)$  is described by the function given in Fig. P3.2. Sketch (a)  $v_R(t)$ , (b)  $v_L(t)$ , and (c)  $v(t)$ .

**3.7** For the circuit shown in Fig. P3.7a, suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $w_C(t)$ , (c)  $p_R(t)$ , (d)  $v_R(t)$ , and (e)  $v_s(t)$ .

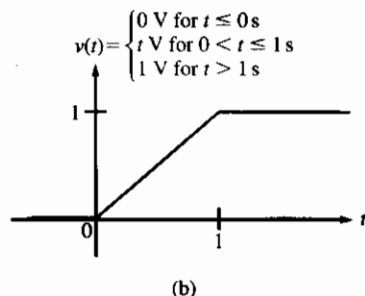**3.8** For the circuit shown in Fig. P3.8, suppose that  $v(t)$  is described by the function given in Fig. P3.7b.



Sketch (a)  $i(t)$ , (b)  $w_C(t)$ , (c)  $p_R(t)$ , (d)  $i_R(t)$ , and (e)  $i(t)$ .

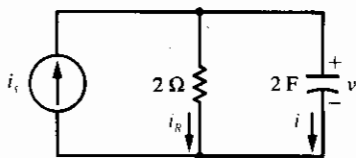


Fig. P3.8

**3.9** For the op-amp circuit shown in Fig. P3.9, suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

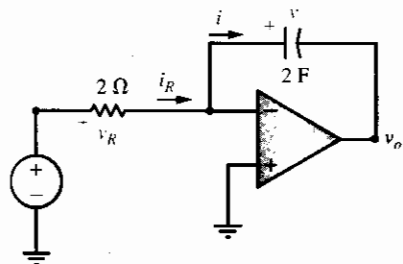


Fig. P3.9

**3.10** For the op-amp circuit shown in Fig. P3.9, connect an additional  $2\text{-}\Omega$  resistor in parallel with the capacitor. Suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

**3.11** For the op-amp circuit shown in Fig. P3.11, suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

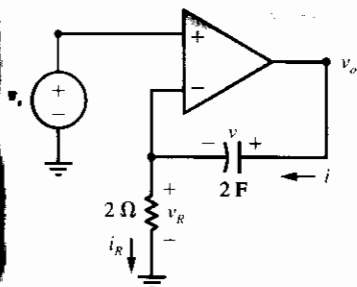


Fig. P3.11

**3.12** For the op-amp circuit given in Fig. P3.11, connect an additional  $2\text{-}\Omega$  resistor in parallel with the capacitor. Suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

**3.13** For the op-amp circuit shown in Fig. P3.13, suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

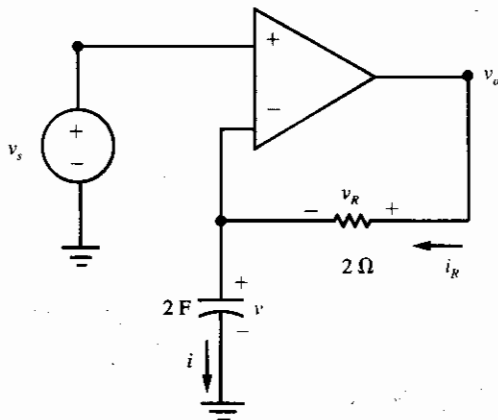


Fig. P3.13

**3.14** For the op-amp circuit shown in Fig. P3.13, connect an additional  $2\text{-}\Omega$  resistor in parallel with the capacitor. Suppose that  $v(t)$  is described by the function given in Fig. P3.7b. Sketch (a)  $i(t)$ , (b)  $i_R(t)$ , (c)  $v_R(t)$ , (d)  $v_s(t)$ , and (e)  $v_o(t)$ .

**3.15** Show the following: (See p. 178.)

- Inductors connected in series can be combined as depicted in Fig. P3.15a.
- Inductors connected in parallel can be combined as depicted in Fig. P3.15b.
- Capacitors connected in parallel can be combined as depicted in Fig. P3.15c.
- Capacitors connected in series can be combined as depicted in Fig. P3.15d.

**3.16** For the circuit shown in Fig. P3.1a, suppose that  $v(t)$  is described by the function given in Fig. P3.16. Sketch (a)  $i(t)$ , (b)  $v_R(t)$ , and (c)  $v_s(t)$ . (See p. 178.)