
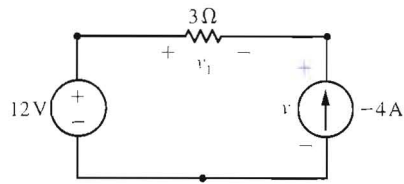



(a)

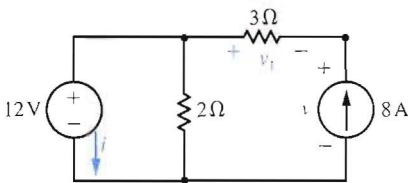

(b)




(c)

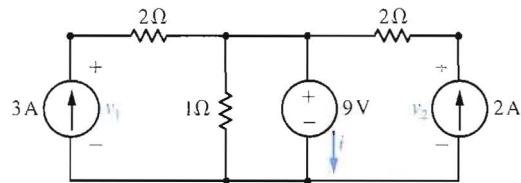


(d)


Fig. P1.26 a-d

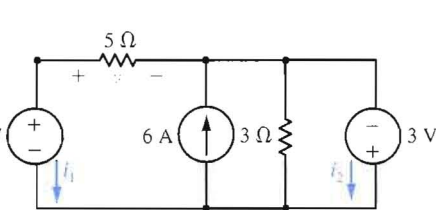

(a)

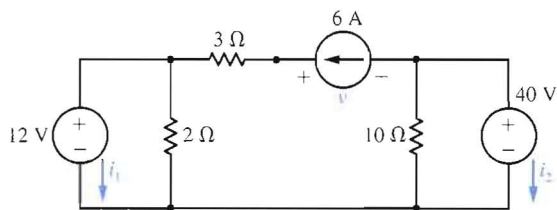

(b)

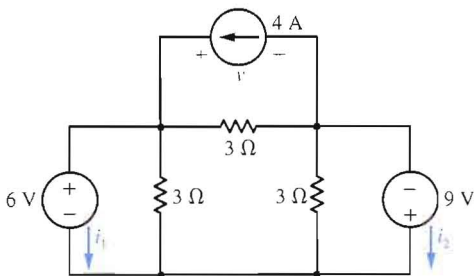

(c)

Fig. P1.27 a-c

**1.30** Find  $v$  and  $i$  for the series-parallel circuit shown in Fig. P1.30.

**1.31** Find  $v$  and  $i$  for the series-parallel circuit shown in Fig. P1.31.

**1.32** Consider the circuit shown in Fig. P1.32. (a) Find  $i$ ,  $v_1$ ,  $v_2$ , and  $v_3$ . (b) Remove the short circuit

between  $a$  and  $b$  (erase it), and find  $i$ ,  $v_1$ , and  $v_2$ . (Don't try to find  $v_3$ —it can't be done!)

**1.33** Consider the series-parallel circuit shown in Fig. P1.33. (a) Find  $V_s$  when  $v_1 = 2$  V. (b) Find  $V_s$  when  $i_3 = 3$  A. (c) Find  $V_s$  when  $i_5 = 4$  A. (d) What is the resistance  $R_{\text{eq}} = V_s/i$  loading the battery for part (a)? For part (b)? For part (c)?

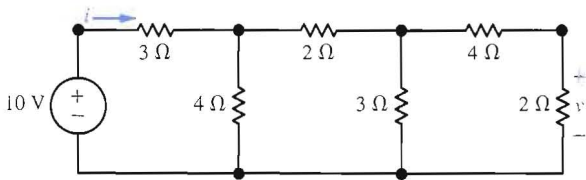


Fig. P1.30

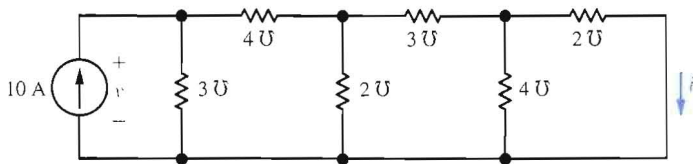


Fig. P1.31

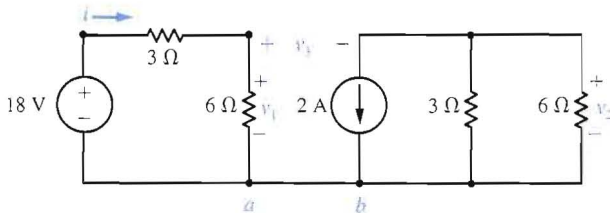


Fig. P1.32

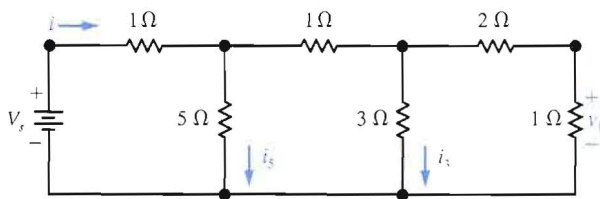


Fig. P1.33

**1.34** Consider the nonseries-parallel circuit shown in Fig. P1.34. (a) When  $R = \frac{1}{3} \Omega$ , then  $v_1 = 6 \text{ V}$ . Determine the resistance  $R_{\text{eq}} = V_s/i$  loading the battery.

**1.35** Consider the nonseries-parallel circuit shown in Fig. P1.34. When  $R = 4 \Omega$ , then  $v_1 = 4 \text{ V}$ . Determine the resistance  $R_{\text{eq}} = V_s/i$  loading the battery.

**1.36** Consider the nonseries-parallel circuit shown in Fig. P1.34. Determine  $R$  and the resistance  $R_{\text{eq}} = V_s/i$  loading the battery when  $v_1 = 3 \text{ V}$ .

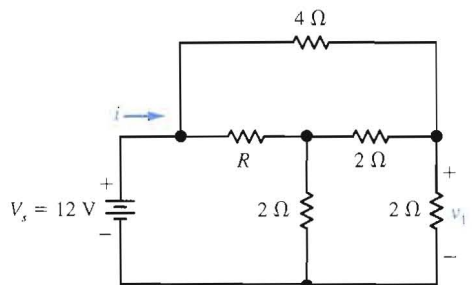


Fig. P1.34

**1.44** Consider the circuit shown in Fig. P1.44. Find  $v$  when (a)  $K = 2$ , and (b)  $K = 4$ .

**1.45** Consider the circuit shown in Fig. P1.45. Find  $i$  when (a)  $K = 2$ , and (b)  $K = 4$ .

**1.46** Consider the circuit shown in Fig. P1.46. (a) Find the resistance  $R_{eq} = v_1/i_1$ . (b) Find the voltage  $v_2$  in terms of the applied voltage  $v_1$ .

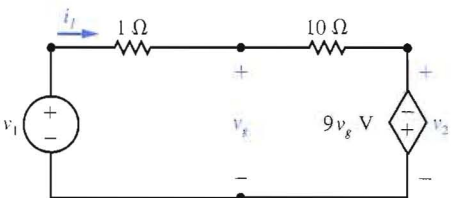


Fig. P1.46

**1.47** Consider the circuit shown in Fig. P1.47. (a) Find the resistance  $R_{eq} = v_1/i_1$ . (b) Use voltage division to find  $v$  in terms of  $v_g$ . (c) Find the voltage  $v_2$  in terms of the applied voltage  $v_1$ .

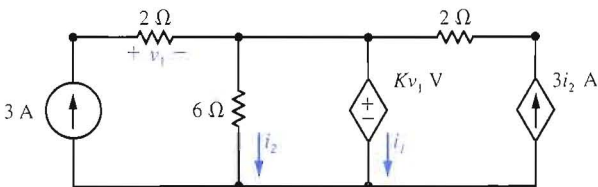


Fig. P1.43

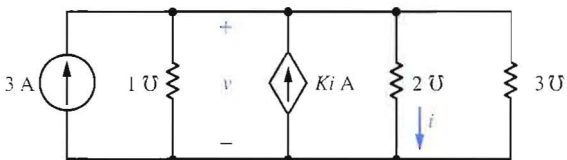


Fig. P1.44

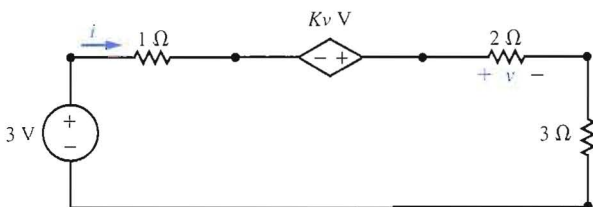


Fig. P1.45

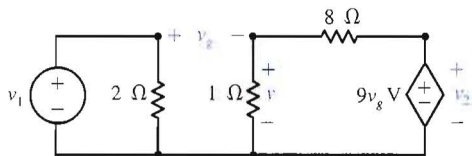


Fig. P1.47

**1.48** For the circuit shown in Fig. P1.48, suppose that  $R = 10 \Omega$ . Determine (a)  $v_s$ , and (b)  $R_{eq} = v_s/i_s$ .


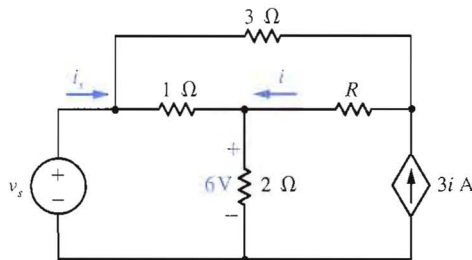


Fig. P1.48

**1.49** For the circuit shown in Fig. P1.48, suppose that  $R = 8 \Omega$ . Determine (a)  $v_s$ , and (b)  $R_{eq} = v_s/i_s$ .


**1.50** For the circuit shown in Fig. P1.50, suppose that  $R = 5 \Omega$ . Determine (a)  $i_s$ , and (b)  $R = v_s/i_s$ .

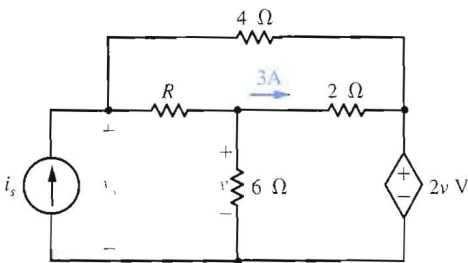


**Fig. P1.50**

**1.51** For the circuit shown in Fig. P1.50, suppose that  $R = 3 \Omega$ . Determine (a)  $i_s$ , and (b)  $R_{\text{cq}} = v_s/i_s$ .

**1.52** The circuit shown in Fig. P1.52 is a single field-effect transistor (FET) amplifier in which the input is  $v_1$  and the output is  $v_2$ . The portion of the circuit in the shaded box is an approximate model of an FET. (a) Find  $v_{gs}$  in terms of  $v_1$ . (b) Find  $v_2$  in terms of  $v_1$ . (c) Find  $v_2$  when  $v_1 = 0.1 \cos 120\pi t$  V.

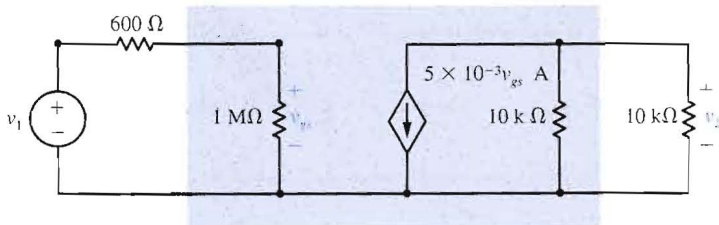

**Fig. P1.52**

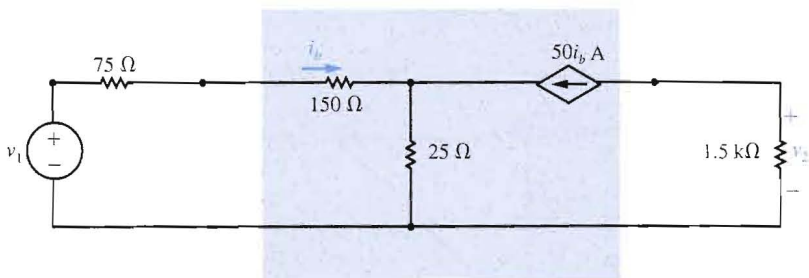

**Fig. P1.53**

**1.53** The circuit shown in Fig. P1.53 is a single bipolar junction transistor (BJT) amplifier in which the input is  $v_1$  and the output is  $v_2$ . The portion of the circuit in the shaded box is an approximate model of a BJT in the common-emitter configuration. (a) Find  $i_b$  in terms of the input voltage  $v_1$ . (b) Find the output voltage  $v_2$  in terms of  $v_1$ . (c) Find  $v_2$  when  $v_1 = 0.1 \cos 120\pi t$  V.

**1.54** The circuit shown in Fig. P1.54 is another single bipolar junction transistor (BJT) amplifier in which the input is  $v_1$  and the output is  $v_2$ . The portion in the shaded box is an approximate model of a BJT in the common-base configuration. (a) Find  $i_e$  in terms of the input voltage  $v_1$ . (b) Find the output voltage  $v_2$  in terms of  $v_1$ . (c) Find  $v_1$  when  $v_1 = 0.1 \cos 120\pi t$  V.

**1.55** For the circuit given in Fig. 1.51 on p. 34,  $v = 12$  V,  $i_1 = 4$  A, and  $i_2 = 6$  A. Determine the power absorbed by each element in the circuit.

**1.56** For the circuit given in Fig. 1.52 on p. 36,  $v = 24$  V. Determine the power absorbed by each element in the circuit.