

Fig. P5.54

- 5.60** Find the Laplace transform of (a)  $\sin(\beta t - \phi)u(t)$ , (b)  $\cos(\beta t - \phi)u(t)$ , (c)  $e^{-\alpha t} \sin(\beta t - \phi)u(t)$ , and (d)  $e^{-\alpha t} \cos(\beta t - \phi)u(t)$ .

- 5.61** Find the inverse Laplace transform of each of the following functions:

(a)  $\frac{600}{s(s+10)(s+30)}$     (b)  $\frac{60(s+4)}{s(s+2)(s+12)}$

- 5.62** Find the inverse Laplace transform of each of the following functions:

(a)  $\frac{12s}{(s+3)(s^2+9)}$     (b)  $\frac{4(s^2+1)}{s(s^2+4)}$

- 5.63** Find the inverse Laplace transform of each of the following functions:

(a)  $\frac{(s+2)(s+3)}{s(s+1)^2}$     (b)  $\frac{10s+80}{s^2+8s+20}$

- 5.64** Find the solution to the differential equation

$$\frac{d^2x(t)}{dt^2} + 7\frac{dx(t)}{dt} + 6x(t) = 36u(t)$$

subject to the initial conditions  $dx(0)/dt = 0$  and  $x(0) = -4$ .

- 5.65** Find the solution to the differential equation

$$\frac{d^2x(t)}{dt^2} + 3\frac{dx(t)}{dt} + 2x(t) = 20 \cos 2t u(t)$$

subject to the zero initial conditions  $dx(0)/dt = x(0) = 0$ .

- 5.66** For the series  $RC$  circuit shown in Fig. P5.66, suppose that  $R = 5 \Omega$  and  $C = 0.1 \text{ F}$ . Find the step responses  $v(t)$  and  $i(t)$  when  $v_s(t) = 20u(t) \text{ V}$ .

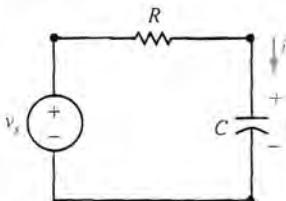


Fig. P5.66

- 5.67** For the series  $RC$  circuit shown in Fig. P5.66, suppose that  $R = 2 \Omega$  and  $C = 2 \text{ F}$ . Find  $v(t)$  and  $i(t)$  when  $v_s(t) = 12e^{-t/2}u(t) \text{ V}$ .

- 5.68** For the series  $RC$  circuit shown in Fig. P5.66, suppose that  $R = 2 \Omega$  and  $C = 2 \text{ F}$ . Find  $v(t)$  and  $i(t)$  when  $v_s(t) = 12e^{-t/4}u(t) \text{ V}$ .

- 5.69** For the series  $RL$  circuit shown in Fig. P5.69, suppose that  $R = 5 \Omega$  and  $L = 5 \text{ H}$ . Find the step responses  $i(t)$  and  $v(t)$  when  $v_s(t) = 20u(t) \text{ V}$ .

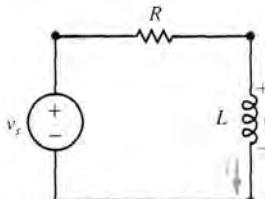


Fig. P5.69