

1. Problem 3.67
2. Problem 3.68
3. Consider the circuit shown below where the switch changes from position  $a$  to position  $b$  at time  $t = 0$  sec. Find the capacitor's voltage  $v(t)$  and inductor's current  $i(t)$  for all time.

