

Fig. P3.60

3.63 For the series RLC circuit shown in Fig. P3.63, suppose that $R = 7 \Omega$, $L = 1 \text{ H}$, $C = 0.1 \text{ F}$, $v_s(t) = 12 \text{ V}$ for $t < 0 \text{ s}$ and $v_s(t) = 0 \text{ V}$ for $t \geq 0 \text{ s}$. Find $v(t)$ and $i(t)$ for all time.

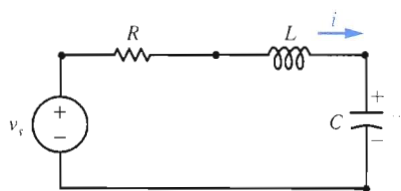


Fig. P3.63

3.64 For the series RLC circuit shown in Fig. P3.63, suppose that $R = 2 \Omega$, $L = 0.25 \text{ H}$, $C = 0.2 \text{ F}$, $v_s(t) = 10 \text{ V}$ for $t < 0 \text{ s}$ and $v_s(t) = 0 \text{ V}$ for $t \geq 0 \text{ s}$. Find $v(t)$ and $i(t)$ for all time.

3.65 For the series RLC circuit shown in Fig. P3.63, suppose that $R = 2 \Omega$, $L = 1 \text{ H}$, $C = 1 \text{ F}$, $v_s(t) = 6 \text{ V}$ for $t < 0 \text{ s}$ and $v_s(t) = 0 \text{ V}$ for $t \geq 0 \text{ s}$. Find $v(t)$ and $i(t)$ for all time.

3.66 For the circuit shown in Fig. P3.66, suppose that $v_s(t) = 6 \text{ V}$ for $t < 0 \text{ s}$ and $v_s(t) = 0 \text{ V}$ for $t \geq 0 \text{ s}$. Find $v_2(t)$ and $v_1(t)$ for all time.

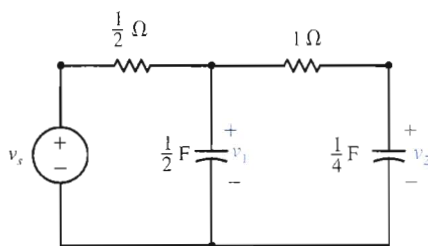


Fig. P3.66

3.67 For the circuit shown in Fig. P3.67, suppose that $v_s(t) = 6 \text{ V}$ for $t < 0 \text{ s}$ and $v_s(t) = 0 \text{ V}$ for $t \geq 0 \text{ s}$. Find $i(t)$ and $v(t)$ for all time.

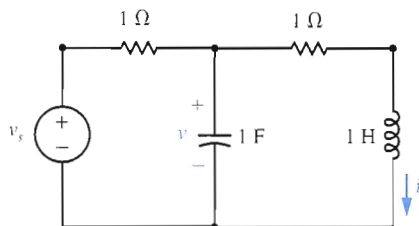


Fig. P3.67

3.68 For the circuit shown in Fig. P3.67, interchange the inductor and the capacitor. Suppose that $v_s(t) = 6 \text{ V}$ for $t < 0 \text{ s}$ and $v_s(t) = 0 \text{ V}$ for $t \geq 0 \text{ s}$. Find the capacitor voltage $v(t)$ and the inductor current $i(t)$ for all time.

3.69 For the parallel RLC circuit shown in Fig. P3.69, suppose that $R = 0.5 \Omega$, $L = 0.2 \text{ H}$, $C = 0.25 \text{ F}$, and $i_s(t) = 2u(t) \text{ A}$. Find the step responses $i(t)$ and $v(t)$.

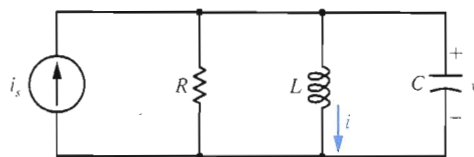


Fig. P3.69

3.70 For the parallel RLC circuit shown in Fig. P3.69, suppose that $R = 3 \Omega$, $L = 3 \text{ H}$, $C = \frac{1}{12} \text{ F}$, and $i_s(t) = 4u(t) \text{ A}$. Find the step responses $i(t)$ and $v(t)$.

3.71 For the series RLC circuit shown in Fig. P3.63, suppose that $R = 7 \Omega$, $L = 1 \text{ H}$, $C = 0.1 \text{ F}$, and $v_s(t) = 12u(t) \text{ V}$. Find the step responses $v(t)$ and $i(t)$.

3.72 For the series RLC circuit shown in Fig. P3.63, suppose that $R = 2 \Omega$, $L = 1 \text{ H}$, $C = 1 \text{ F}$,